

**CS221: Digital Design**

**<http://jatinga.iitg.ernet.in/~asahu/cs221/>**

# **FF, Register and Memory**

A. Sahu


Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

# Outline

- FF: Characterization Table and Equation
  - RS, D, JK and T Flip flop
- Register
  - Parallel Load, Parallel out : (PIPO)
  - Serial Load, Wrap around load, Serial out (SISO)
  - PISO, SIPO Register
- Multifunction Register : How to design?

# Given a D FF: Construct T FF

 

T	D	$TQ' + T'Q$
0	Q	$0Q' + 1Q$
1	Q'	$1Q' + 0Q$

$$D = TQ' + TQ$$

# Characteristic Equations

- A descriptions of the next-state table of a flip-flop
- Constructing from the Karnaugh map for  $Q_{t+1}$  in terms of the present state and input

# Characteristic tables

- The tables that we've made so far are called **characteristic tables**.
  - They show the next state  $Q(t+1)$  in terms of the current state  $Q(t)$  and the inputs.
  - For simplicity, the control input  $C$  is not usually listed.
  - Again, these tables don't indicate the positive edge-triggered behavior of the flip-flops that we'll be using.

J	K	Q+
0	0	$Q_t$
0	1	0
1	0	1
1	1	$Q_t'$

D	Q+
0	0
1	1

T	Q+
0	$Q_t$
1	$Q_t'$

# Characteristic equations

- We can also write **characteristic equations**, where the next state  $Q(t+1)$  is defined in terms of the current state  $Q(t)$  and inputs.

J	K	Q+
0	0	Q <sub>t</sub>
0	1	0
1	0	1
1	1	Q <sub>t</sub> '

$$\begin{aligned}Q_+ &= J'K'Q + JKQ_t' + JK' \\&= J'K'Q + JKQ' + JK'Q' + JK'Q \\&= J'K'Q + JK'Q + JKQ' + JK'Q' \\&= (J+J')K'Q + J(K+K')Q'\end{aligned}$$

$$Q^+ = K'Q + JQ'$$

$$Q(t+1) = K'Q(t) + JQ'(t)$$

# Characteristic equations

- We can also write **characteristic equations**, where the next state  $Q(t+1)$  is defined in terms of the current state  $Q(t)$  and inputs.

D	$Q^+$
0	0
1	1

$$Q^+ = D$$

$$Q(t+1) = D$$

T	$Q^+$
0	$Q_t$
1	$Q_t'$

$$Q^+ = T'Q + TQ' = T \oplus Q$$

$$Q(t+1) = T'Q(t) + TQ'(t) = T \oplus Q(t)$$

# Characteristic equations

	SR			
	00	01	11	10
0	0	0	-	1
1	1	0	-	1

$$Q^+ = S + R'Q \quad (SR=0)$$

Flip Flop Type	Characteristic Equation
SR	$Q^+ = S + R'Q \quad (SR=0)$
JK	$Q^+ = JQ' + K'Q$
D	$Q^+ = D$
T	$Q^+ = TQ' + T'Q = T \oplus Q$



# FF with Asynchronous Inputs


- S-R, D and J-K inputs are synchronous inputs
  - As data on these inputs are transferred to the flip-flop's output
  - Only on the triggered edge of the clock pulse.
- **Asynchronous** inputs affect the state of the flip-flop independent of the clock
- Example:
  - *Preset (PRE) and clear (CLR)*
  - or *direct set (SD) and direct reset (RD)*

# FF with Asynchronous Inputs

- When  $PRE=HIGH$ ,  $Q$  is immediately set to HIGH.
- When  $CLR=HIGH$ ,  $Q$  is immediately cleared to LOW.
- Flip-flop in normal operation mode when both  $PRE$  and  $CLR$  are LOW.

 
# Asynchronous Inputs

- A J-K flip-flop with active-LOW preset and clear inputs.



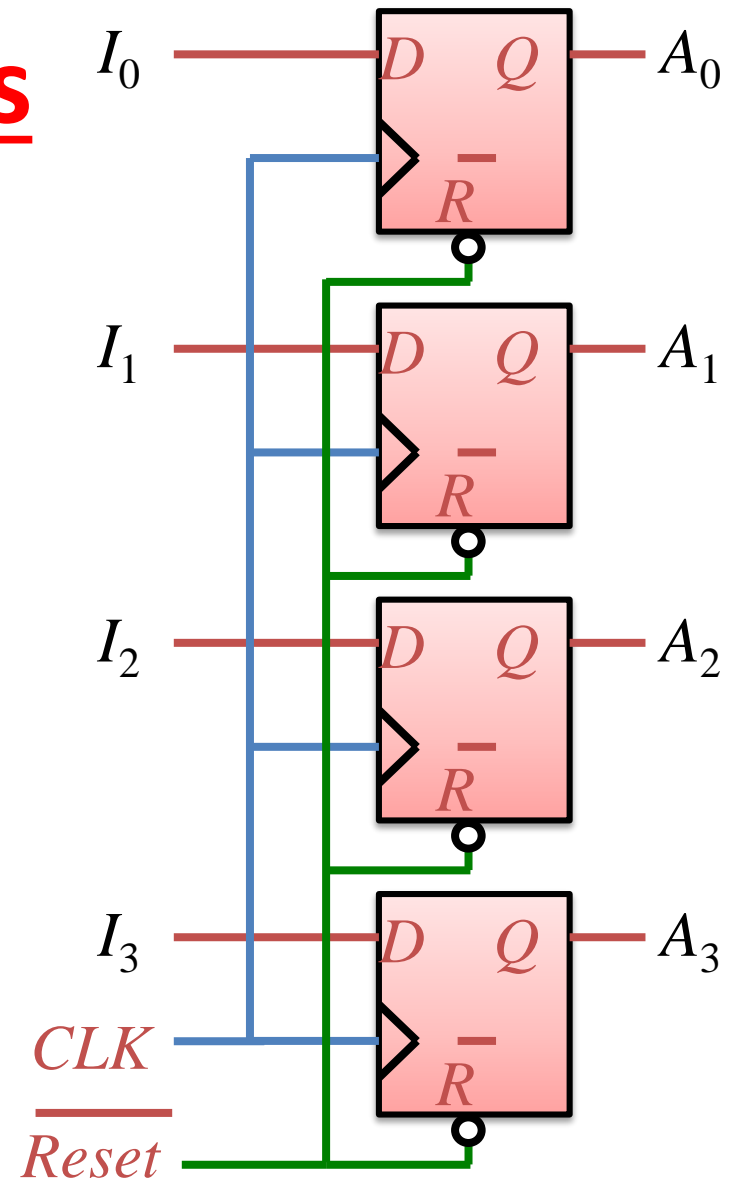
# Registers


- Group of  $D$  Flip-Flops
- Synchronized (Single Clock)
- Store Data



# Registers

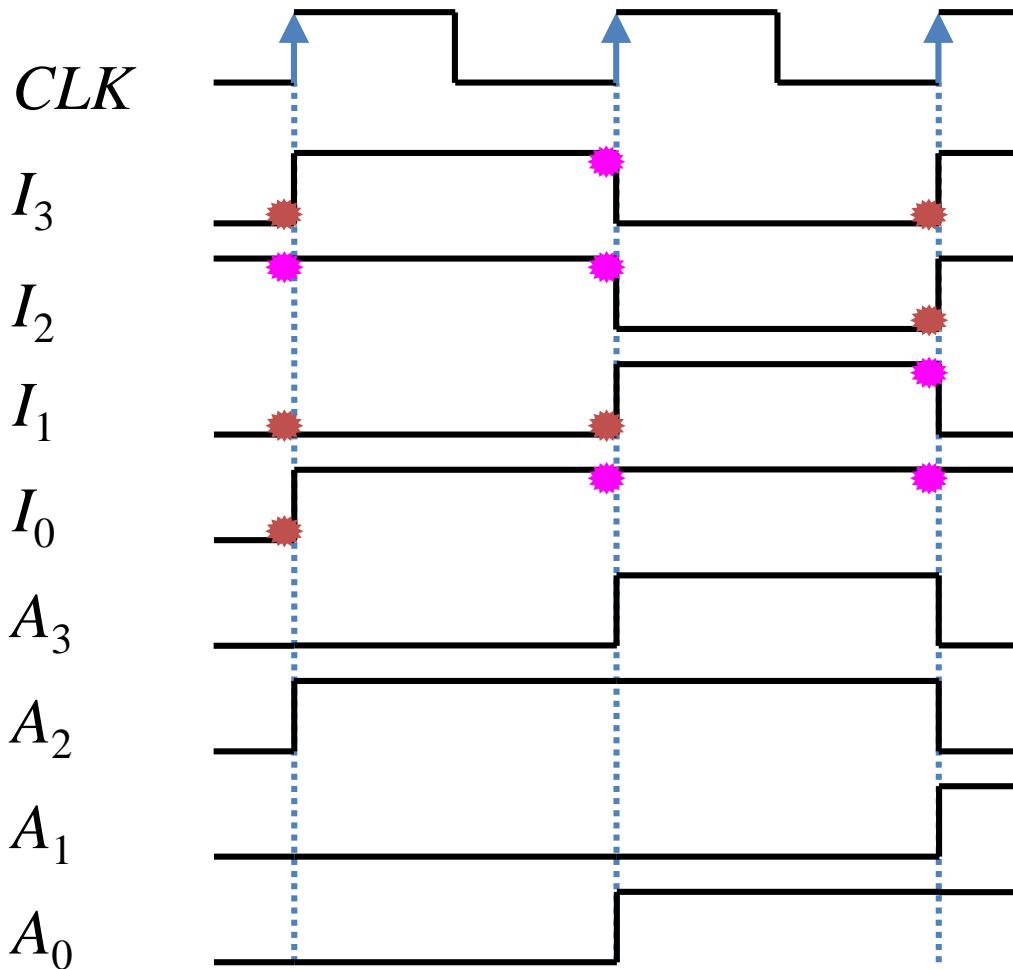

 
*Note:* New data has to go in with every clock



See carefully: Input at the dotted will be reflected to output : Just before rising edges
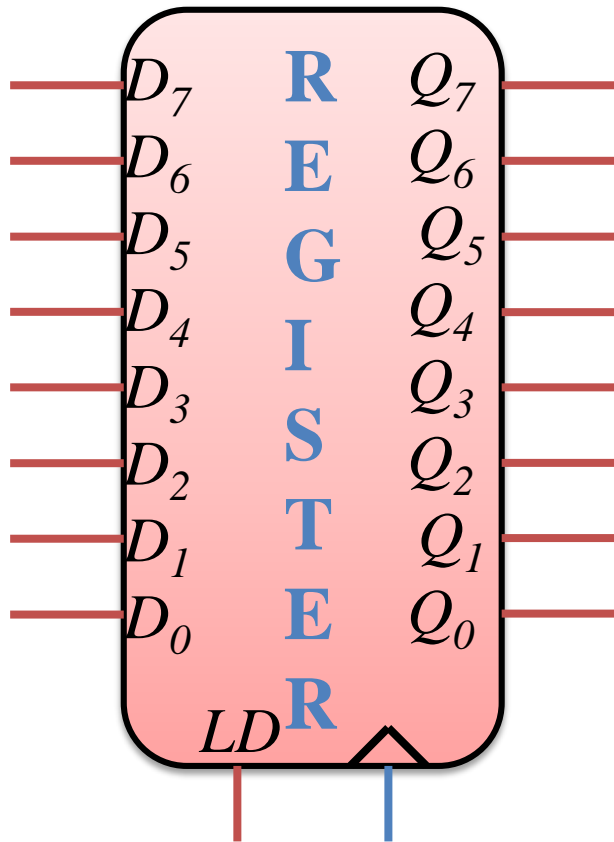
# Registers with Parallel Load


- Control **Loading** the Register with New Data



LD	$Q(t+1)$
0	$Q(t)$
1	D

 
# Registers with Parallel Load

- Should we block the “Clock” to keep the “Data”?



# Registers with Parallel Load

- Circulate the “old data”

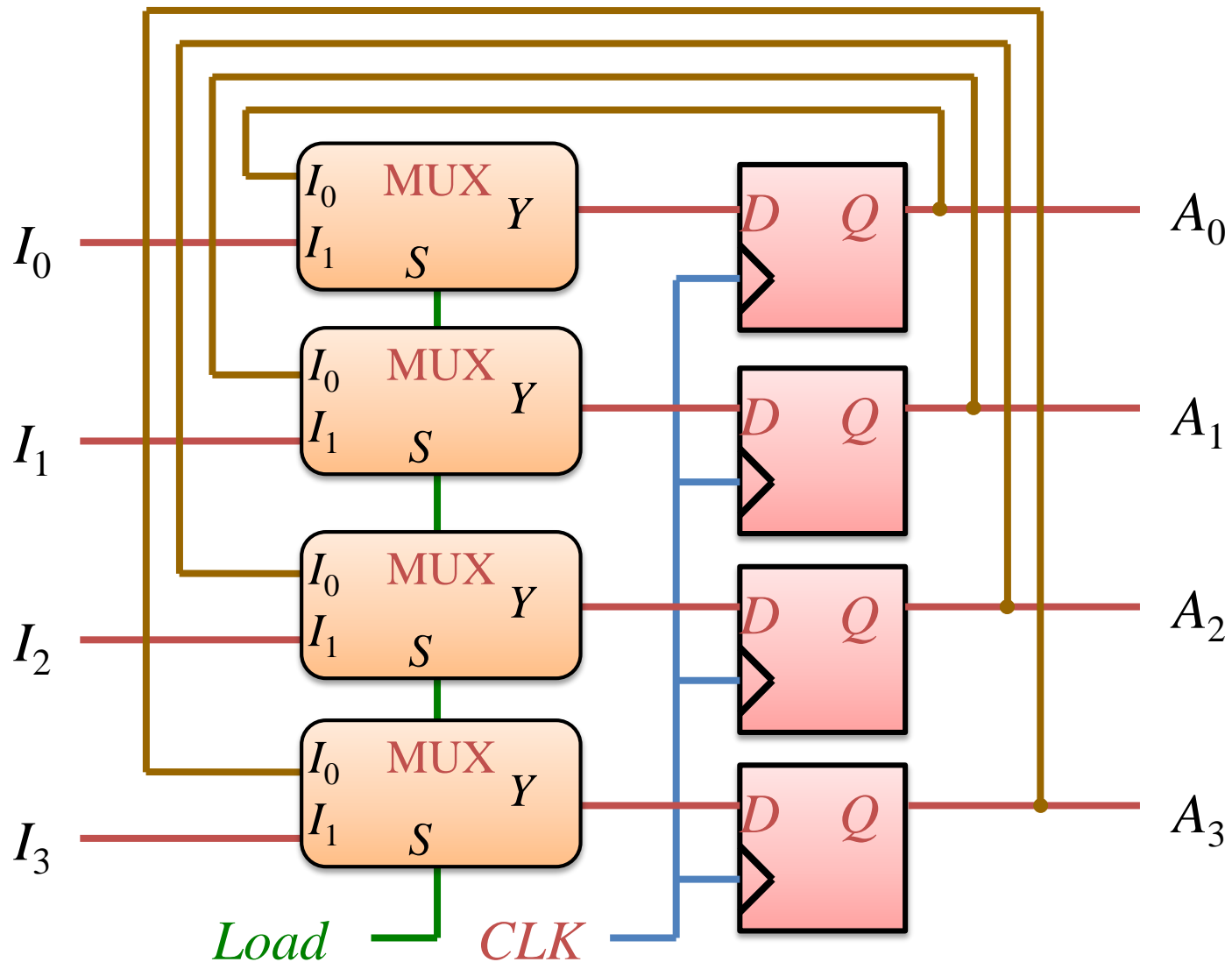



# **Shift Registers**

- Register (Set of FFs)
- 4-Bit Shift Register (Example)
- Serial in Serial Out (SISO)

# Shift Register

- Right Shift Example (Left shift is similar)
  - Move each bit one position right
  - Shift in 0 to leftmost bit

Q: Do four right shifts on 1001, showing value after each shift


A: 1001 (original)

0100


0010

0001


0000

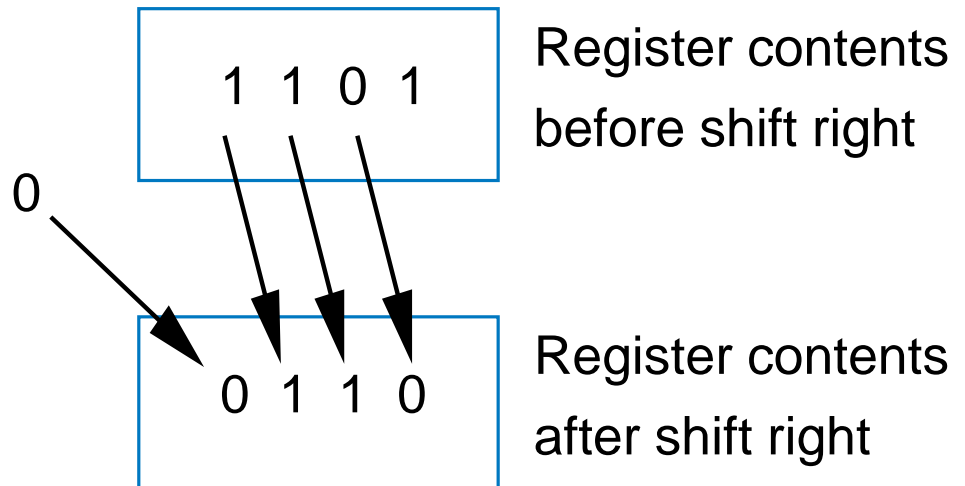

# Shift Register

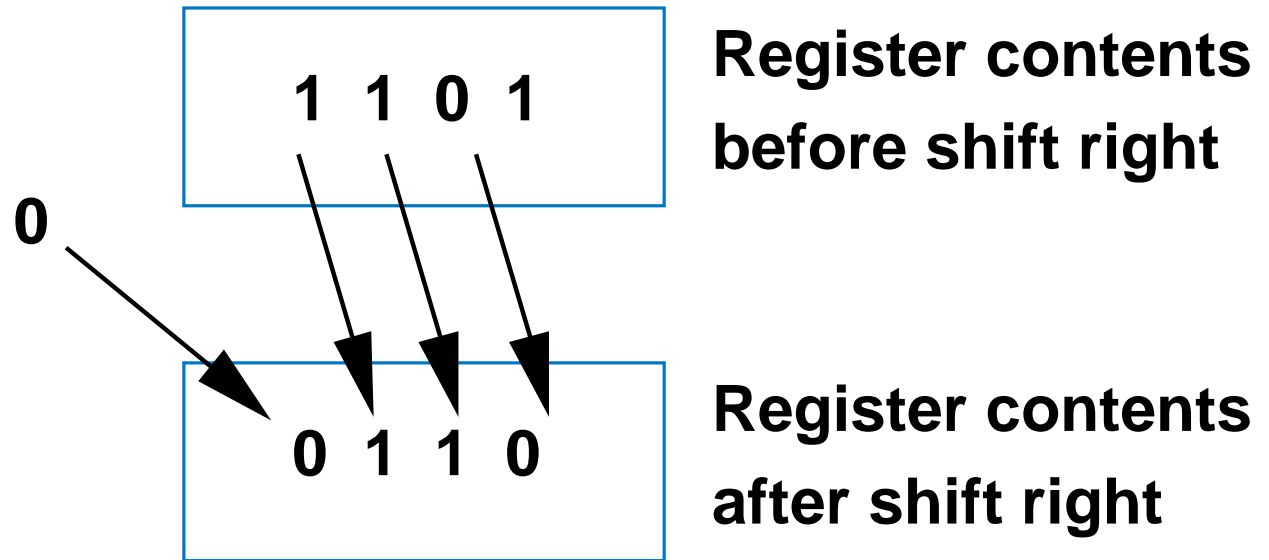


 - **Implementation: Connect flip-flop output to next flip-flop's input**



 
# Shift Registers

- 4-Bit Shift Register
- Serial in Serial Out (SISO)




# Shift Registers (SISO)

 

 
# Shift Register with Control

- To allow register to either shift or retain, use 2x1 muxes
  - **Shift Control: shr: 0 means retain, 1 shift**
  - shr\_in: value to shift in : May be 0/1, or right most bit



 
# Shift Register with Control

Shift Control=1, Do one right shift per cycle




# Shift Register with Control

Shift Control=0, No change to Data

 




# Shift Register with Control

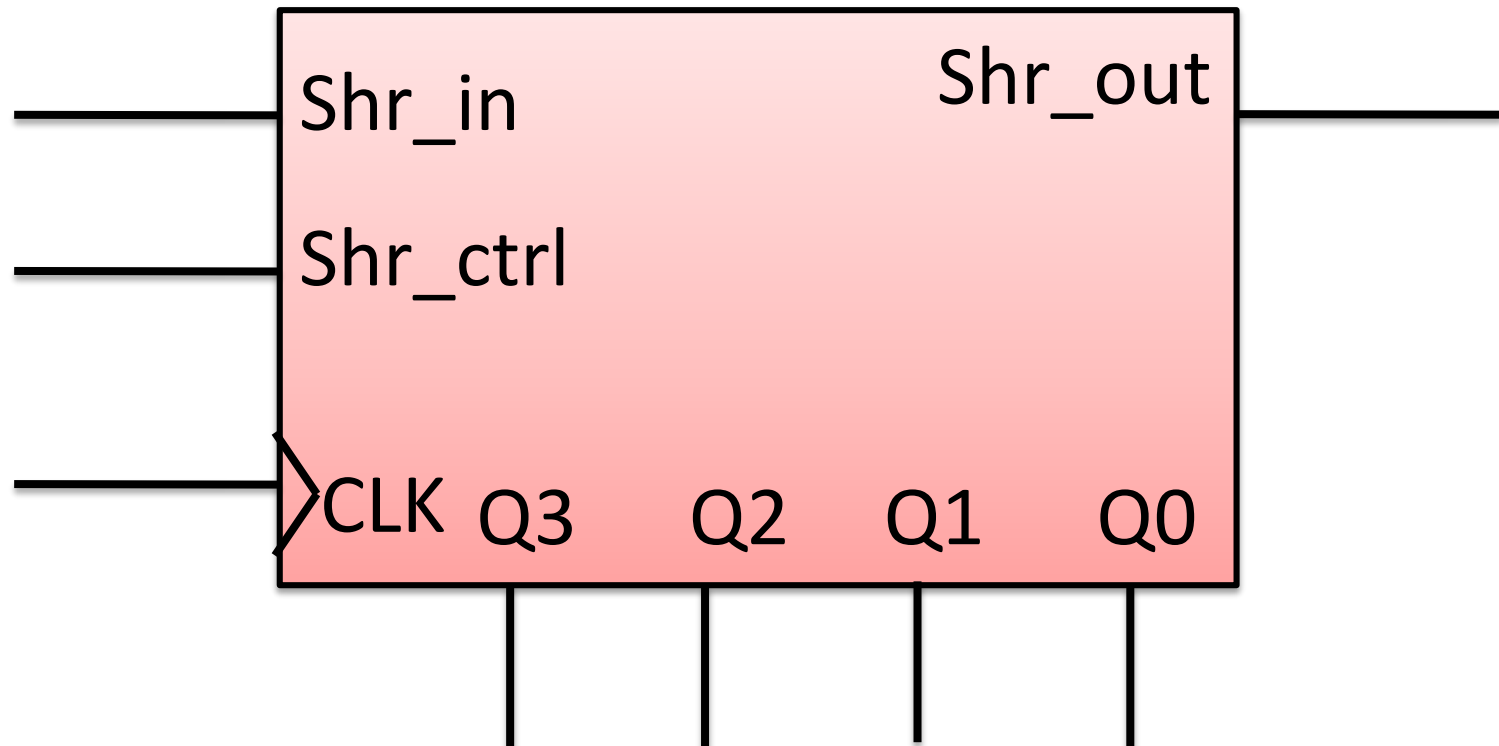

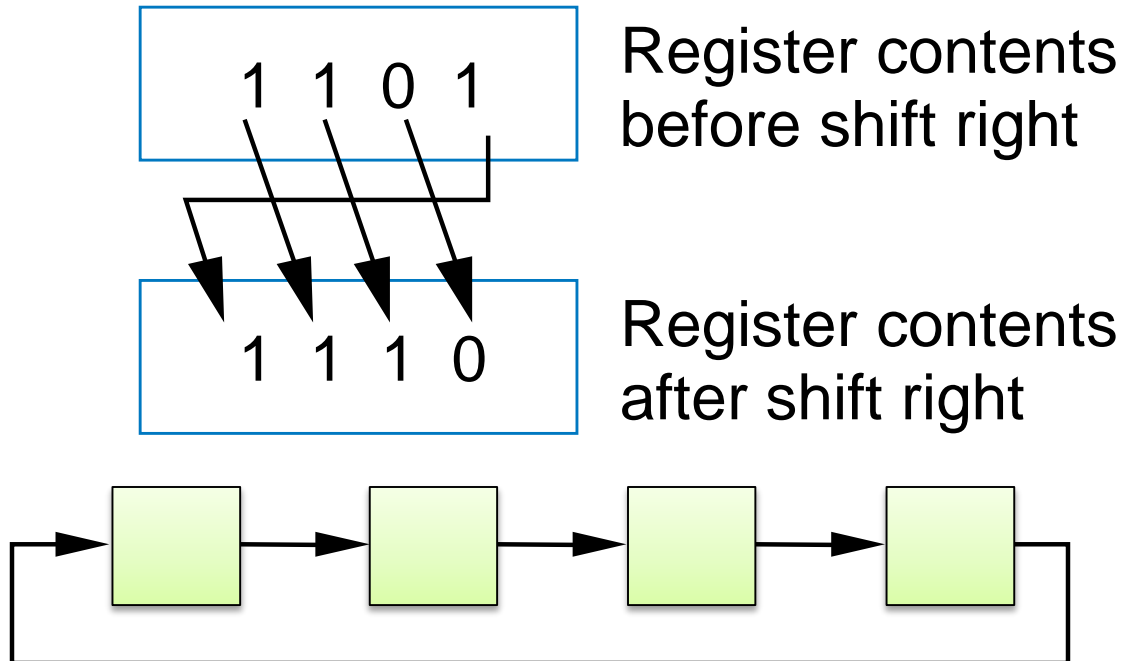
# Rotate Register

- Rotate right: Like shift right, but leftmost bit comes from rightmost bit




# Serial Transfer

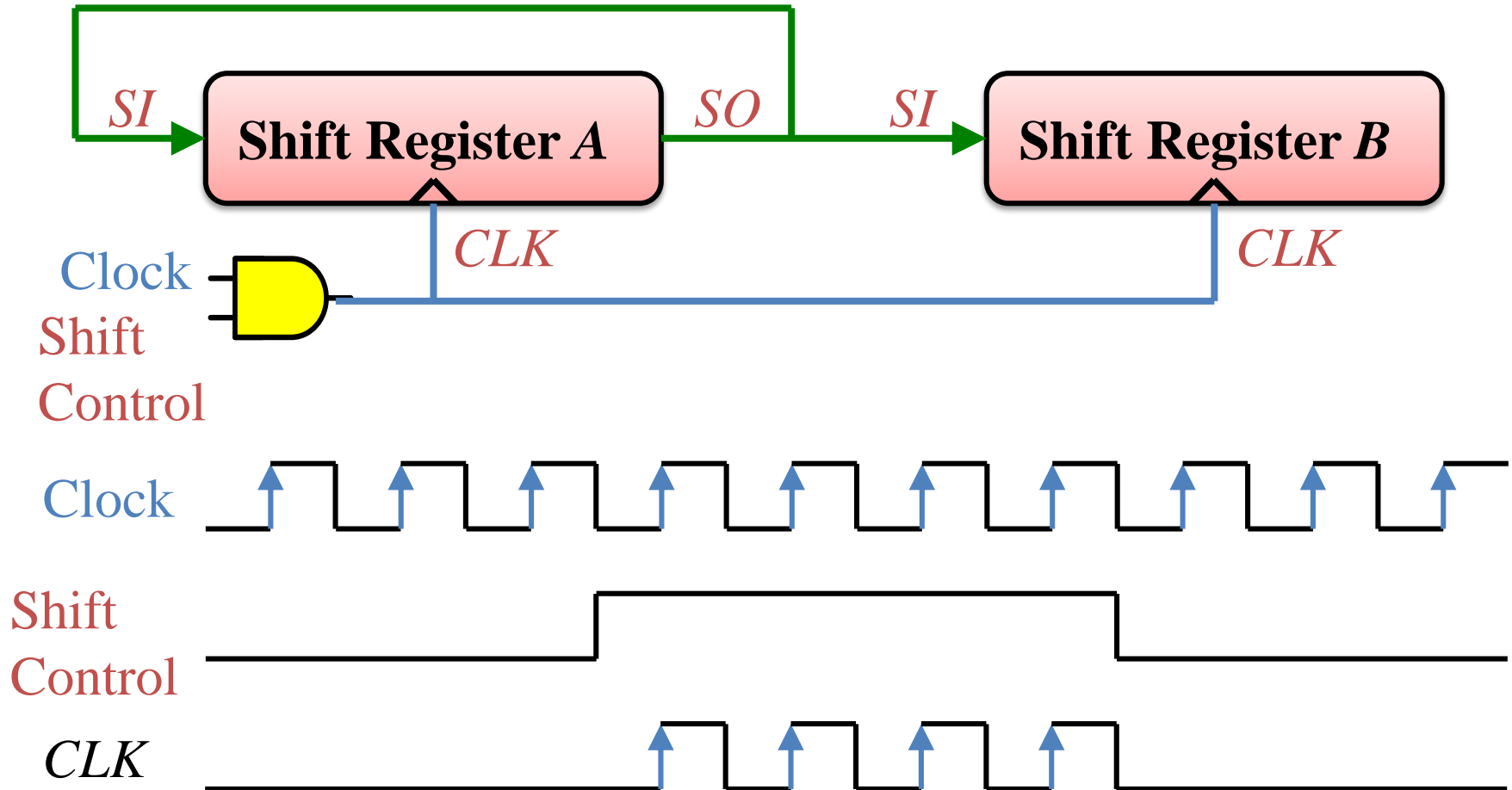


# N-Bit RCA: Series of FA Cells

- To add two n-bit numbers

 


 - Adder delay =  $T_c * n$
- $T_c = (C_{in} \text{ to } C_{out} \text{ delay}) \text{ of a FA}$



# N-Bit Ripple-Carry Adder


- To add two n-bit numbers

 

- Any point of time: only one FA is active

**Do we require N Full Adder?**


# Serial Addition

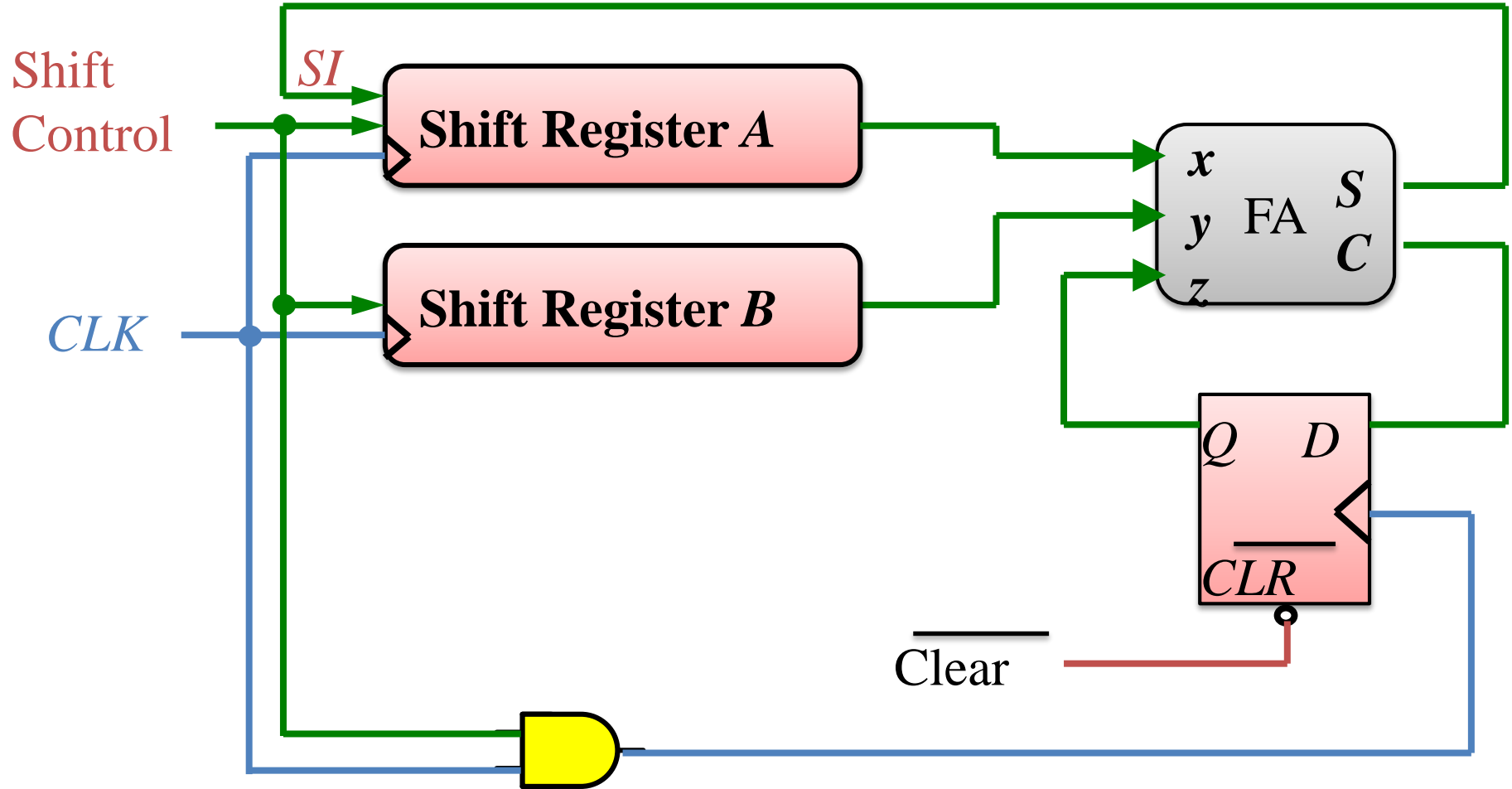

# Universal Shift Register

- Parallel-in Parallel-out (PIPO)
- Serial-in Serial-out (SISO)
- Serial-in Parallel-out (SIPO)
- Parallel-in Serial-out (PISO)

# Universal Shift Register

 




# Universal Shift Register

How to design  
such an USR?


# Universal Shift Register

 


# Operation Table for USR

S1	S0	Register Operation
0	0	No Change
0	1	Shift Right
1	0	Shift Left
1	1	Parallel Load


# Universal Shift Register: $S_1S_0=00$

 


# Universal Shift Register: $S_1S_0=01$

 

# Universal Shift Register: $S_1S_0=10$

 

# Universal Shift Register: $S_1S_0=11$

 

# Design of Multifunction Register


- M function N bit Register
  - Last example : 4 functions and 4 bits register
- N number of  **$\text{ceil}[\text{Log}_2 M] \times 2^{\text{ceil}[\text{Log}_2 M]}$**  size Multiplexor (Mux)
  - For 4 function 2x4 Mux
  - For 5 function 3x8 Mux
- Extra functions of Mux need to shunted (ignored) to do no work
  - For 5 function need a 3x8 Mux, we need to shunt  $8-5=3$  lines shunted (ignored) to do no work




# Memory

- Universal register : One register with many functionality
- Many registers clubbed with less functionality
  - No Shift
- Parallel load (In) or Parallel Out to a specific register
- Multiplexors used for selection of registers


# Register(PIPO)

 


# Register(PIPO)

 

# Tri-state Buffer

 

# Register with Read and write control

 


If  $S = 0$ , TS1 and TS2 will be open


$S=1$ ,  $RW=1$  , Write to Register 4 bit of data

$S=1$ ,  $RW=0$ , Read data from Register


# Register with Read and write control

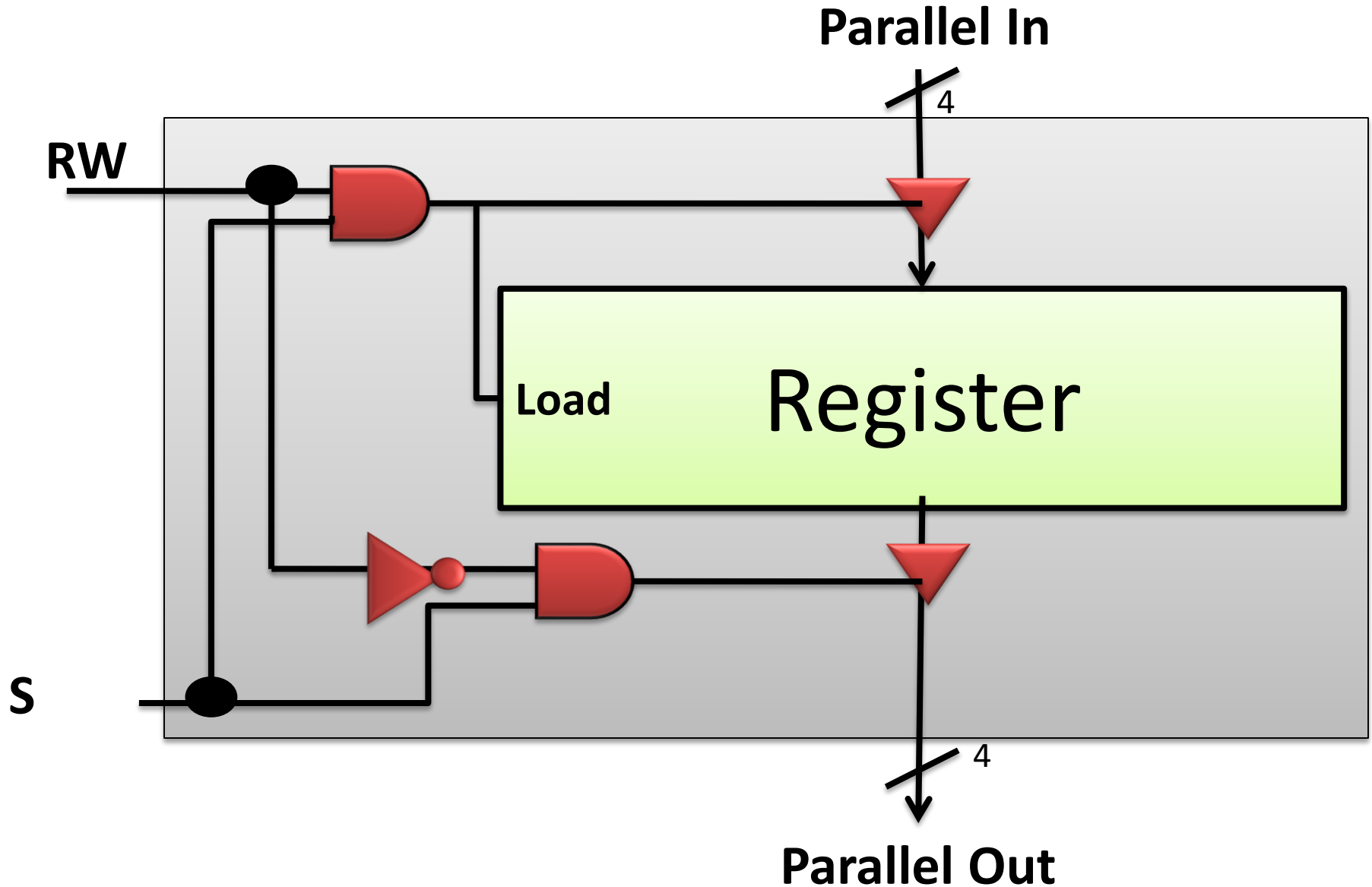

# Many Register with RW control

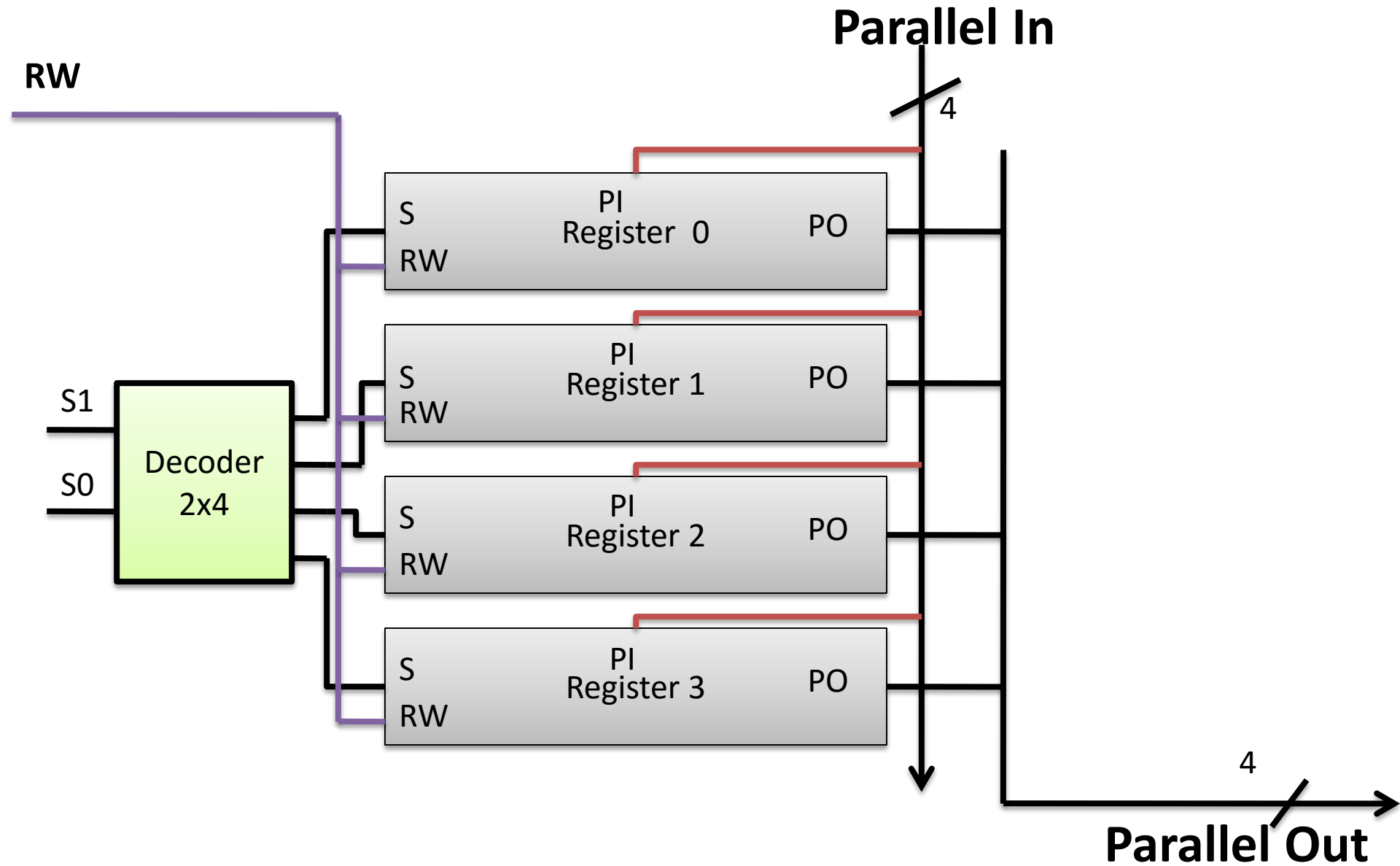


# Many Register with RW control

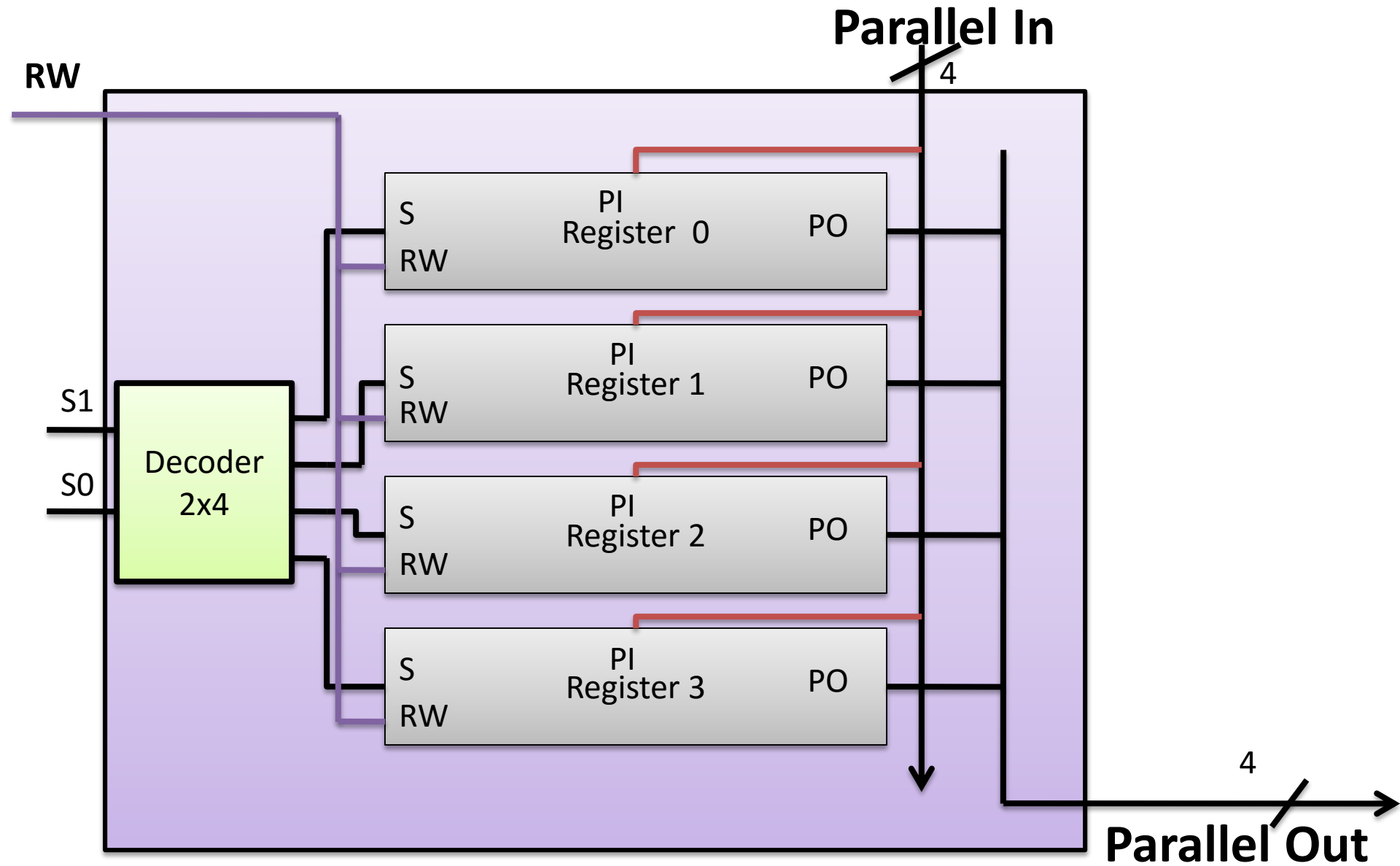





# Memory with MAR and MDR

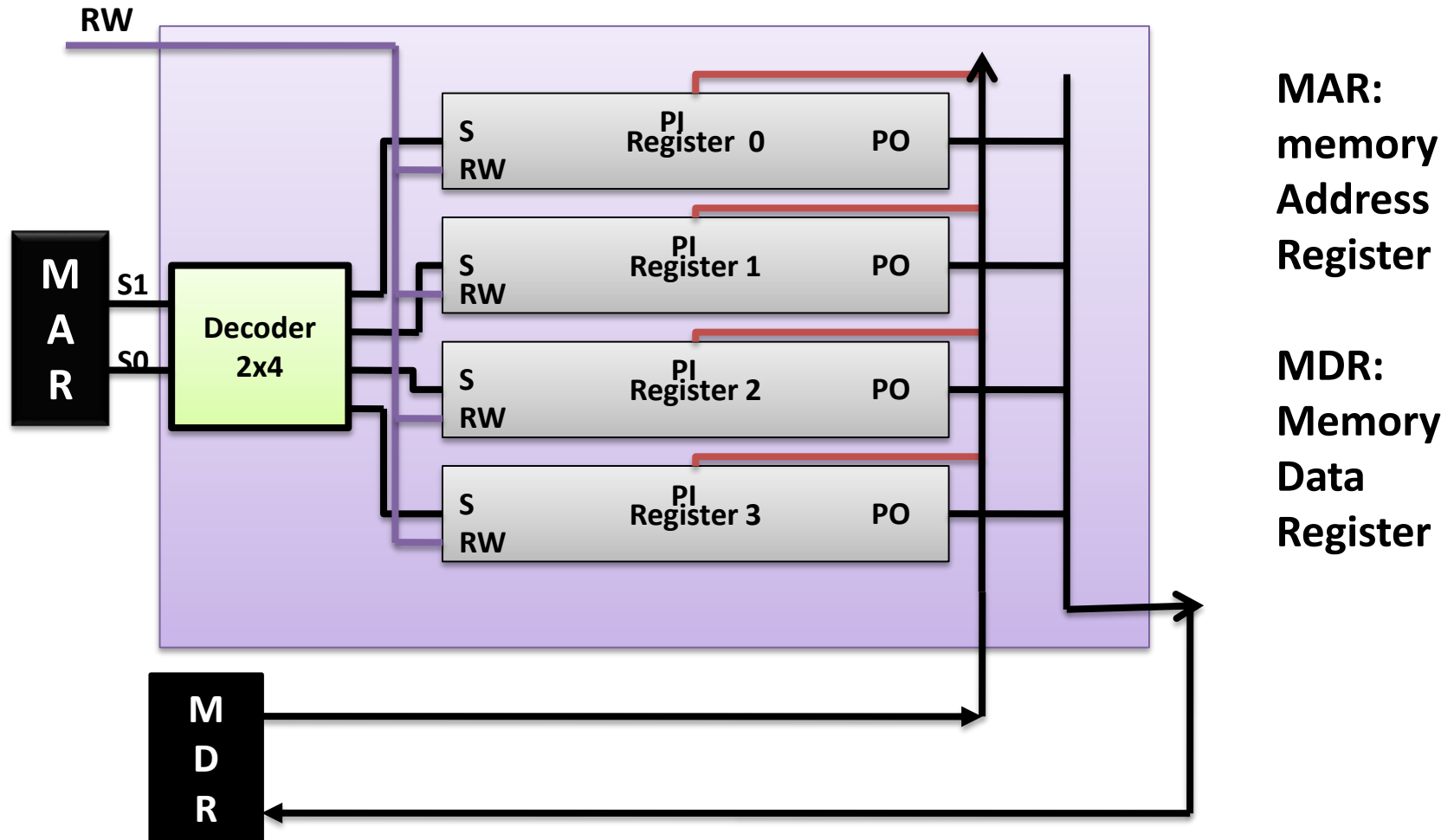
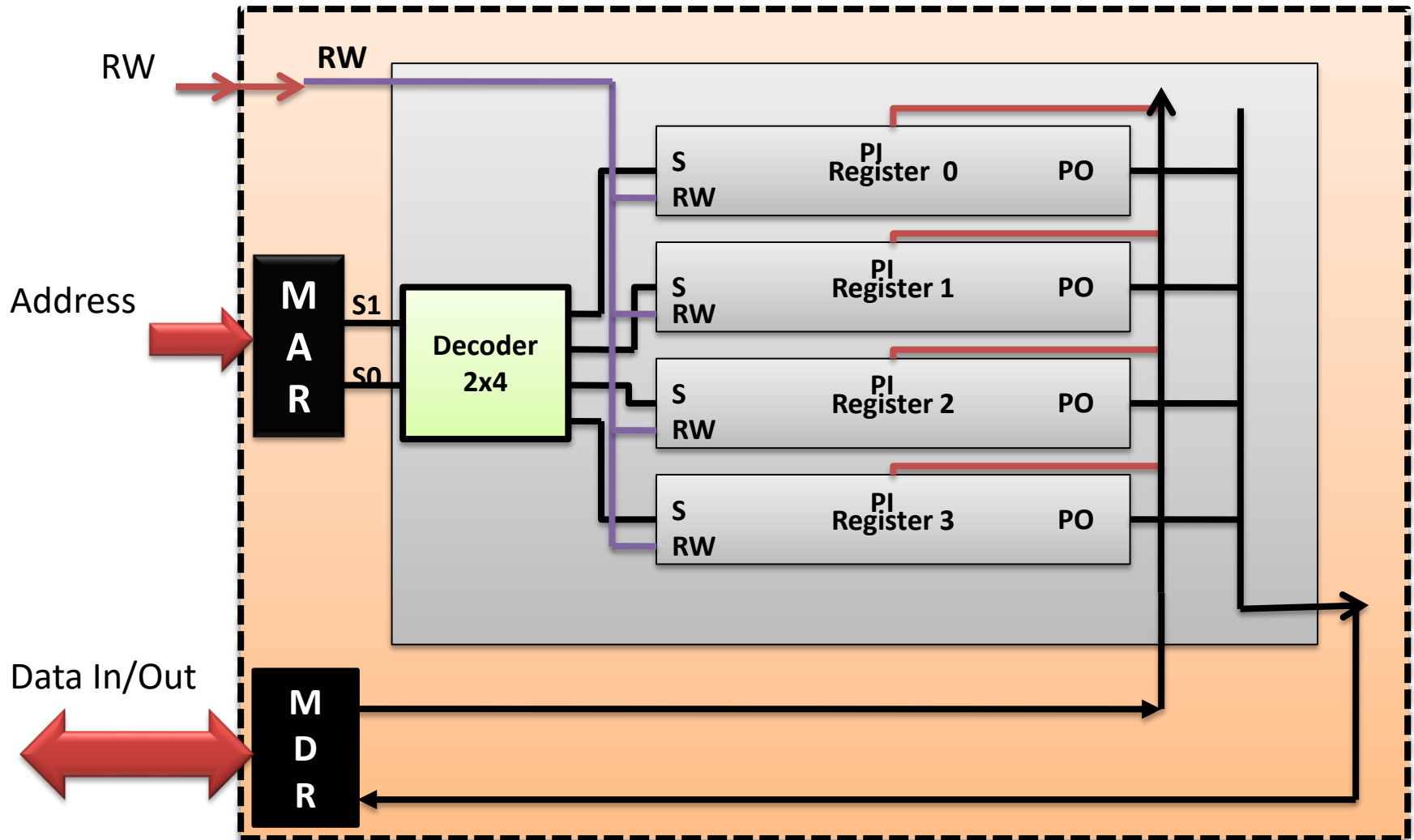
# Many Register with RW control: 4 four bit word Memory




# General Memory

 

# Memory : Locations & Word size

- ADDRESS decides the number of memory location
- MDR size : decides the WordSize
- Number of registers :  $2 + \text{NumLocations}$ 
  - $2 + 2^{\text{AddressSize}}$
  - 1 for MBR, 1 for MAR
- $\text{NumFF} = \text{MARsize} + \text{MDRsize} + \text{NumLoc} * \text{MDRSize}$

# Designing 1KB Mem using two 1KN Mem

 

**Thanks**