

CS221: Digital Design

<http://jatinga.iitg.ernet.in/~asahu/cs221>

Finite State Machine

A. Sahu

Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

Outline

- Digital Clock Design
- Finite State Machine
- Formal definition
- State machine types
- FSM implementation

Design of Digital Wall Clock


- Given 256Mhz Clock Quartz and other Digital components





Design of Digital Wall Clock

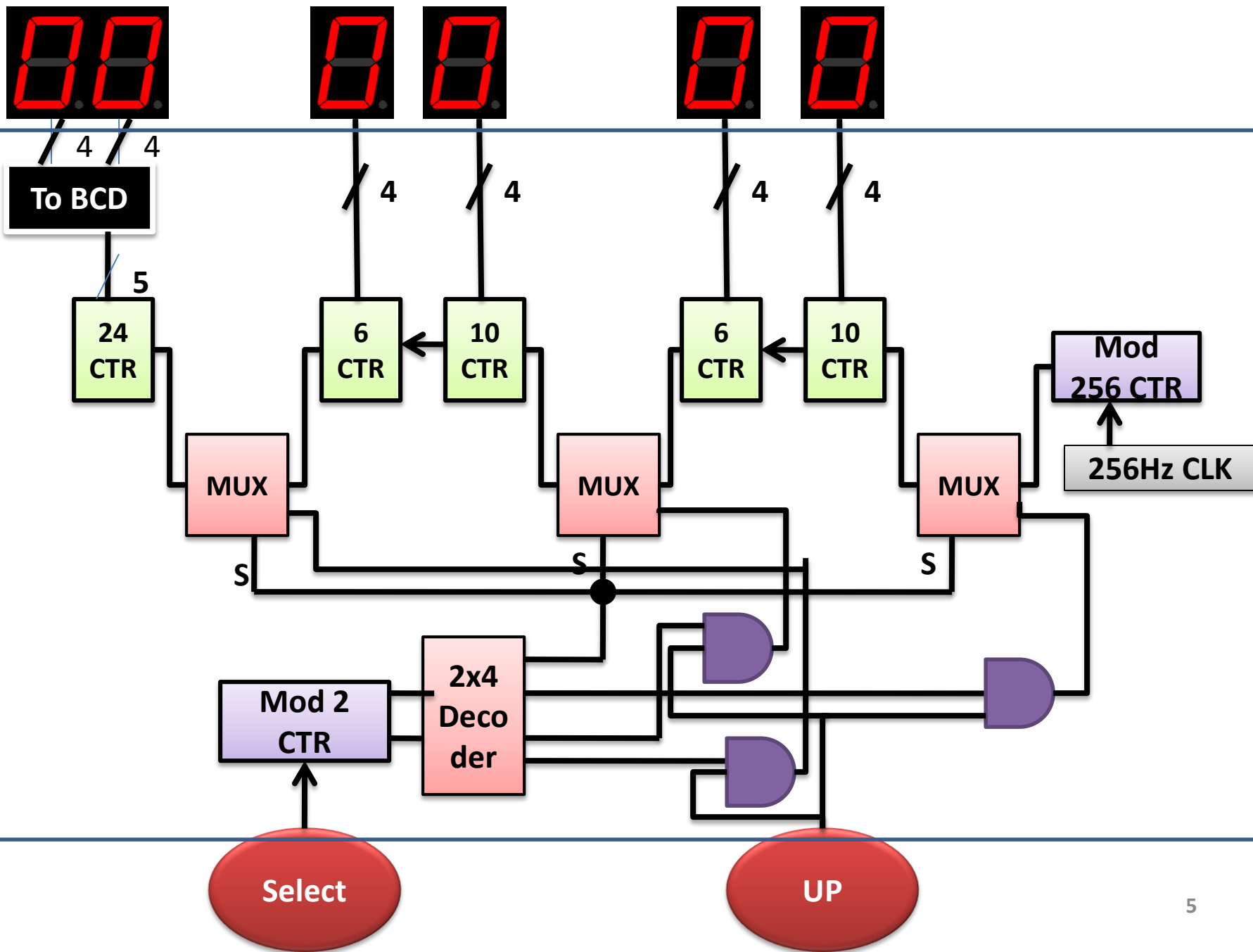
- Given 256Mhz Clock Quartz and other Digital components
- Design a Wall Clock
 - To display time : HH : MM :SS format
 - Should support Reset/Adjust of time using selectable switch
 - Button 1: for select the Mod Ctr
 - Button 2: increasing select mod Ctr






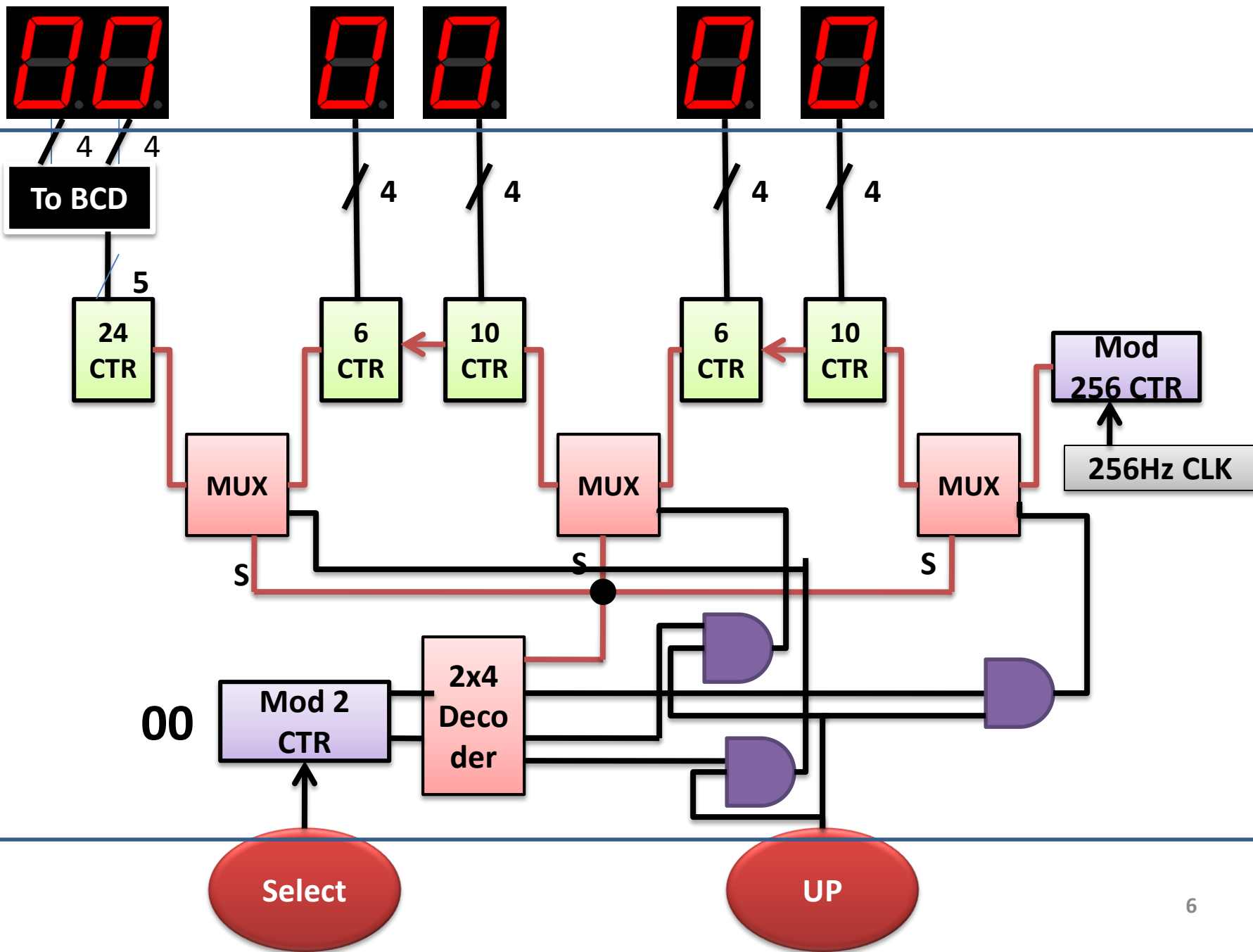

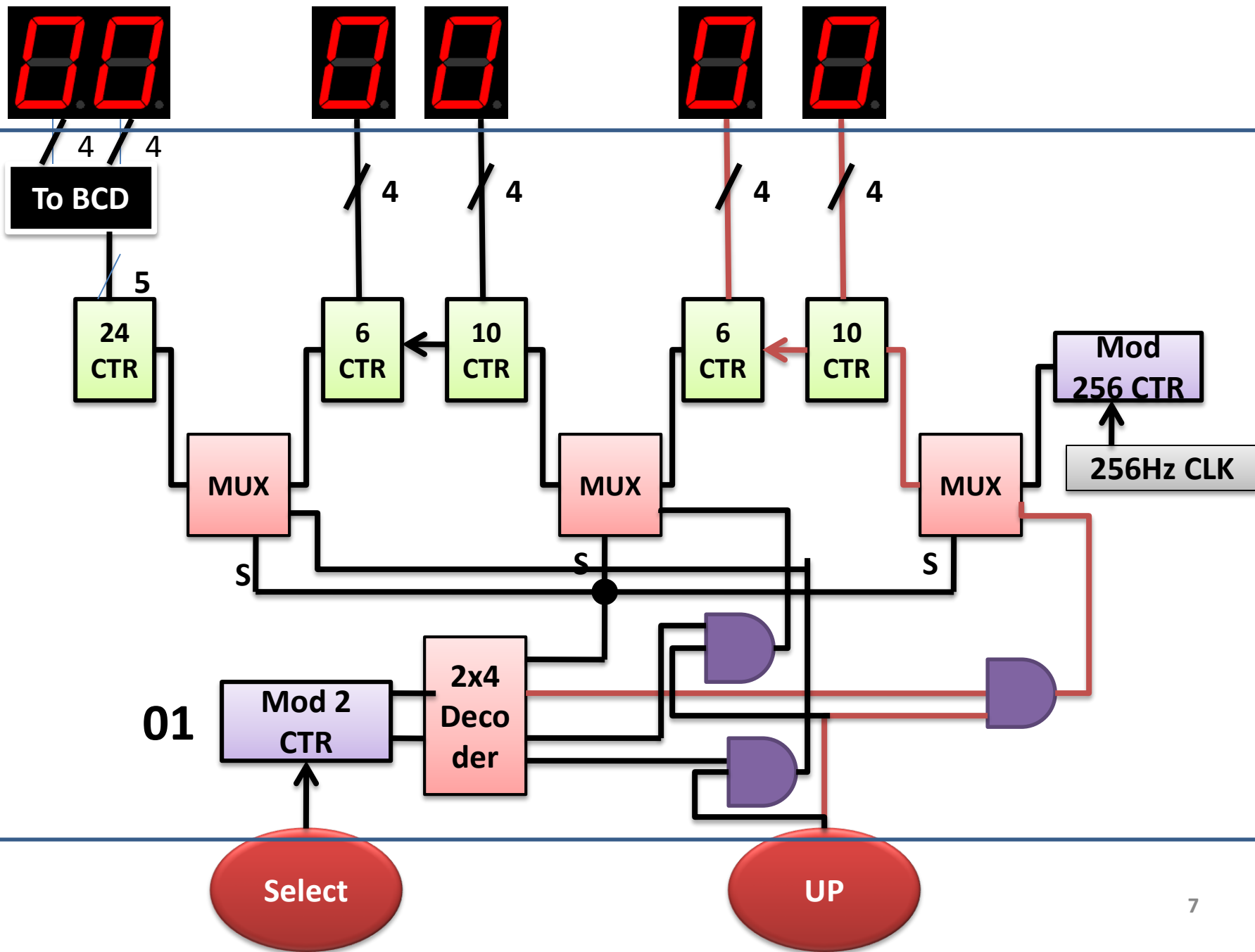

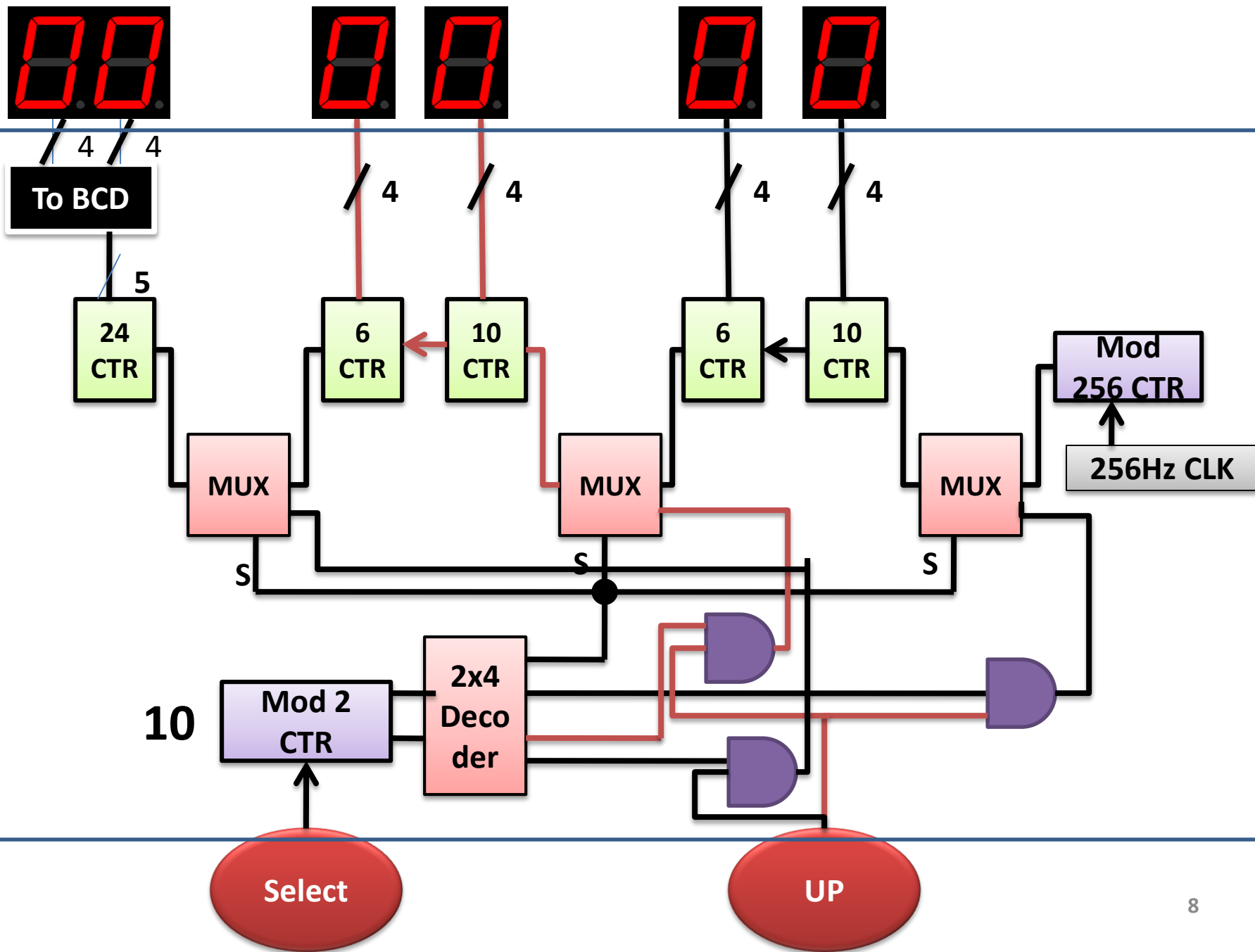

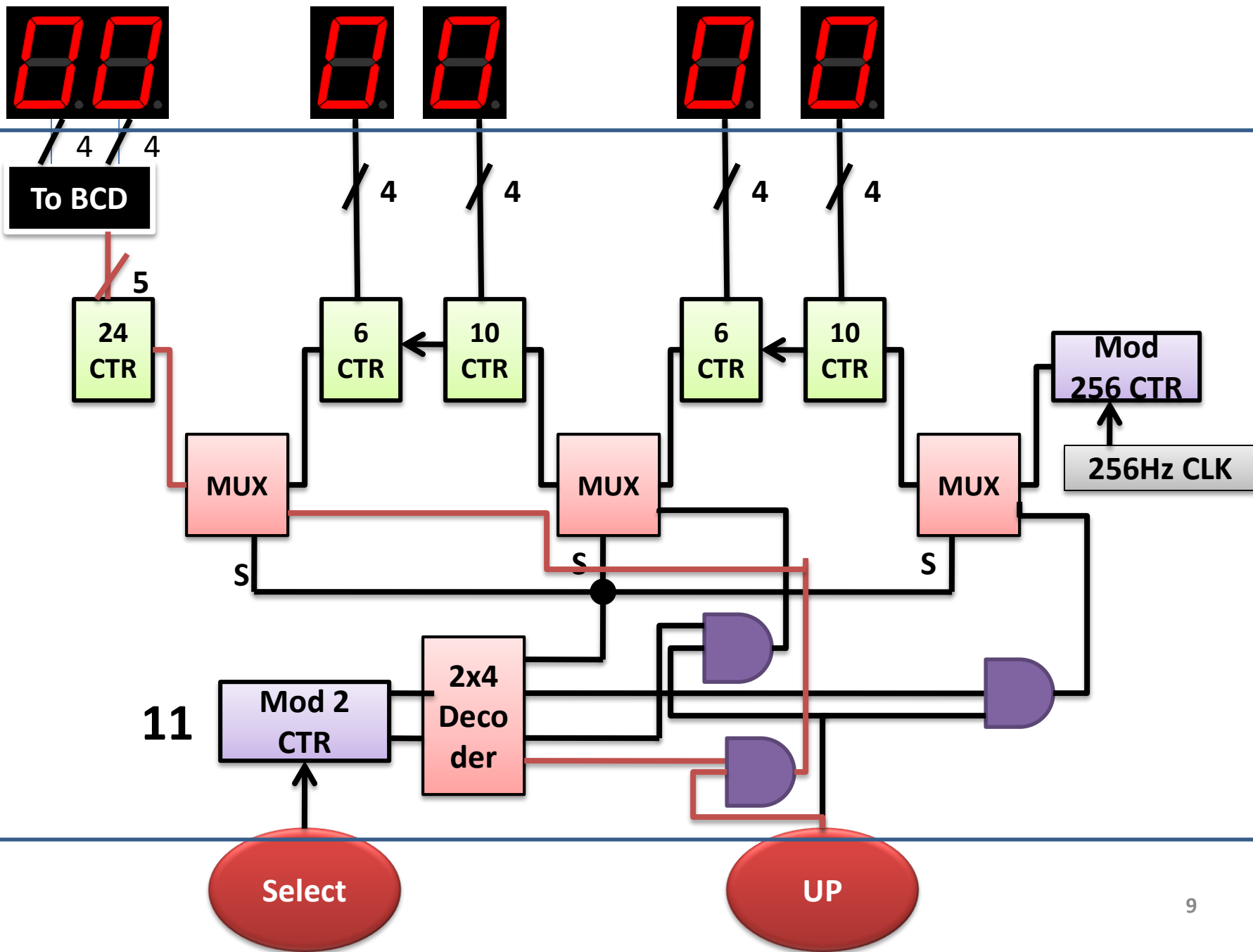

Sequential Circuit: FSM


- Combinational Circuit : Formal Approach
 - Boolean Algebra
 - Circuit Minimization (K-Map, Quine McCluskey, Espresso...)
- Sequential Circuit : Formal Approach
 - Finite State Machine

Formally Describe/mathematically Describe

Boolean Algebra: Working Combinational Circuit

Finite State Machine: Working of Sequential Circuit

Sequential Circuit: FSM

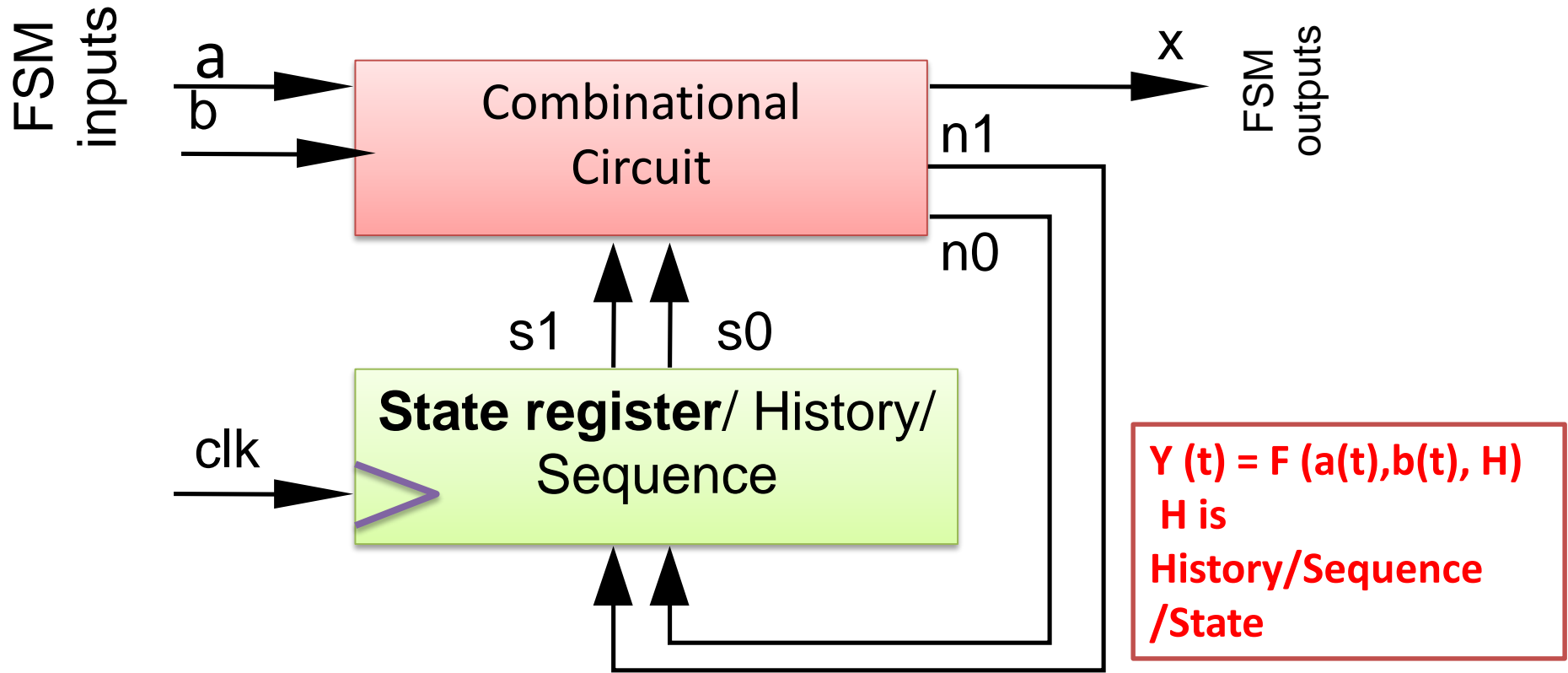

Formally Describe/mathematically Describe

Boolean Algebra: Working Combinational Circuit

Finite State Machine: Working of Sequential Circuit

Boolean Combinational Circuit

- Can you formally model All Boolean Combinational Circuit using Boolean Algebra?



Already Designed Sequential Circuit

- Flip Flops (RS, JK, T, D)
- Register (Shift, PIPO), Memory
- Counter : Async, Sync, Modulo Counter
- Counter using Shift register


Till now we have not used
formal Approach to design
these

Need a Better Way to Design Sequential Circuits

- Combinational circuit design process had two important things
 1. A formal way to describe desired circuit behavior
 - Boolean equation, or truth table
 2. A well-defined process to convert that behavior to a circuit
- We need those things for sequence circuit design

Sequential Circuit

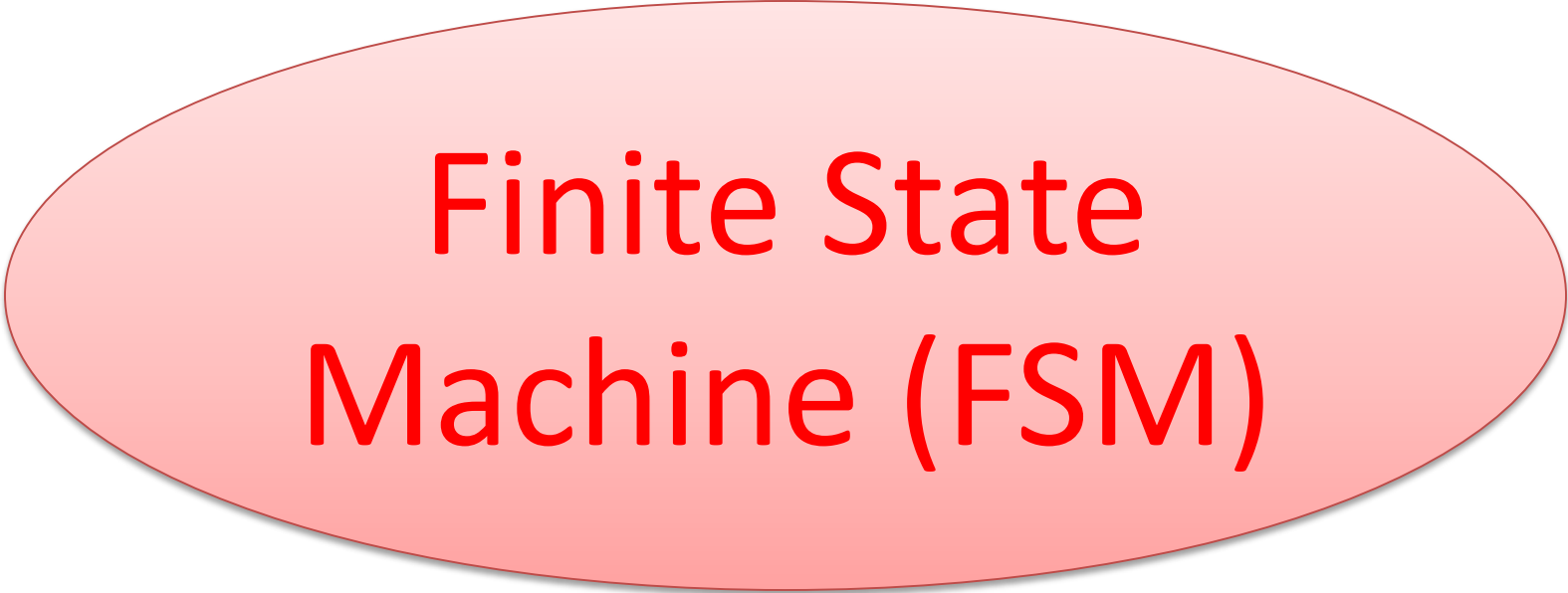- Can we model All Synchronous Sequential Circuit using some model?



Finite State
Machine (FSM)

Finite State Machine

- Finite-State Machine (FSM)
 - A way to describe desired behavior of sequential circuit
 - Akin to Boolean equations for combinational behavior
 - List states, and transitions among states

FSM Types

- Two main types of FSMs
 - Moore FSM : output is only function of state
 - Mealy FSM: output is function of state and inputs

Set Theoretic Description

Moore Machine is an ordered quintuple

$$M o o r e = (S, I, O, \delta, \lambda)$$

where

S = Finite set of states $\neq \Phi, \{s_1, s_2, \dots, s_n\}$

I = Finite set of inputs $\neq \Phi, \{i_1, i_2, \dots, i_m\}$

O = Finite set of outputs $\neq \Phi, \{o_1, o_2, \dots, o_l\}$

δ = Next state function which maps $S \times I \rightarrow S$

λ = Output function which maps $S \rightarrow O$

Set Theoretic Description

Mealy Machine is an ordered quintuple

$$\text{Mealy} = (\mathbf{S}, \mathbf{I}, \mathbf{O}, \delta, \beta)$$

where

\mathbf{S} = Finite set of states $\neq \Phi, \{s_1, s_2, \dots, s_n\}$

\mathbf{I} = Finite set of inputs $\neq \Phi, \{i_1, i_2, \dots, i_m\}$

\mathbf{O} = Finite set of outputs $\neq \Phi, \{o_1, o_2, \dots, o_l\}$

δ = Next state function which maps $\mathbf{S} \times \mathbf{I} \rightarrow \mathbf{S}$

β = Output function which maps $\mathbf{S} \times \mathbf{I} \rightarrow \mathbf{O}$

Clocked synchronous FSM


- **Clocked**
 - All storage elements employ a clock input (i.e. all storage elements are flip-flops)
- **Synchronous**
 - All of the flip flops use the same clock signal

Clocked Asynchronous FSM


- **FSM**
 - State machine is simply another name for sequential circuits. Finite refers to the fact that the number of states the circuit can assume is finite
- **Async FSM:** A synchronous clocked FSM changes state only when a triggering edge (or tick) occurs on the clock signal

Clocked synchronous FSM structure

 - **States:** determined by possible values in sequential storage elements
- **Transitions:** change of state
- **Clock:** controls when state can change by controlling storage elements




Moore machine

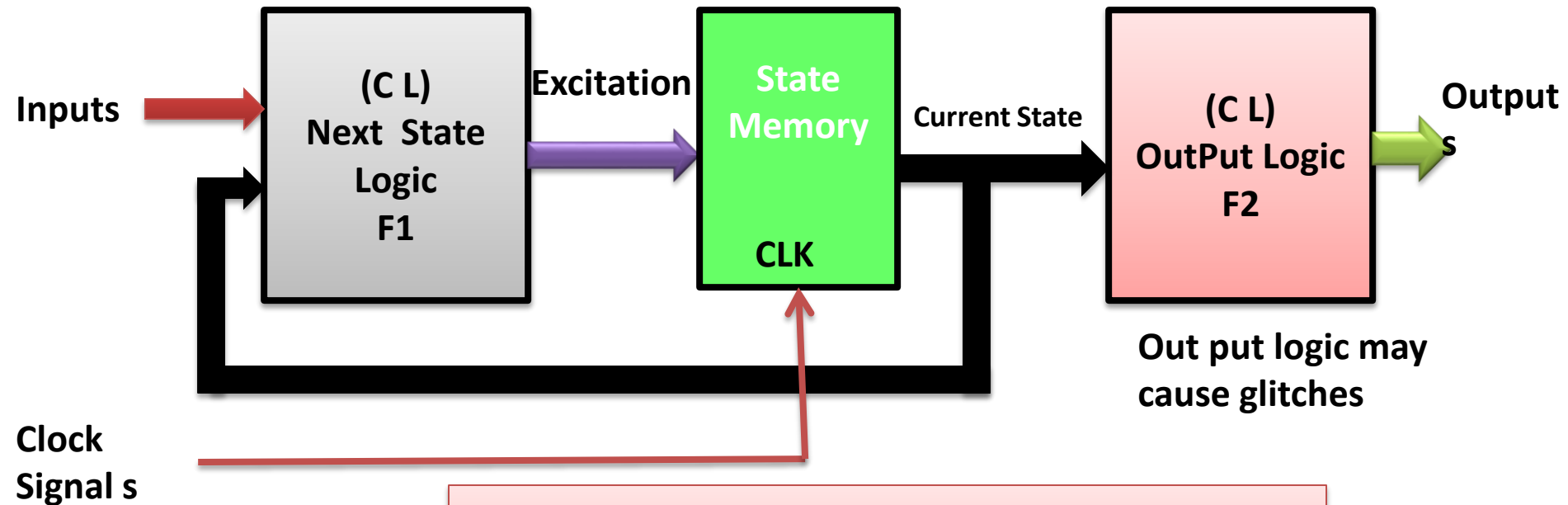

Next state = $F_2(\text{current state, inputs})$
Output = $G_2(\text{current state})$

Mealy machine

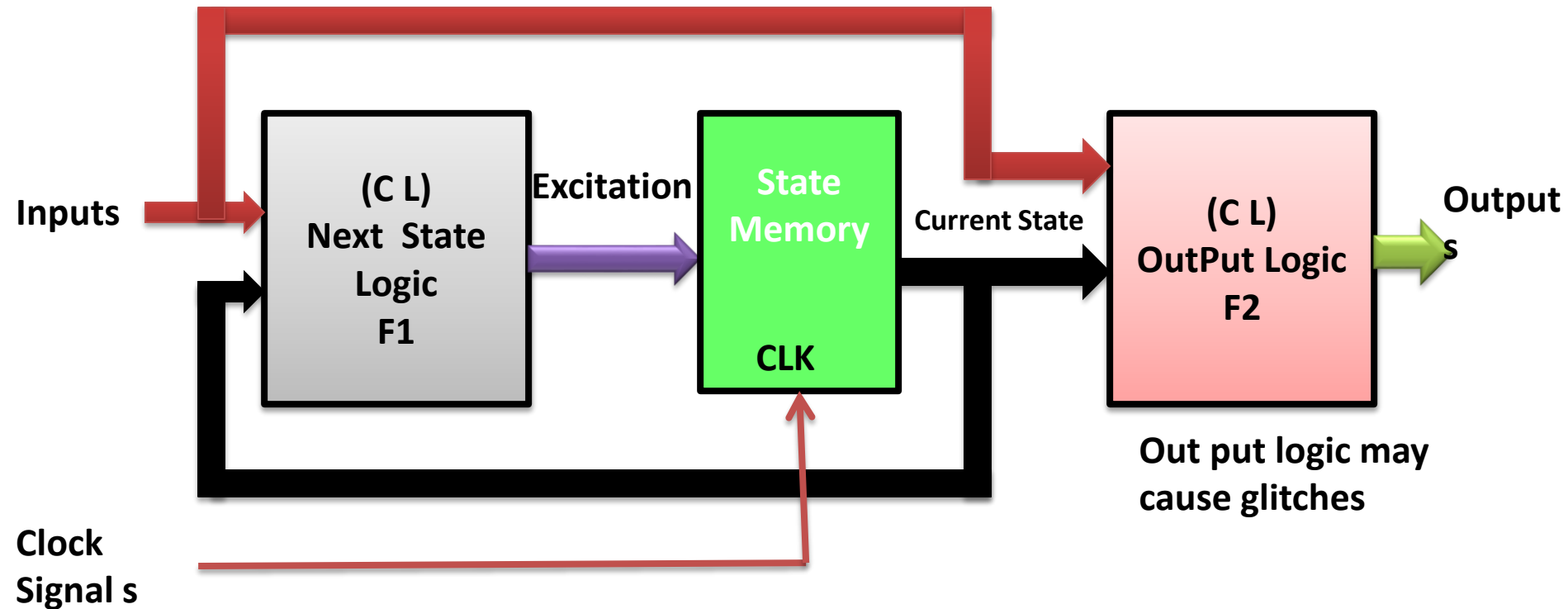
- A Much better name of State “Memory” is State Storage



State Storage= Set of n FFs
 2^n State can be stored

Next state = $F_1(\text{current state, inputs})$
Output = $F_2(\text{current state, inputs})$

Moore machine: For next some examples

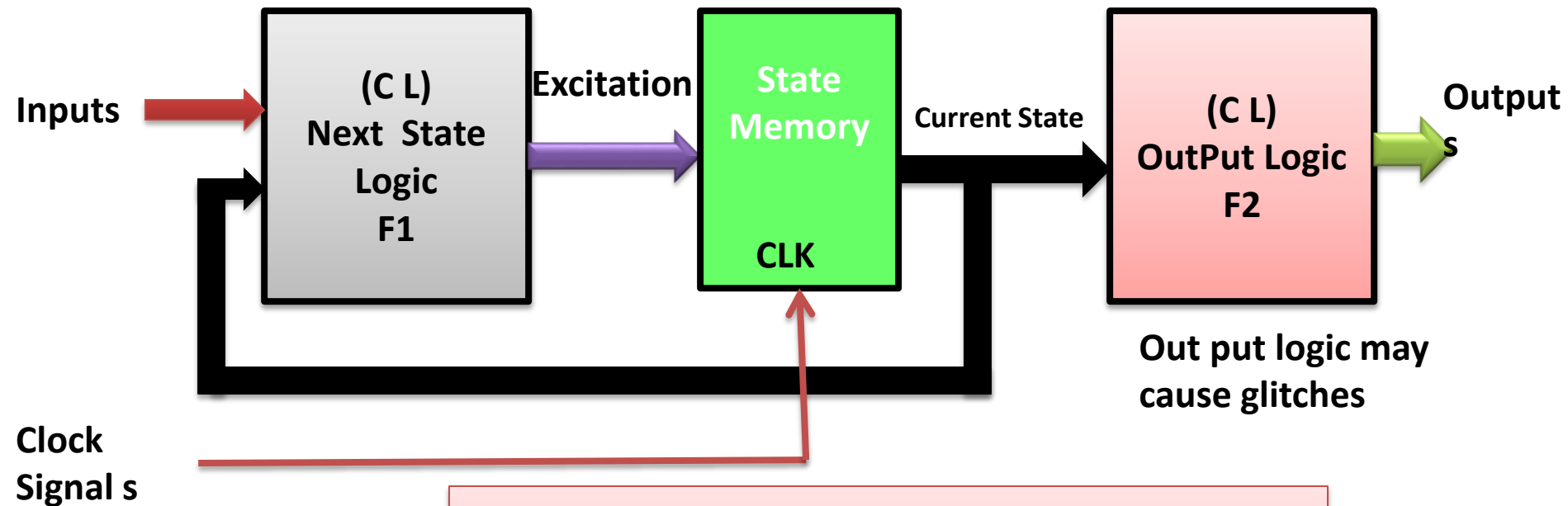



Out put logic may cause glitches

Next state = $F_2(\text{current state, inputs})$
Output = $G_2(\text{current state})$

Finite State Machine: Example

- Example: Make x change toggle (0 to 1, or 1 to 0) every clock cycle
- Two states: “Off” ($x=0$), and “On” ($x=1$)
- Transition from Off to On, or On to Off, on rising clock edge
- Arrow with no starting state points to initial state (when circuit first starts)

Finite State Machine: Example

 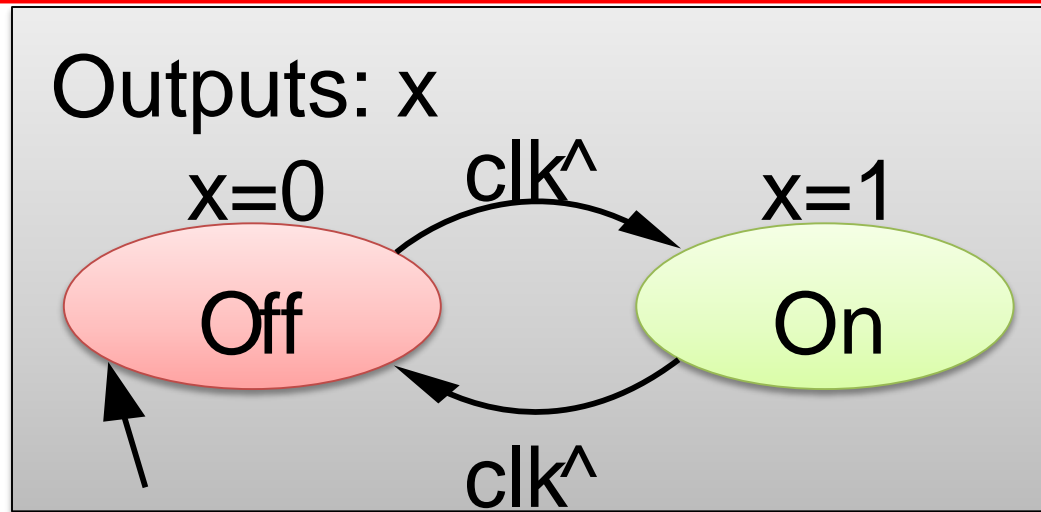


FSM

We often draw FSM graphically, known as *state diagram*

Can also use table (state table), or textual languages

Controller for On-Off



Input		Output	
CLK	P	X	N
RE 1	0	1	1
RE 1	1	0	0

 

Think of Clock Enable: only **Rising Edge (RE)**
Above one may not work: Level Sensitive

Controller for On-Off

Input		Output	
CLK	P	X	N
RE 1	0	1	1
RE 1	1	0	0

 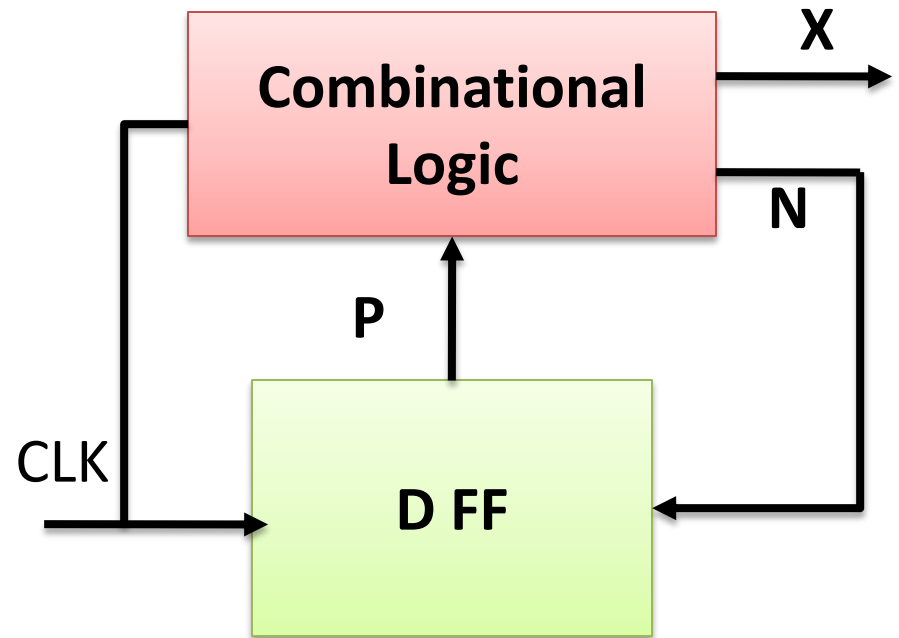

Rising Edge: Clock implicit

FSM for D-FF


PS= Q(t)	Input	NS =Q(t+1)
0	0	0
0	1	1
1	0	0
1	1	1

$$Q(t+1)=Q(t)$$

State: 0, 1

Input : 0, 1

Output: 0,1

 

FSM Controller for D-FF is D-FF


PS= Q(t)	Input	NS =Q(t+1)
0	0	0
0	1	1
1	0	0
1	1	1

$$Q(t+1)=Q(t)$$

State: 0, 1

Input : 0, 1

Output: 0,1

 

FSM for T-FF


PS= Q(t)	Input	NS =Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

$$Q(t+1)=Q(t)T(t)+Q(t)T(t)$$

State: 0, 1

Input : 0, 1

Output: 0,1

 

FSM Controller for T-FF


PS= Q(t)	Input	NS =Q(t+1)
0	0	0
0	1	1
1	0	0
1	1	1

$$Q(t+1)=Q(t)$$

State: 0, 1

Input : 0, 1

Output: 0,1

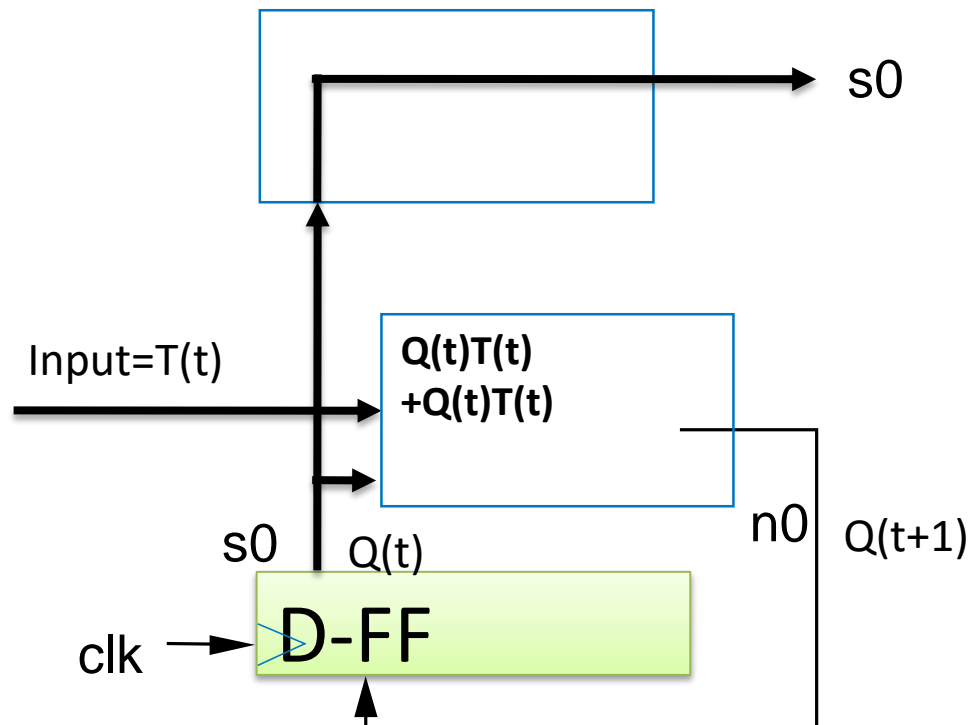


FSM for JK-FF

State: 0, 1

Input : 00, 01,10,11

Output: 0,1

 

FSM for JK-FF

State: 0, 1

Input : 00, 01, 10, 11

Output: 0, 1

PS= Q(t)	Input(JK)	NS =Q(t+1)
0	00	0
0	01	0
0	10	1
0	11	1
1	00	1
1	01	0
1	10	1
1	11	0

$$Q(t+1) = JQ'(t) + K'Q(t)$$


FSM Controller for JK-FF

State: 0, 1

Input : 00, 01, 10, 11

Output: 0, 1

$$Q(t+1) = JQ'(t) + K'Q(t)$$

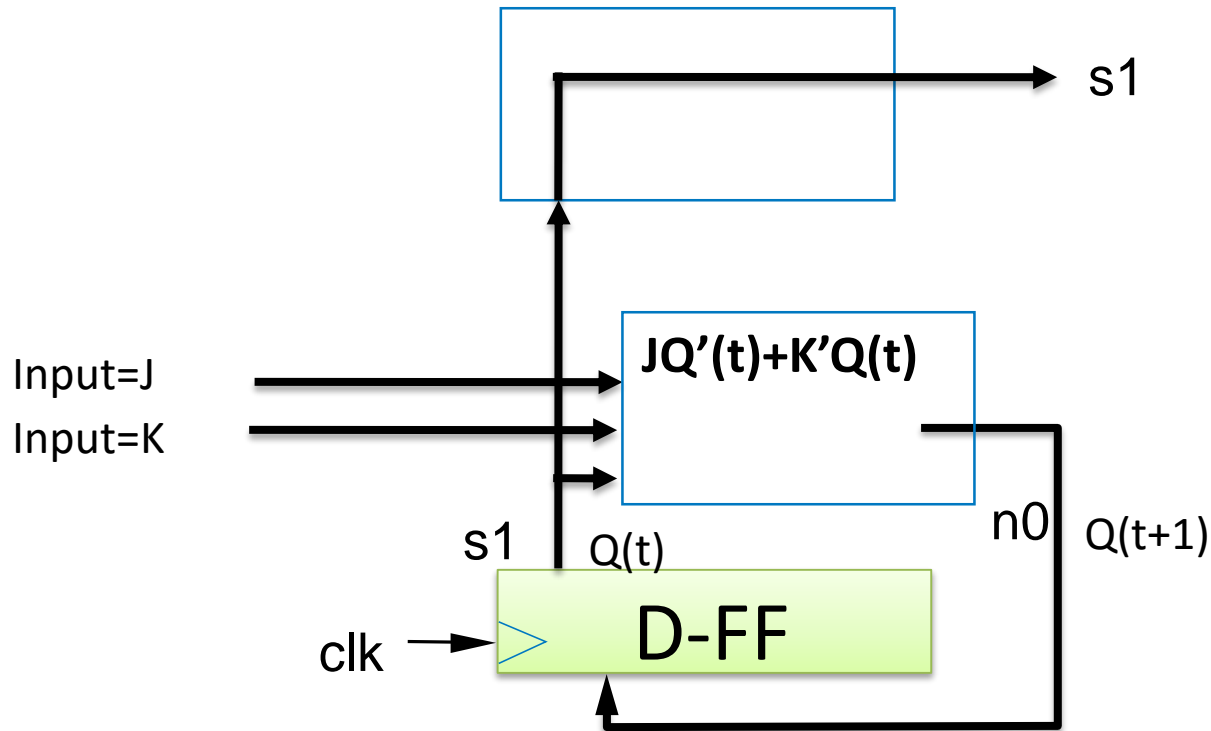

FSM for RS-FF

State: 0, 1

Input : 00, 01, 10, 11


Output: 0, 1

PS= Q(t)	Input(RS)	NS =Q(t+1)
0	00	0
0	01	0
0	10	1
0	11	x
1	00	1
1	01	0
1	10	1
1	11	x

$$Q(t+1) = R + Q(t).S'$$


FSM Example: 0,1,1,1,repeat

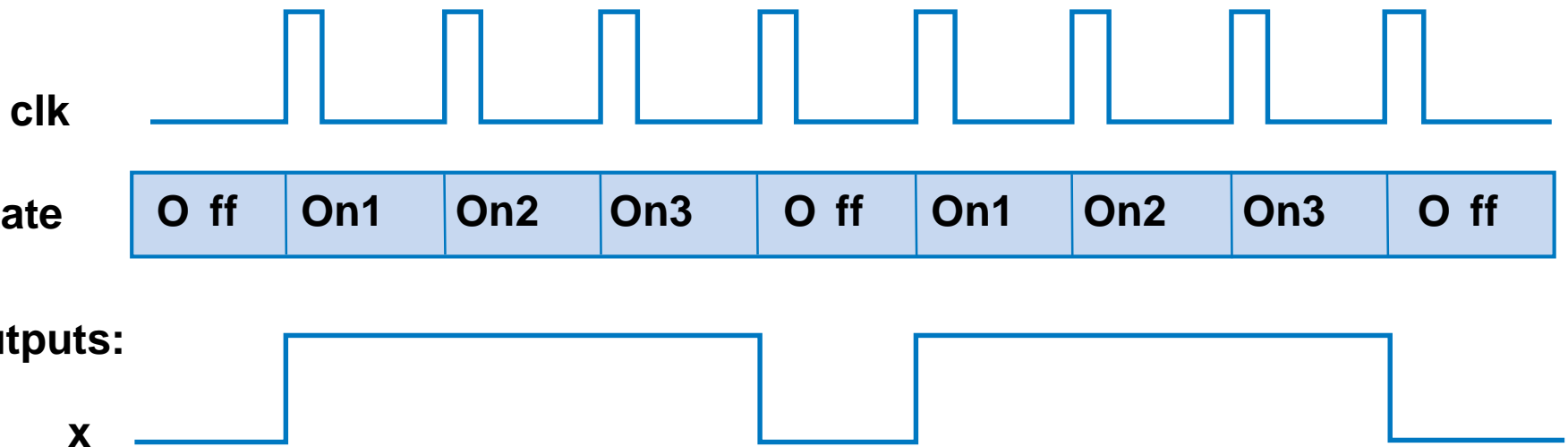- Want 0, 1, 1, 1, 0, 1, 1, 1, ...
 - Each value for one clock cycle
- Can describe as FSM: Four states, Transition on rising clock edge to next state



FSM Example: 0,1,1,1,repeat

 
- Want 0, 1, 1, 1, 0, 1, 1, 1, ...
 - Each value for one clock cycle
- Can describe as FSM: Four states, Transition on rising clock edge to next state




Extend FSM to Three-Cycles High Laser Timer

- Four states: Wait in “Off” state while b is 0 (b')
- When $b=1$ (& rising clock edge), transition to On1
 - Sets $X=1$
 - On next two clock edges, transition to On2, then On3, which also set $x=1$
- So $x=1$ for three cycles after button pressed

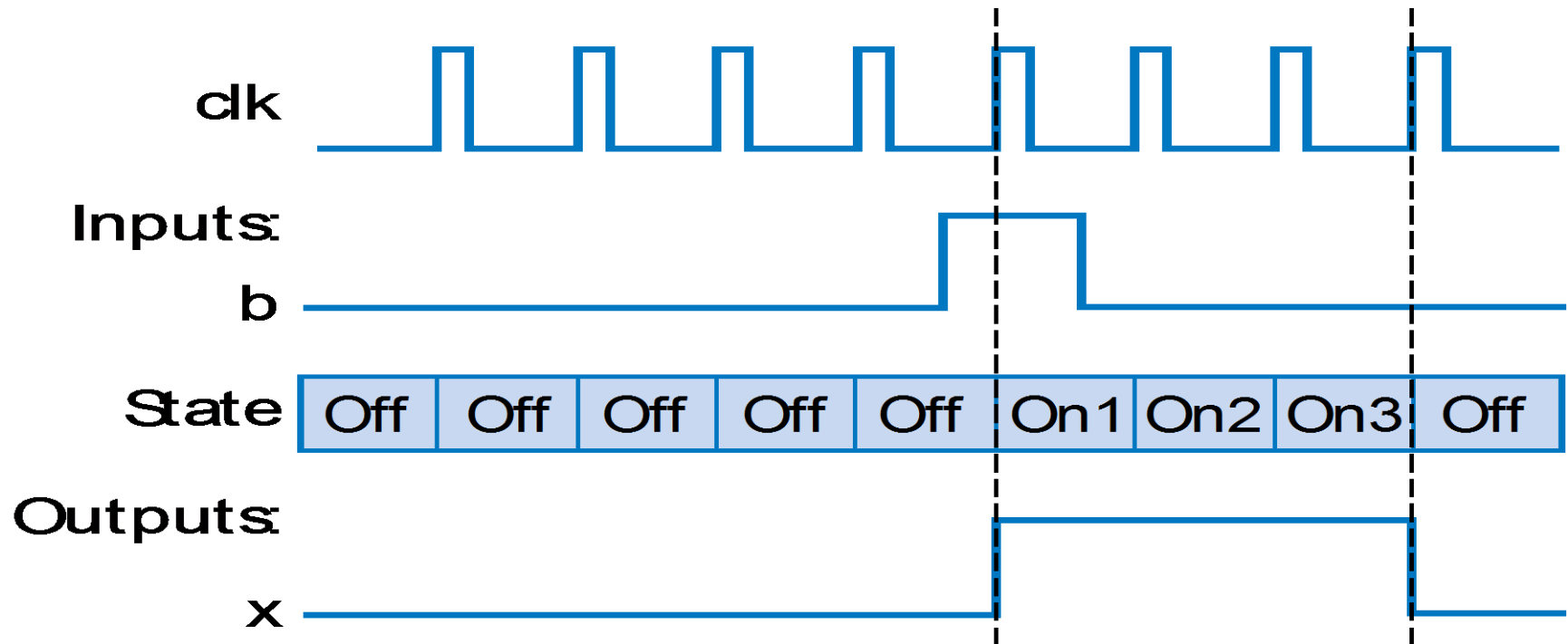Extend FSM to Three-Cycles High Laser Timer



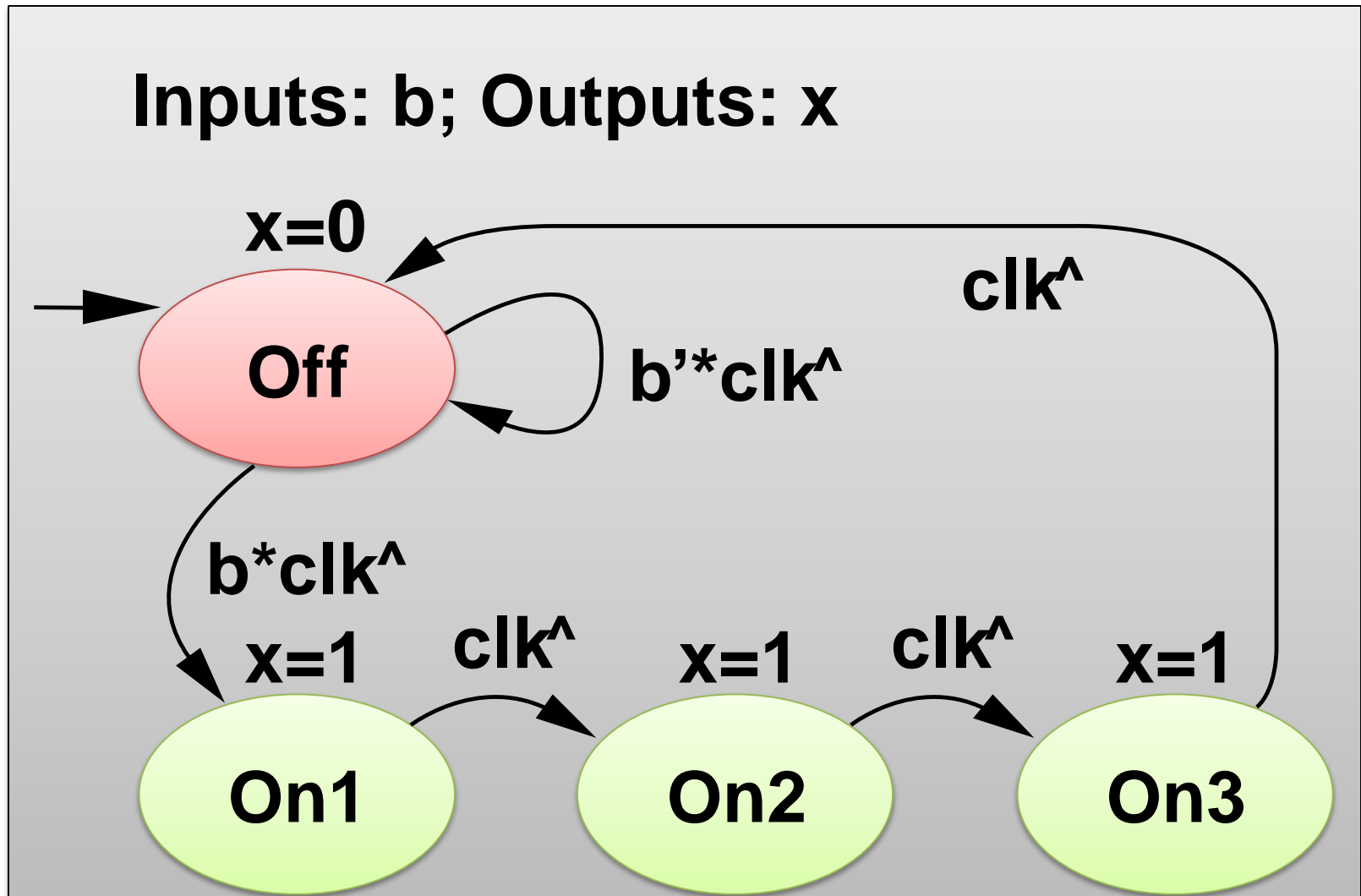Extend FSM to Three-Cycles High Laser Timer




FSM Simplification: Rising Clock Edges Implicit

- Showing rising clock on every transition: cluttered
- Make implicit -- assume every edge has rising clock
- What if we wanted a transition *without* a rising edge
 - Asynchronous FSMs -- less common, and advanced topic
 - We consider *synchronous* FSMs
 - **All transition on rising edge**

FSM Simplification: Rising Clock Edges Implicit


Inputs: b ; Outputs: x

 

Note: Transition with no associated condition thus transistions to next state on next clock cycle

FSM Simplification: Rising Clock Edges Implicit


Inputs: b ; Outputs: x

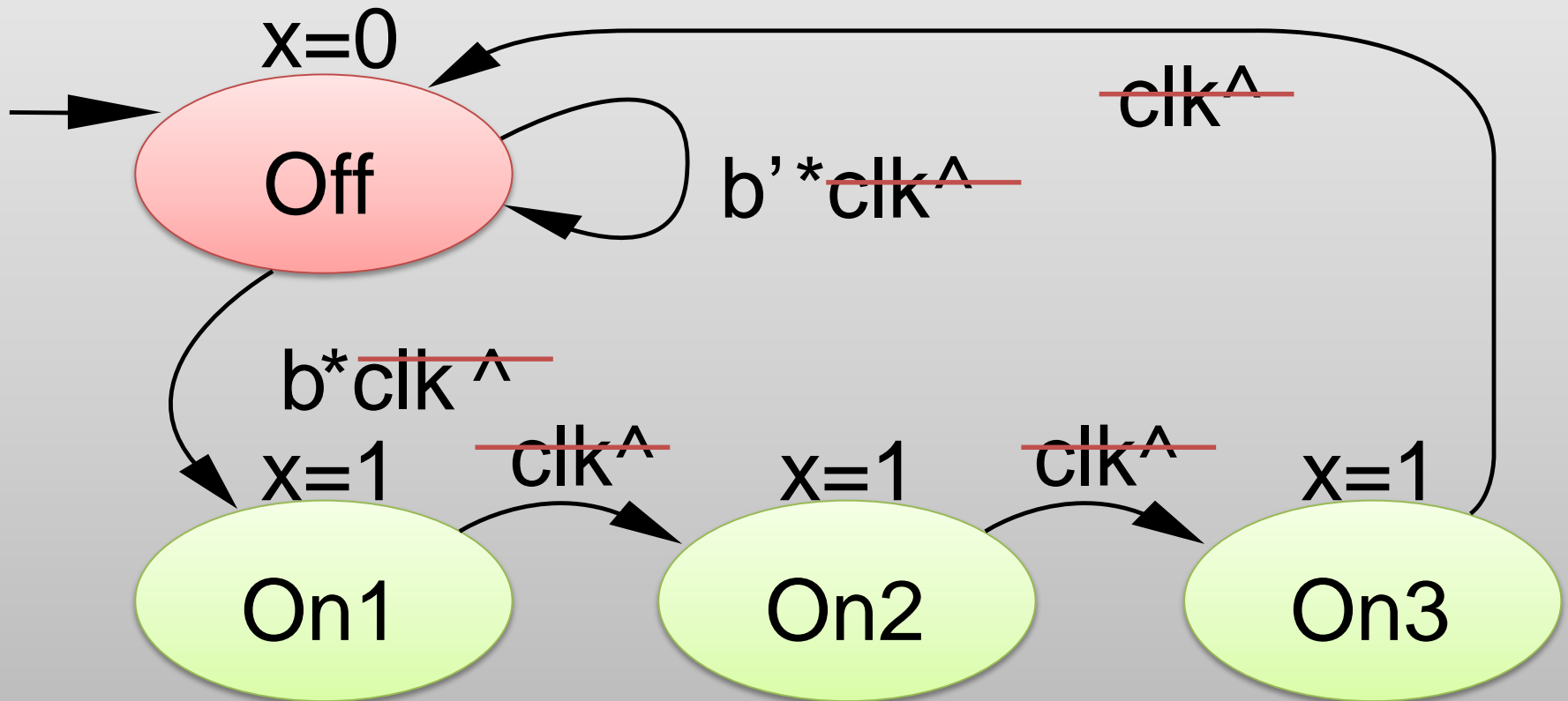

Note: Transition with no associated condition thus transistions to next state on next clock cycle

FSM Simplification: Rising Clock Edges Implicit

Inputs: b ; Outputs: x

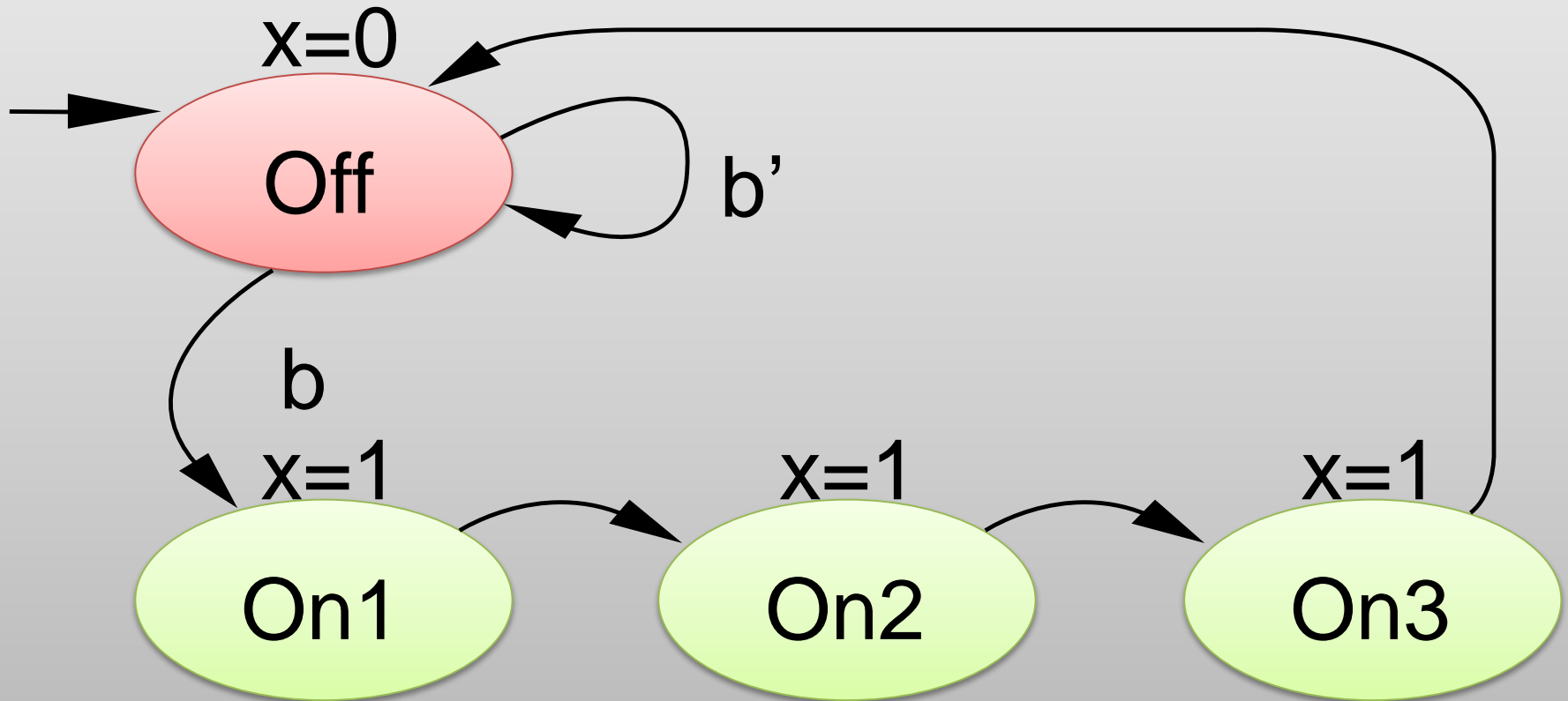

Note: Transition with no associated condition thus transistions to next state on next clock cycle