

**CS221: Digital Design**

# **Sequential Logic Design (Latch & FF)**

A. Sahu

Dept of Comp. Sc. & Engg.


Indian Institute of Technology Guwahati

# Outline

- Combinational Vs Sequential Logic Design
- Design a **flip-flop**, that stores one bit
  - RS latch
- Stabilizing RS latch : Level Sensitive
- Clocked Latch : Flip Flop- Edge Sensitive
- D, JK, T flip flops
- Characterization Table and Equation
  - RS, D, JK and T Flip flop
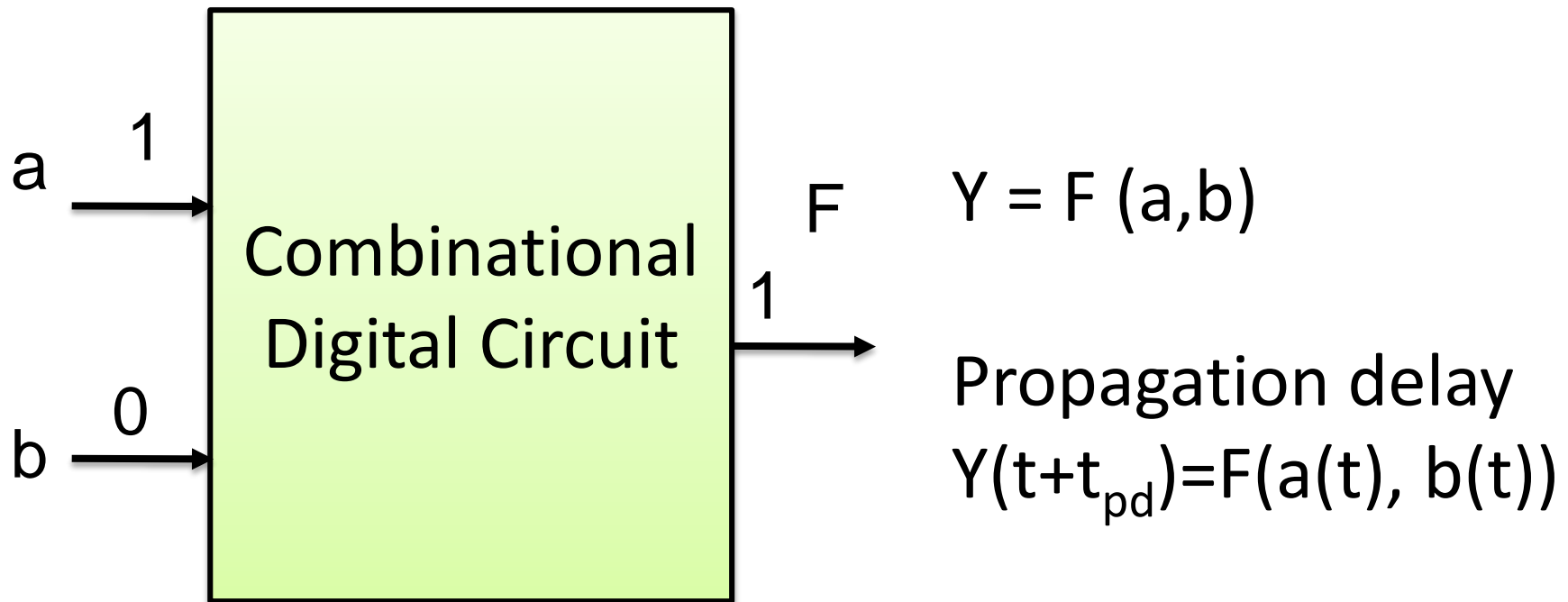
# Combinational Vs Sequential Logic

- Combinational circuit
  - **Output depends on present input**
  - Examples: F (A,B,C), FA, HA, Multiplier, Decoder, Multiplexor, Adder, Priority Encoder




# Combinational Vs Sequential Logic

- Sequential circuit
  - Output depends not just on present inputs
  - But also on past sequence of inputs (State)
    - Stores bits, also known as having “state”
 
# Combinational Vs Sequential Logic

- Simple example: a circuit that counts up in binary




*Must know sequence of past inputs to know output*

$$Y(t) = F(a(t), b(t), H)$$

**H is History/Sequence/State**

# Sequential Circuit

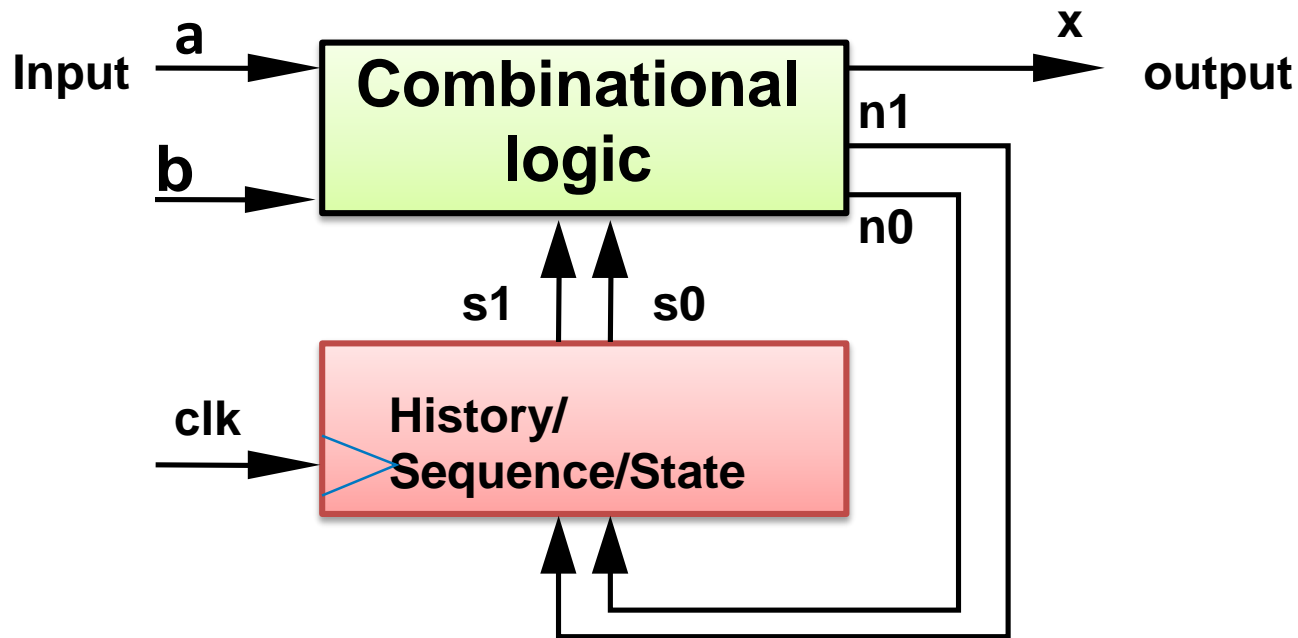

$$Y(t) = F(a(t), b(t), H)$$

H is History/Sequence/State

Where to  
Store this  
History

(Memory  
Element)


# Example Needing Bit Storage

- Example: Flight attendant call button
  - Press call: light turns on
    - ***Stays on*** after button released
  - Press cancel: light turns off




How to design a  
circuit for this ?


# Example Needing Bit Storage

 

 *1. Call button pressed – light turns on*



 *2. Call button released – light stays on*



*3. Cancel button pressed – light turns off*



# Example Needing Bit Storage


- Flight attendant call button
  - Press call: light turns on
    - ***Stays on*** after button released
  - Press cancel: light turns off



How to design a  
circuit for this ?
 
# Example Needing Bit Storage

- Flight attendant call button
  - Press call: light turns on : ***Stays on*** after button released
  - Press cancel: light turns off
- Logic gate circuit to implement this?




Doesn't work.  $Q=1$  when  $\text{Call}=1$ , but doesn't stay 1 when Call returns to 0

*Need some form of “feedback” in the circuit*

 
## First attempt at Bit Storage

- We need some sort of feedback
  - Does circuit this circuit do what we want?



- No: Once **Q** becomes 1 (when **S**=1), **Q** stays 1 forever – no value of **S** can bring **Q** back to 0


# First attempt at Bit Storage

 

Once  $Q$  becomes 1 (when  $S=1$ ),  $Q$  stays 1 forever – no value of  $S$  can bring  $Q$  back to 0


 
# Bit Storage Using an SR Latch

- With cross-coupled NOR gates
  - Does the circuit to the right ?
  - Do what we want?




- Yes! How did someone come up with that circuit?
  - Maybe just trial and error, a bit of insight...

# Bit Storage Using an SR Latch

  

# Function Table of SR Latch


 


S	R	Q	Q'	
1	0	1	0	
0	0	1	0	After S=1, R=0
0	1	0	1	
0	0	0	1	After S=0, R=1
1	1	0	0	Forbidden

*Set : make out put 1*

*Reset : make out put 0*


# Example Using SR Latch for Bit Storage

  

- SR latch can serve as bit storage of flight-attendant call button : 😊 😊 😊 Great
  - Call=1 : sets Q to 1
    - Q stays 1 even after Call=0
  - Cancel=1 : resets Q to 0
- **But, there's a problem...**



# SR Latch with NAND Gates

 


S	R	Q+
0	0	1*0* (Unpredictable)
0	1	1
1	0	0
1	1	Q

Opposite to SR Latch with NOR Gates

Set will do  $Q=0$  and Reset will  $Q=1$

# Problem with SR Latch: SR=11




 
- Problem
  - If  $S=1$  and  $R=1$  simultaneously, we don't know what value  $Q$  will take (Unpredictable)




**Race Condition :-**

**Who will win 0 or 1?  
Eventually, what will be the  
value of  $Q$ ?**

# Problem with SR Latch

    


 Q may oscillate. Then, because one path will be slightly longer than the other, Q will eventually settle to 1 or 0 – but we don't know which.


 
# Solution to Race Condition

- We try to avoid  $S=1$  and  $R=1$  by the following circuit




- Can we ensure value  $S=1$  and  $R=1$  will not happen at the same time?

# Problem with SR Latch


- Problem not just one of a user pressing two buttons at same time
- Can also occur even if SR inputs come from a circuit that supposedly never sets  $S=1$  and  $R=1$  at same time
  - But does, due to different delays of different paths

# Problem with SR Latch

- $X=1$  and  $Y=1$  set

 



Yesterday it was  
my mistake

 

The longer path from X to R than to S causes  $SR=11$  for short time – could be long enough to cause oscillation

 
 
# Solution: Level-Sensitive SR Latch

- Add enable input “C or En”
  - Only let S and R change when  $C = 0$  : Ensure circuit in front of SR never sets  $SR = 11$ , except briefly due to path delays
  - Change C to 1 only after sufficient time for S and R to be stable
  - When C becomes 1, the stable S and R value passes through the two AND gates to the SR latch’s S1 R1 inputs.



**Level-sensitive SR latch symbol**

 
 
# Level Sensitive: SR Latch with NAND Gate




Level-sensitive SR  
latch symbol


 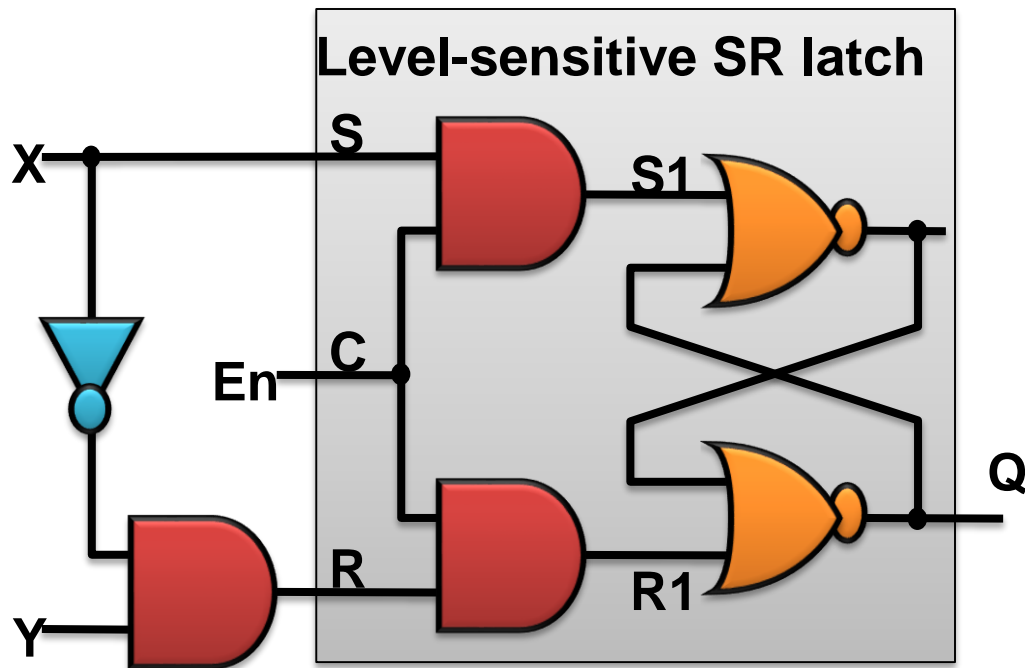
# Ensure $S=1$ and $R=1$ should not happened to Level-Sensitive SR Latch



# Solution: Ensure, Stabilize, Store

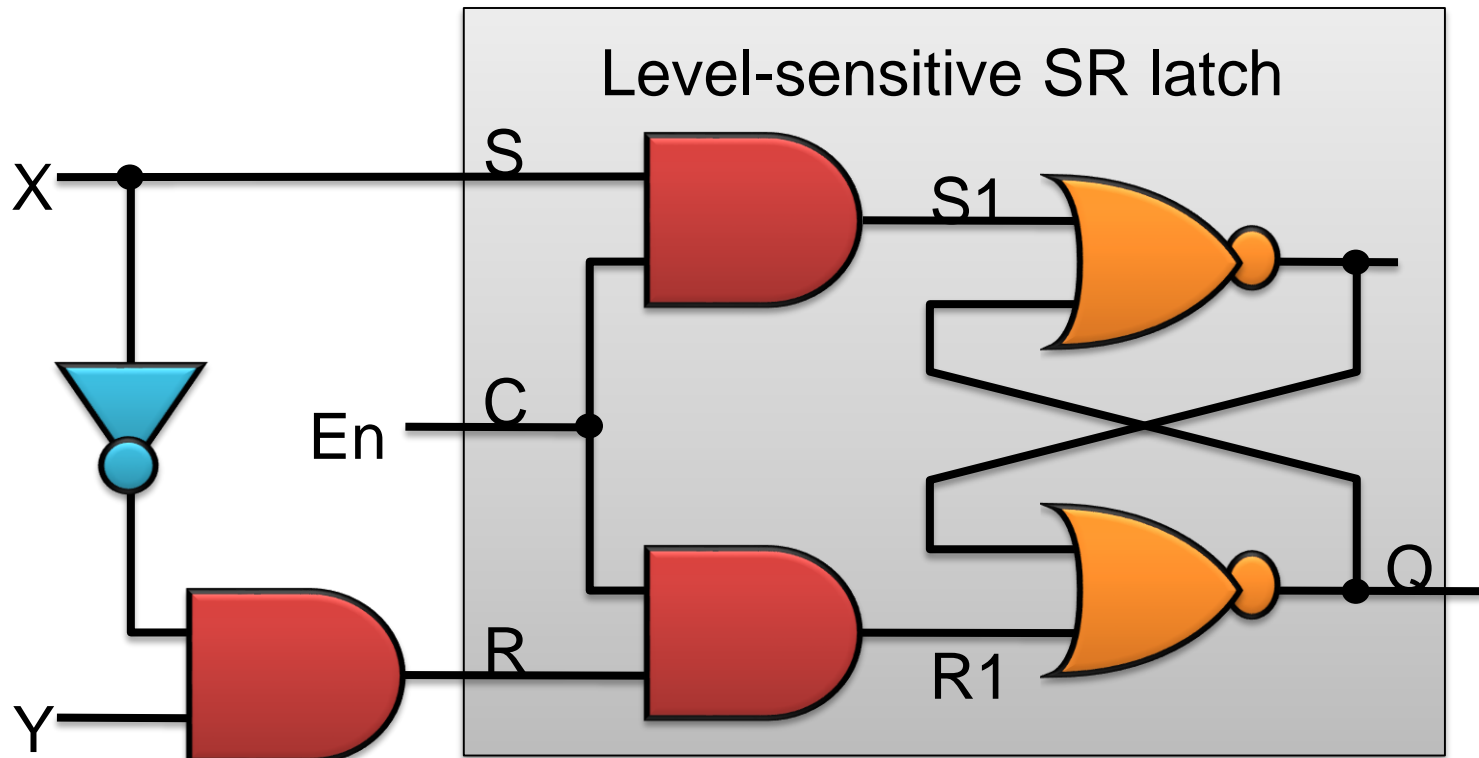

Ensure  
Stage

Never Happens  
SR=11

Stabilize  
Stage

When C=0  
Stabilize SR and  
Use when C=1

Store  
Stage

Store bit

**Thanks**