

**CS221: Digital Design**

# **Sequential Logic Design (Latch & FF)**

A. Sahu


Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

# Outline

- Combinational Vs Sequential Logic Design
- Design a **flip-flop**, that stores one bit
  - RS latch
- Stabilizing RS latch : Level Sensitive
- Clocked Latch : Flip Flop- Edge Sensitive
- D, JK, T flip flops
- Characterization Table and Equation
  - RS, D, JK and T Flip flop

# Solution: Ensure, Stabilize, Store

 

Ensure  
Stage

Never Happens  
SR=11


Stabilize  
Stage

When C=0  
Stabilize SR and  
Use when C=1

Store  
Stage

Store bit

# Clocks


 


- ***Clock period***: time interval between pulses
- ***Clock cycle***: one such time interval
- ***Clock frequency***:  $1/\text{period}$ 
  - frequency =  $1 / 20 \text{ ns} = 50 \text{ MHz}$

- $1 \text{ Hz} = 1/\text{s}$


Freq	Period
1 GHz	1 ns
100 MHz	10 ns
10 MHz	100 ns

# Clock Signal for RS latch

  



 
# Clock Signals for a RS Latch

- How do we know when it's safe to set  $C=1$ ?
  - Most common solution – make  $C$  pulse up/down
  - $C=0$ : Safe to change  $X, Y$      $C=1$ : Must *not* change  $X, Y$
  - **Clock** signal -- Pulsing signal used to enable latches
    - Because it ticks like a clock
  - Sequential circuit whose storage components all use clock signals: **synchronous** circuit


   
# Level-Sensitive D Latch


- SR latch requires careful design to ensure  $SR=11$  never occurs
- D latch relieves designer of that burden
  - Inserted inverter ensures R always opposite of S



D latch symbol
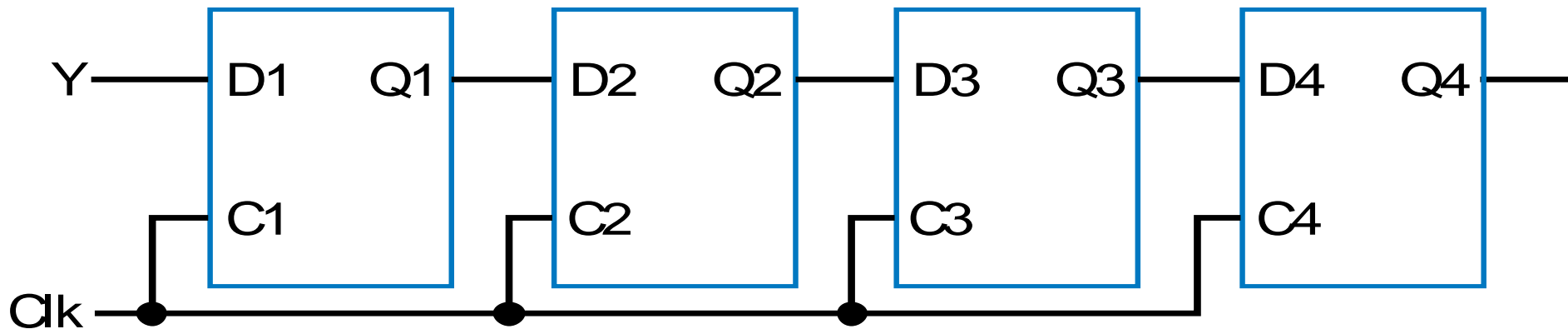
# Level-Sensitive D Latches

- Suppose D FFs are arranged in linear fashion connected using a single clock signal Clk
- Every clock we want to shift one bit to right
  - Right shift one bit per cycle




**Does this circuit (with level sensitive D latch)  
Shift one bit per cycle ?**



 
# Problem with Level-Sensitive D Latch

- D latch still has problem (as does SR latch)
  - When  $C=1$ , through how many latches will a signal travel?
  - Depends on for how long  $C=1$ 
    - Clk\_A -- signal may travel through multiple latches
    - Clk\_B -- signal may travel through fewer latches
  - **Hard to pick C that is just the right length**


 
## Problem with Level-Sensitive D Latch


- We want do the work: one per clock cycle
  - Independent of length of clock (1 time)




Is there any solution to  
this ?
 
# Problem with Level-Sensitive D Latch

- We want do the work: one per clock cycle
  - Independent of length of clock (1 time)



 - Can we design bit storage that only stores a value on the rising edge of a clock signal?
  - There is exactly one rising edge per clock cycle
  - There is exactly one falling edge per clock cycle



# Make Edge Sensitive Bit Storage

- Latch : Level sensitive storage
- Flip-Flop : Edge sensitive storage
  - Value get changed only at edges of clock




How to make a  
Flip Flop out of  
Latch?

# Master -Slave D Flip-Flop

- **Two latches**, output of first goes to input of second, master latch has inverted clock signal
- So master loaded when  $C=0$ , then servant when  $C=1$
- When  $C$  changes from 0 to 1, master disabled, servant loaded with value that was at  $D$  just before  $C$  changed
  - i.e., Value at  $D$  during rising edge of  $C$
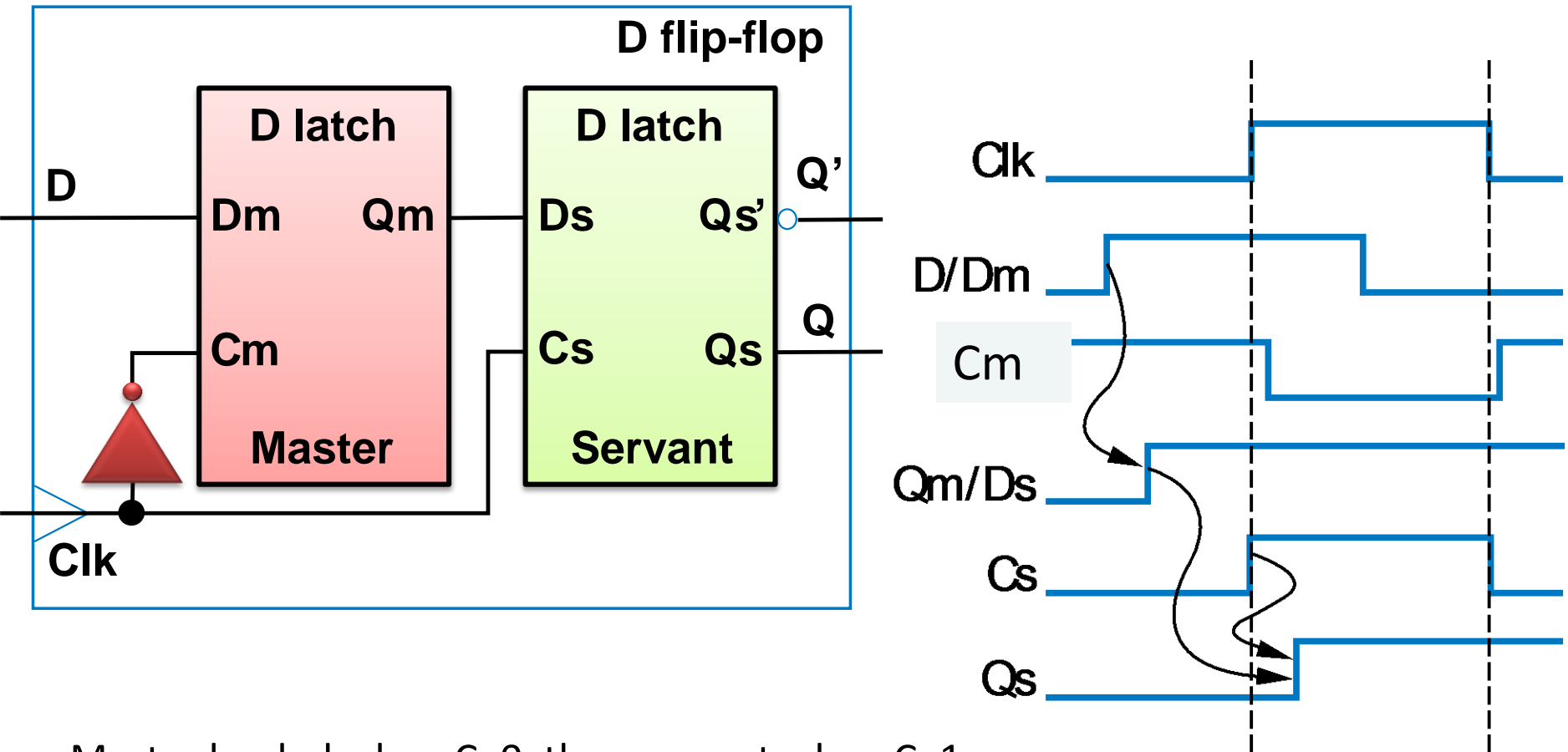
# Master -Slave D Flip-Flop



- ***Flip-flop***: stores on clock edge, not level




Master loaded when C=0, then servant when C=1

When C changes from 0 to 1, master disabled, servant loaded with value that was at D just before C changed -- i.e., value at D during rising edge of C


# D Flip-Flop ( Rising & Falling Edges)

  

Rising edges

 


Falling edges

 
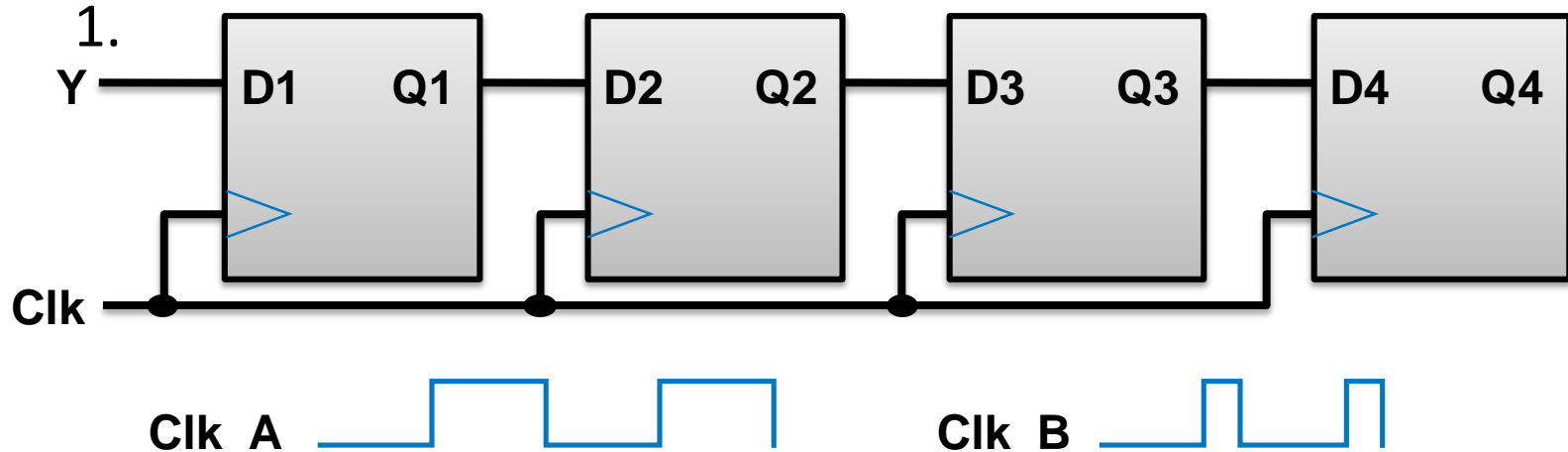
# D Flip-Flops

- Solves problem of not knowing through how many latches a signal travels when  $C=1$ 
  - Signal travels through exactly one FF, for Clk\_A or Clk\_B. **Why?**
  - Because on rising edge of Clk, all four flip-flops are loaded simultaneously -- then all four no longer pay attention to their input, until the next rising edge. Doesn't matter how long Clk is




***Two latches inside each flip-flop***



# D Latch vs. D Flip-Flop


- Latch is level-sensitive: Stores D when C=1
- Flip-flop is edge triggered: Stores D when C changes from 0 to 1
  - Saying “level-sensitive latch,” or “edge-triggered flip-flop,” is redundant
  - Two types of flip-flops -- rising or falling edge triggered.
 
# Positive Edge Triggered D-Flip Flop: Optimization



**GATE COUNT: 10**  
**4 NOR, 4 AND**  
**and 2 NOT**

# Remember: SR Latch with NAND Gates

 


S	R	Q+
0	0	1*0* (Unpredictable)
0	1	1
1	0	0
1	1	Q

Opposite to SR Latch with NOR Gates


Set will do  $Q=0$  and Reset will  $Q=1$
 
# Positive-Edge Triggered D-FF: Economical



 
# Positive-Edge Triggered D-FF: Economical

- When  $\text{CLK}=0$ ,  $S'R'=11$ ,  $Q^+=Q$  (Independent of D)



 
# Positive-Edge Triggered D-FF: Economical

- When  $\text{CLK}=1$ ,  $D=0$ ,  $Q^+=0$



 
# Positive-Edge Triggered D-FF: Economical

- After that When CLK=1, D=1: No changes to R'S':  
 $Q^+=0$  It locked


 
# Positive-Edge Triggered D-FF: Economical



**GATE COUNT: 6**  
**6 NAND, Same types**




**Transistor level optimization  
is  
out of syllabus**

**But showing two slides 😊 😊 😊**


# Master-Slave Edge-Triggered Flip-Flop

**2 x 8 = 16 Transistors**

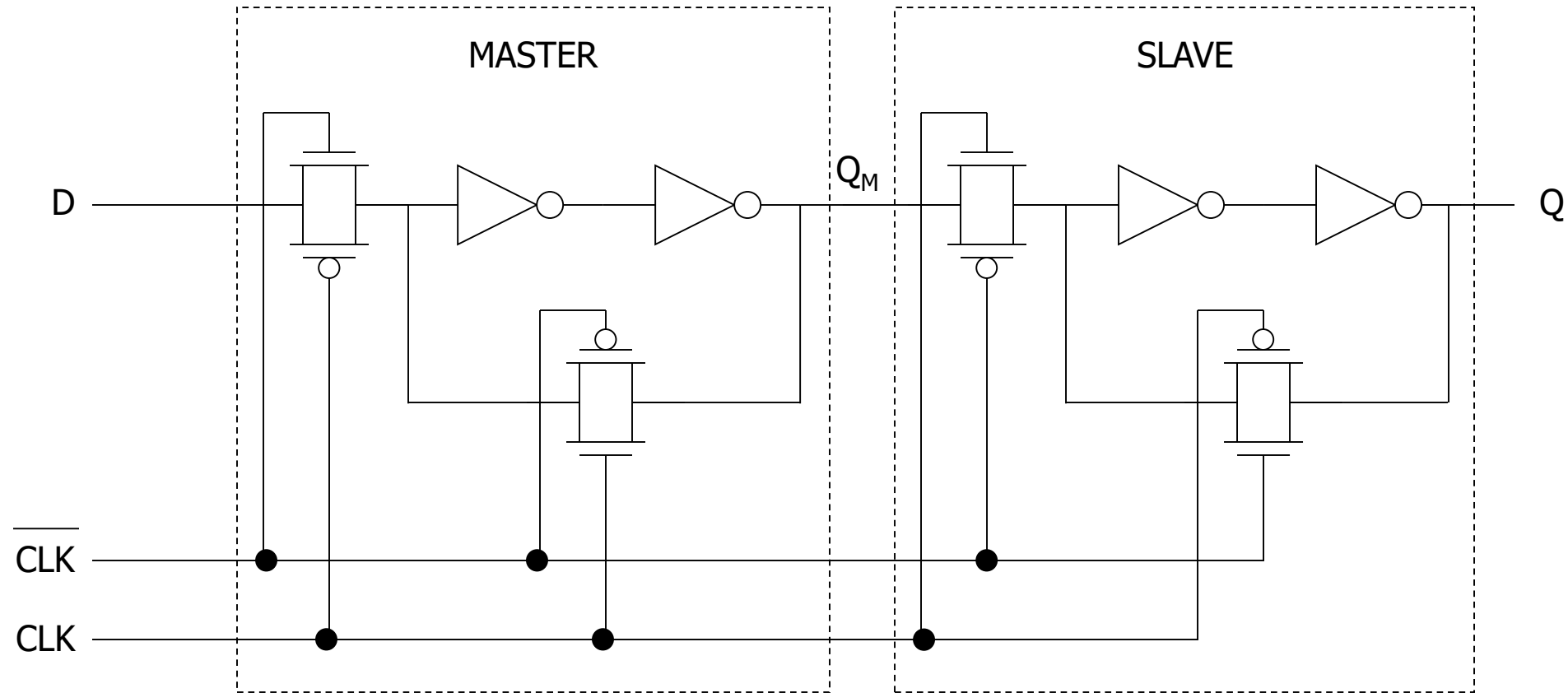
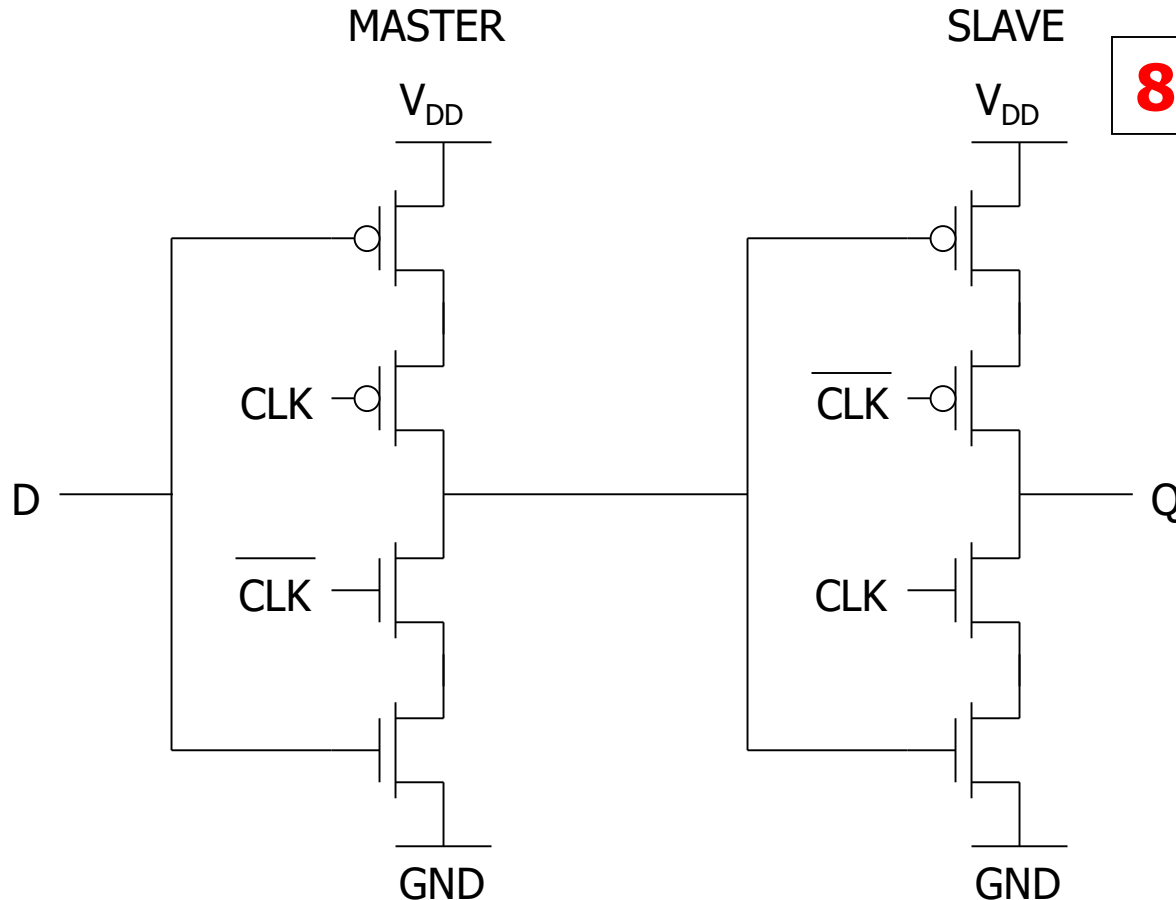
# More Efficient Master-Slave Edge-Triggered Flip-Flop

- Called a C<sup>2</sup>MOS (Clocked CMOS) design




**8 Transistors**

# Problem handled in Designing FF

- OR Gate : worked just like a ringing bell
- OR gate with Feed back : ( $Q=1$  can never be changed)
- Two NOR gates with cross coupled out put and input : Solved to store a bit but Race condition
- Ensure  $RS=11$  will not happed by adding Not and AND gate
- Enable Signal to put remove : delay of added Ckt
- Master Slave Latches to make a FF
- Optimized D-FF (using only NAND Gates)
 
# Conventions

- The circuit is *set* means output = 1
- The circuit is *reset* means output = 0
- Flip-flops have two output Q and Q'
- Due to time related characteristic of the flip-flop:
  - $Q_t$  or Q: present state
  - $Q_{t+1}$  or  $Q^+$ : next state




## 4 Type of Flip Flop

- **SR Flip Flop** : Set/Reset Flip Flop
- **D Flip Flop** : Data Flip Flop to store Bit
- **J-K Flip Flop**: Unavoidable SR=11 state to Toggle (All input values are useful)
  - The JK Flip Flop was named to honour "**Jack Kilby**" of Texas Instrument engineer who invented the concept of IC.
- **T Flip Flop**: Toggle Flip Flop
 
# J-K Latches


- The JK flip-flop augments the behavior of the SR flip-flop (J=Set, K=Reset) by interpreting the  $S = R = 1$  condition as a "flip" or toggle command.



J	K	Q+
0	0	Qt
0	1	0
1	0	1
1	1	Qt'

$$Q^+ = K'Q + JQ'$$


# Master Slave J-K Flip Flop

 

$$Q^+ = K'Q + JQ'$$



# Master Slave J-K Flip Flop

 

$$Q^{+} = K'Q + JQ'$$

# J-K Flip Flop

- To synthesize a D flip-flop, simply set K equal to the complement of J.
- The JK flip-flop is a universal flip-flop
  - Because it can be configured to work as any FF
  - T flip-flop or D flip-flop or SR flip-flop.



J=T	K=T	Q+
0	0	Q <sub>t</sub>
0	1	0
1	0	1
1	1	Q <sub>t</sub> '

J=D	K=D'	Q+
0	0	Q <sub>t</sub>
0	1	0
1	0	1
1	1	Q <sub>t</sub> '

J=S	K=R	Q+
0	0	Q <sub>t</sub>
0	1	0
1	0	1
1	1	Q <sub>t</sub> '

# Toggle Flip-Flop: T FF

- $J=K=1$ ,  $Q^+ = Q'$

  

# 4 Types of Flip-Flops

S	R	Q+
0	0	$Q_t$
0	1	0
1	0	1
1	1	U




D	Q+
0	0
1	1

J	K	Q+
0	0	$Q_t$
0	1	0
1	0	1
1	1	$Q_t'$



T	Q+
0	$Q_t$
1	$Q_t'$


# Given a D FF: Construct JK FF

 

$$D = K'Q + JQ'$$

J	K	D	$K'Q + JQ'$
0	0	Q	$1Q + 0Q'$
0	1	0	$0Q + 0Q'$
1	0	1	$1Q + 1Q'$
1	1	Q'	$0Q + 1Q'$

# Given a D FF: Construct T FF

 

T	D	$TQ' + T'Q$
0	Q	$0Q' + 1Q$
1	Q'	$1Q' + 0Q$

$$D = TQ' + TQ$$

# Characteristic Equations

- A descriptions of the next-state table of a flip-flop
- Constructing from the Karnaugh map for  $Q_{t+1}$  in terms of the present state and input

# Characteristic tables

- The tables that we've made so far are called **characteristic tables**.
  - They show the next state  $Q(t+1)$  in terms of the current state  $Q(t)$  and the inputs.
  - For simplicity, the control input  $C$  is not usually listed.
  - Again, these tables don't indicate the positive edge-triggered behavior of the flip-flops that we'll be using.

J	K	Q+
0	0	$Q_t$
0	1	0
1	0	1
1	1	$Q_t'$

D	Q+
0	0
1	1

T	Q+
0	$Q_t$
1	$Q_t'$



# Characteristic equations

- We can also write **characteristic equations**, where the next state  $Q(t+1)$  is defined in terms of the current state  $Q(t)$  and inputs.

J	K	Q+
0	0	Q <sub>t</sub>
0	1	0
1	0	1
1	1	Q <sub>t</sub> '

$$\begin{aligned}Q^+ &= J'K'Q + JKQ_t' + JK' \\&= J'K'Q + JKQ' + JK'Q' + JK'Q \\&= J'K'Q + JK'Q + JKQ' + JK'Q' \\&= (J+J')K'Q + J(K+K')Q'\end{aligned}$$

$$Q^+ = K'Q + JQ'$$

$$Q(t+1) = K'Q(t) + JQ'(t)$$

# Characteristic equations

- We can also write **characteristic equations**, where the next state  $Q(t+1)$  is defined in terms of the current state  $Q(t)$  and inputs.

D	Q+
0	0
1	1

$$Q^+ = D$$

$$Q(t+1) = D$$

T	Q+
0	$Q_t$
1	$Q_t'$

$$Q^+ = T'Q + TQ' = T \oplus Q$$

$$Q(t+1) = T'Q(t) + TQ'(t) = T \oplus Q(t)$$

# Characteristic equations

	SR			
	00	01	11	10
0	0	0	-	1
1	1	0	-	1

$$Q^+ = S + R'Q \quad (SR=0)$$

Flip Flop Type	Characteristic Equation
SR	$Q^+ = S + R'Q \quad (SR=0)$
JK	$Q^+ = JQ' + K'Q$
D	$Q^+ = D$
T	$Q^+ = TQ' + T'Q = T \oplus Q$

# FF with Asynchronous Inputs


- S-R, D and J-K inputs are synchronous inputs
  - As data on these inputs are transferred to the flip-flop's output
  - Only on the triggered edge of the clock pulse.
- **Asynchronous** inputs affect the state of the flip-flop independent of the clock
- Example:
  - *Preset (PRE) and clear (CLR)*
  - or *direct set (SD) and direct reset (RD)*

# FF with Asynchronous Inputs

- When  $PRE=HIGH$ ,  $Q$  is immediately set to HIGH.
- When  $CLR=HIGH$ ,  $Q$  is immediately cleared to LOW.
- Flip-flop in normal operation mode when both  $PRE$  and  $CLR$  are LOW.
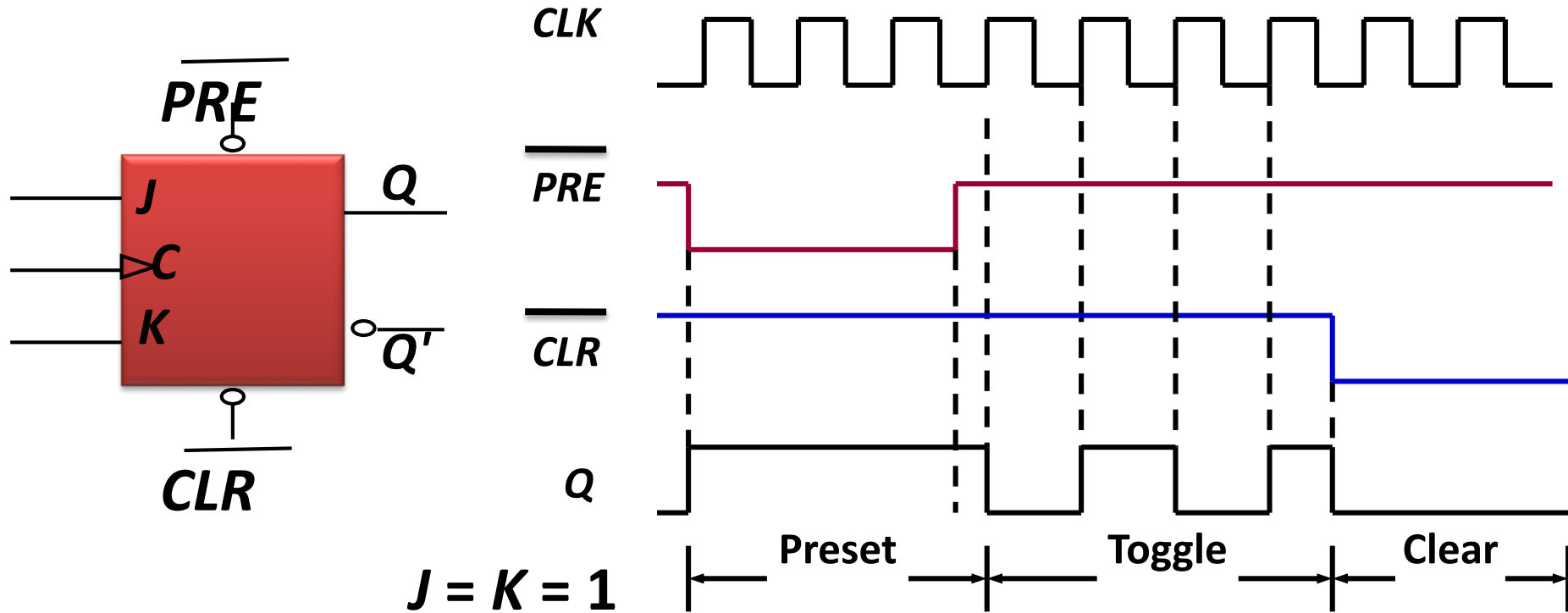
# Asynchronous Inputs

- A J-K flip-flop with active-LOW preset and clear inputs.



**Thanks**