

CS221: Digital Design

<http://jatinga.iitg.ernet.in/~asahu/cs221>

FSMD and ASM

A. Sahu

Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

ASM Overview

- Drawbacks of state diagrams for real systems:
 - Many inputs & many outputs -> awkward to list all of these as each transition arc.
 - On any given arc
 - Typically most inputs are don't care
 - Typically most outputs are unchanged from the settings in the previous state
 - Tedious & repetitive to list exhaustively

ASM Overview


- Not a clear structure for illustrating/designing control flow
- What about generic memory/data
 - Do they really need to be part of the state?
If we have many bits of data, this would lead to a huge state
 - **E.g. state diagram for counter or shift register is pointless**
 - **32 bit counter have 2^{32} states**

ASM Overview

- Some problems analogous to before
 - Combinational:
 - Small problems – truth tables ok/easy
 - Adders, Muxes – TT get out of hand
 - Design 2 level ckt for 32 Adders : 64 inputs and 32 output using TT method, worst case delay (2^{63} or gate)
 - Worst case OR gate size or # of Product term $\Rightarrow 2^{N-1}-1$
 - CLA : prefix sum example

CLA: PrefixSum

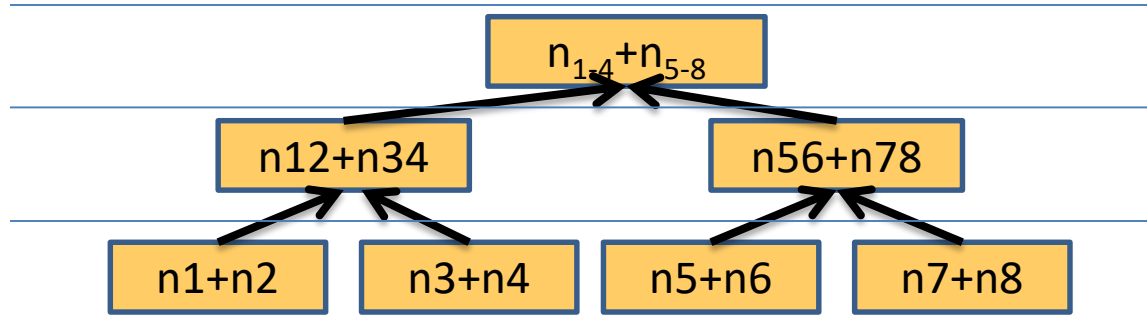- Sum of 8 numbers
 - Serial Require 1 adder, Delay n
($n_1+n_2+n_3+n_4+n_5+n_6+n_7+n_8$)
 - Parallel, require $n/2$ adder, Delay $\lg n$



- Prefix Sum of 8 numbers
 - 8 numbers, at each position sum upto that number
 - $n_1, n_1+n_2, n_1+n_2+n_3, \dots, n_1+n_2+\dots+n_8$
 - Two pass tree operation : $\log N$ time

ASM Overview

- Some problems analogous to before
 - Sequential:
 - Small – state diagrams easy
 - Real, Data – state diagrams not helpful

Algorithmic State Machine

Algorithmic State Machine –
representation of a Finite State Machine
suitable for FSMs with a larger number of
inputs and outputs compared to FSMs
expressed using state diagrams and state
tables.


ASM Overview

- We need to separate controller & data processor
 - Controller – What actions need to be taken?
What is fundamental operating mode?
 - Processor – Undertake the action.
Manipulate the data

**The ultimate Goal of this course : Design
using Control Path + Data Approach : RTL
Design**

ASM Overview


- Control and data path interaction

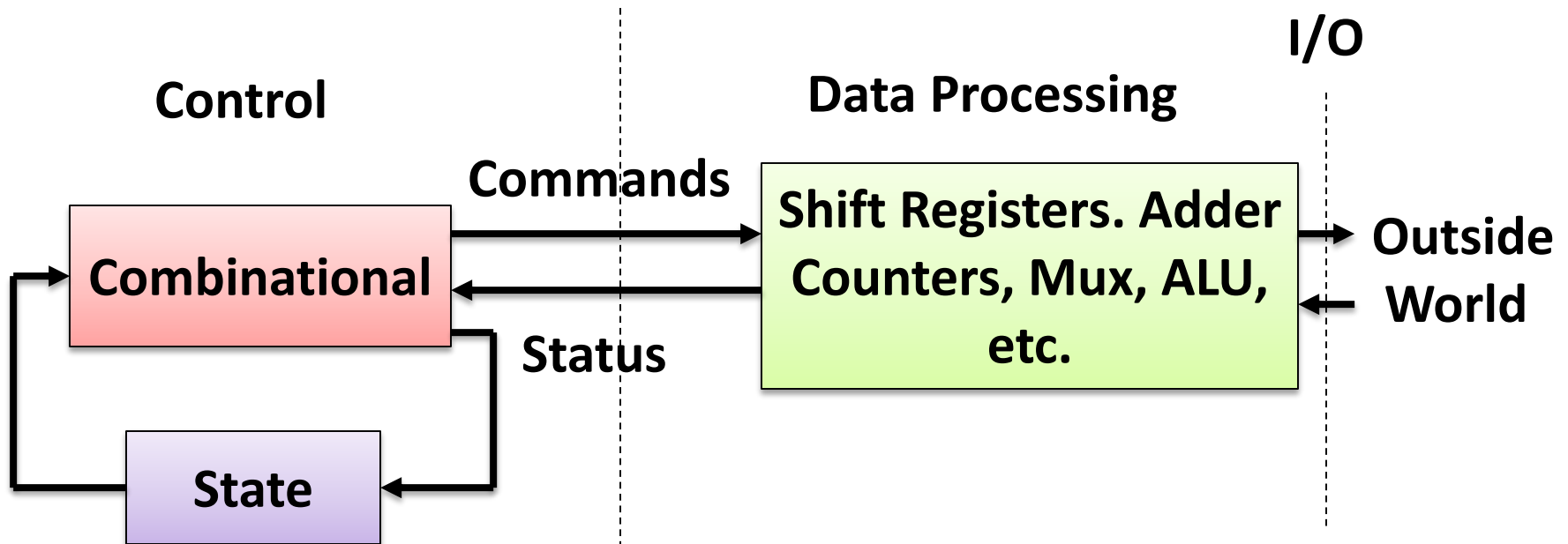


- Our circuit is now explicitly separated

ASM Overview : High Level

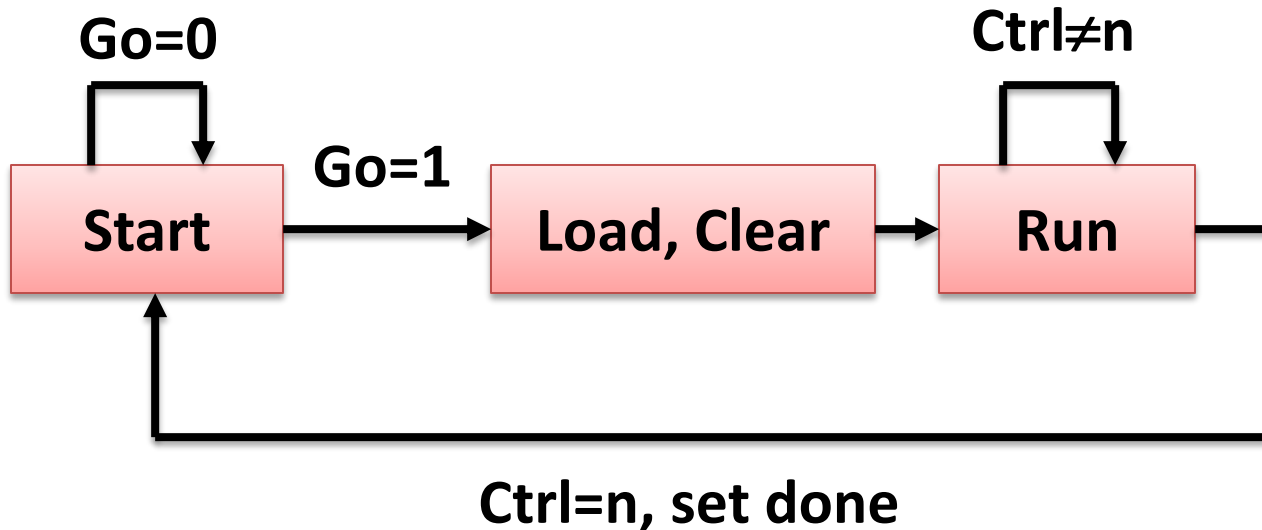- Ex. Serial Addition
- Control Part/Path



Serial Addition Data Path

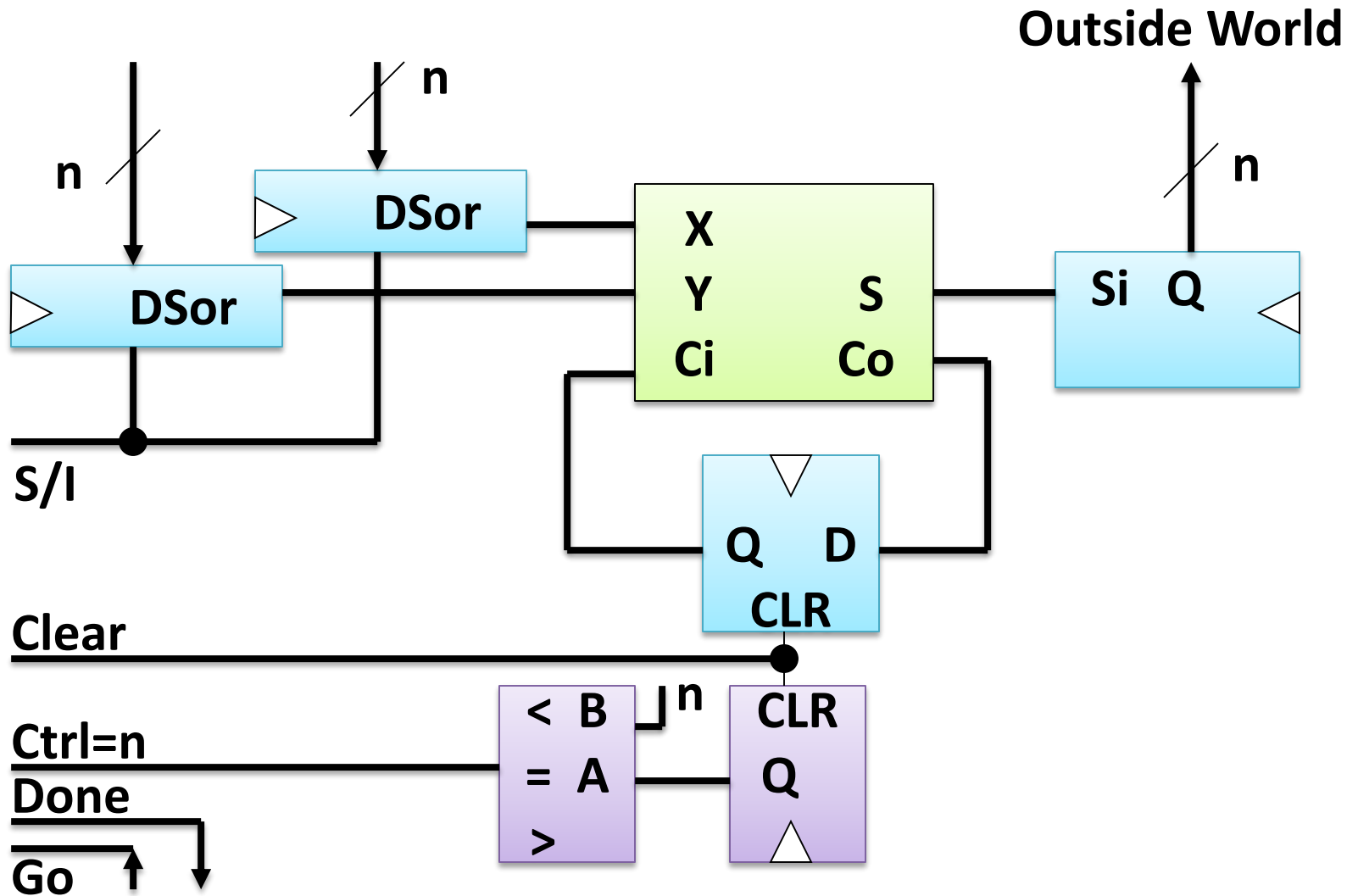

ASM Design : Data processing

- What sorts of manipulations of the input and output data are requested?
- How many/what sorts of things need to be stored?
- How to design
 - Ad hoc/creative/by insight
 - List requested operations/manipulations
 - Include initialization controls
 - Include status lines

ASM Design : Control logic

- All of the commands to the data proc. logic need to be controlled,
- And the status lines need to be monitored and acted upon.
- ASM charts are like state diagrams, but without specific drawbacks.
 - Don't list all inputs for each transition – don't care inputs
 - Don't list all outputs for each state – not changed outputs


ASM Design

- How to design - ASM chart/state diagram (**for small problems**)
 - State assignment
 - State table
 - Kmap-gates/FF/Reg Mux Dec/EPRROM, or, creatively, a combination of them


ASM Design

- ASM charts are like flowcharts, with a few crucial differences.
- Be careful, especially with timing.
- Three type components/Box
 - **State Box**
 - **Decision Box**
 - **Combinational Box/Transition Box/Conditional Box**


Elements used in ASM charts

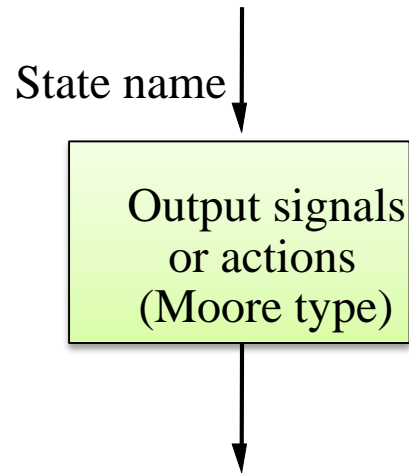

(a) State box

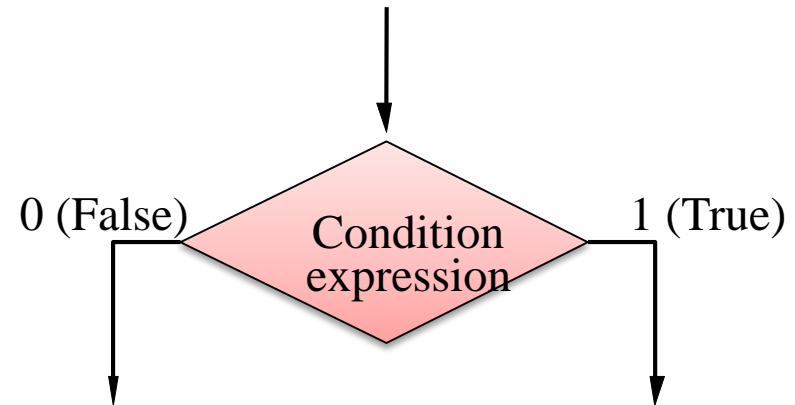

(b) Decision box

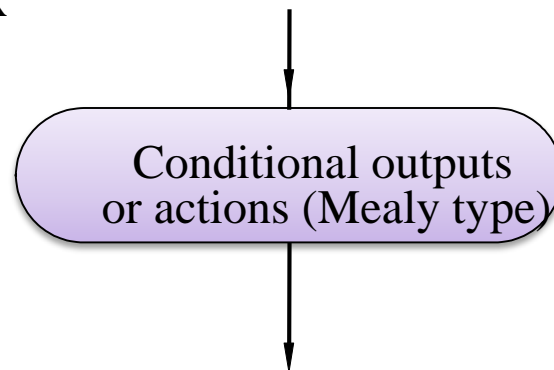

(c) Conditional output box