

CS221: Digital Design

<http://jatinga.iitg.ernet.in/~asahu/cs221>

RTL Examples with ASMD and FSMD

A. Sahu

Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati


RTL Design

- We need to separate controller & data processor
 - Controller – What actions need to be taken?
What is fundamental operating mode?
 - Processor – Undertake the action.
Manipulate the data

**The ultimate Goal of this course : Design
using Control Path + Data Approach : RTL
Design**

RTL Design


- Control and data path interaction

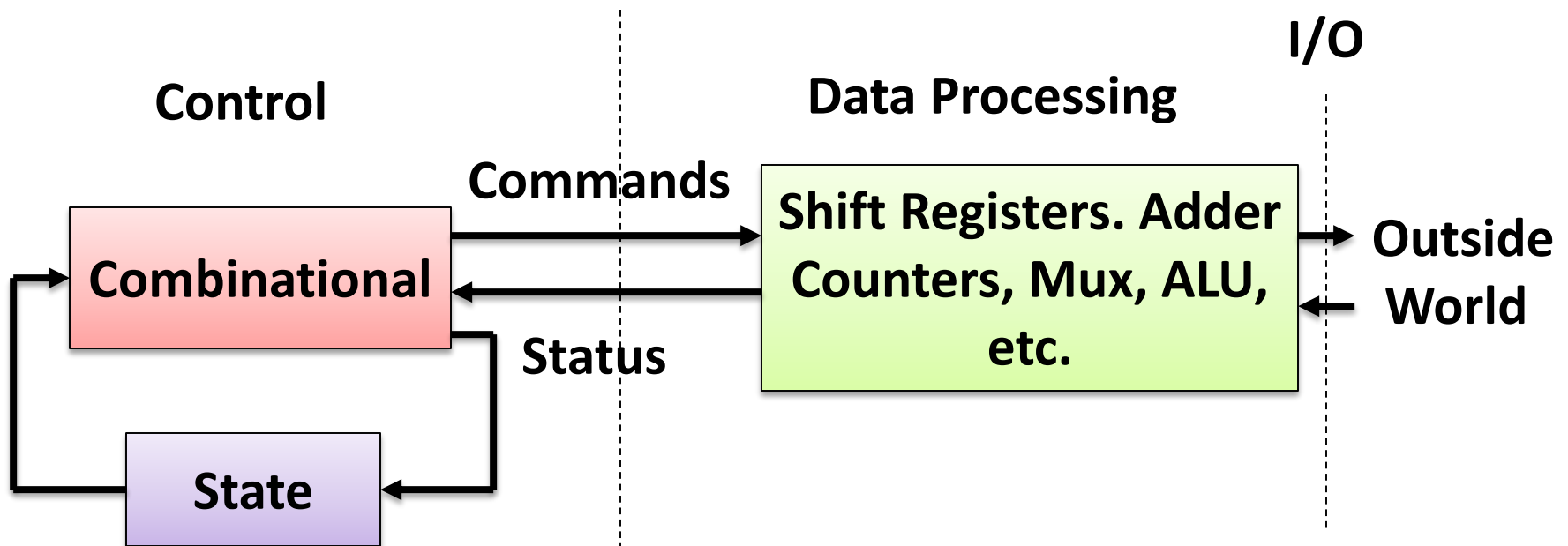


- Our circuit is now explicitly separated

ASM/FSM Overview : High Level

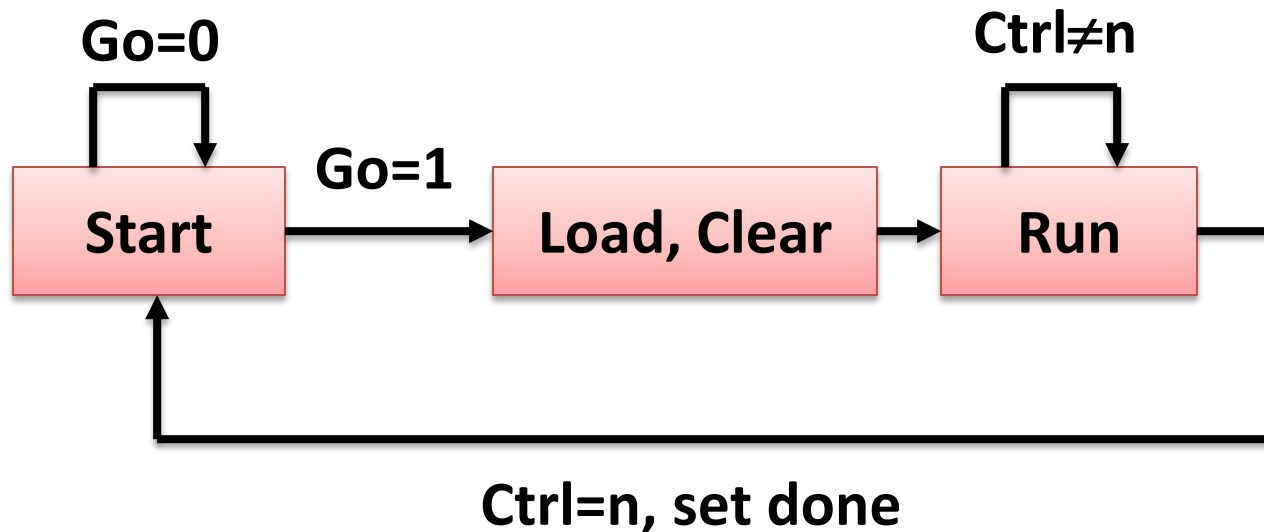- Ex. Serial Addition
- Control Part/Path




Serial Addition Data Path

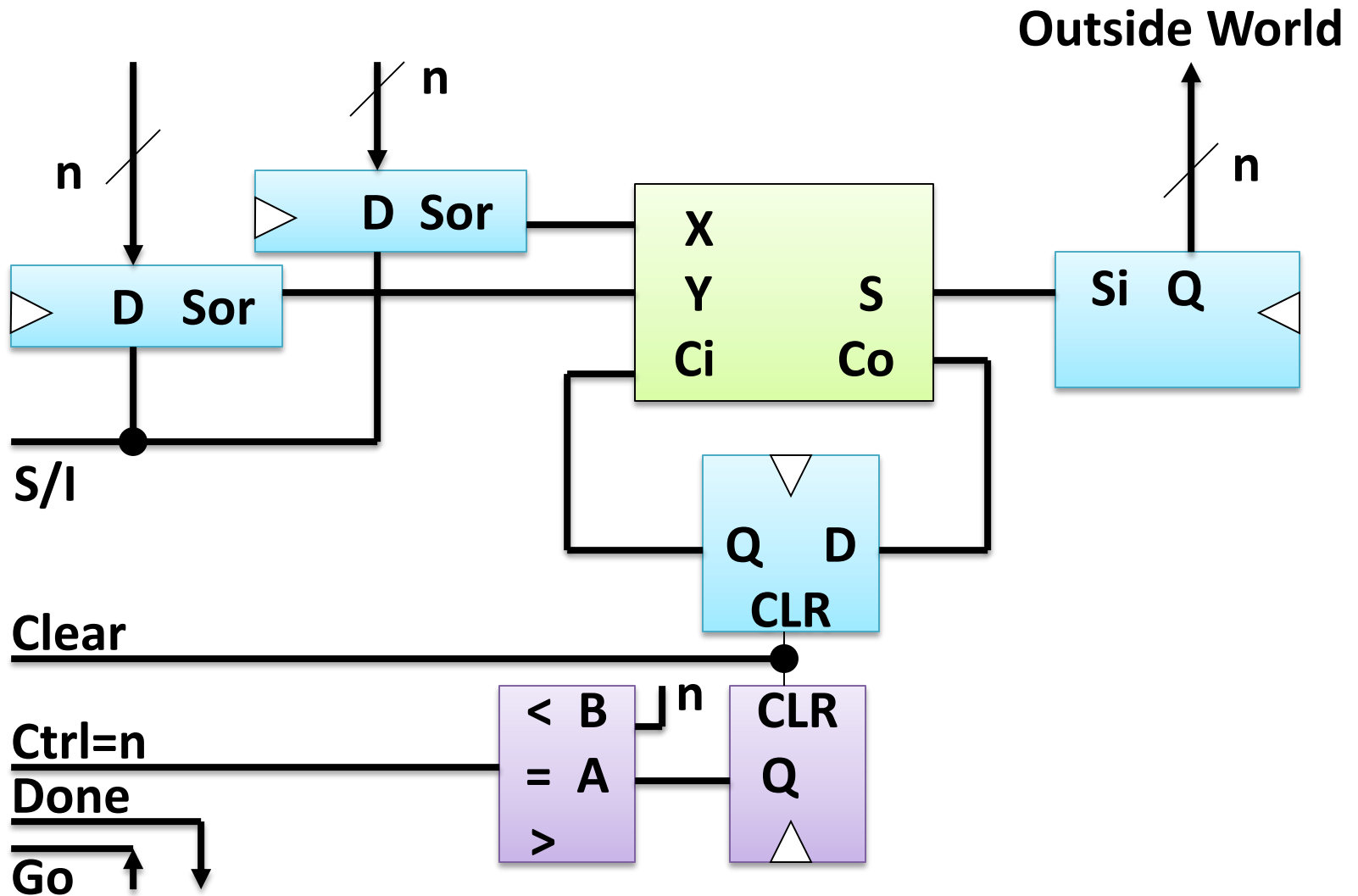


ASM Design

- ASM charts are like flowcharts, with a few crucial differences.
- Be careful, especially with timing.
- Three type components/Box
 - **State Box**
 - **Decision Box**
 - **Combinational Box/Transition Box/Conditional Box**


Elements used in ASM charts

 

(a) State box

 


(b) Decision box

 

(c) Conditional output box


ASM Blocks

One ASM block
execute in one cycle

 

ASM Timing

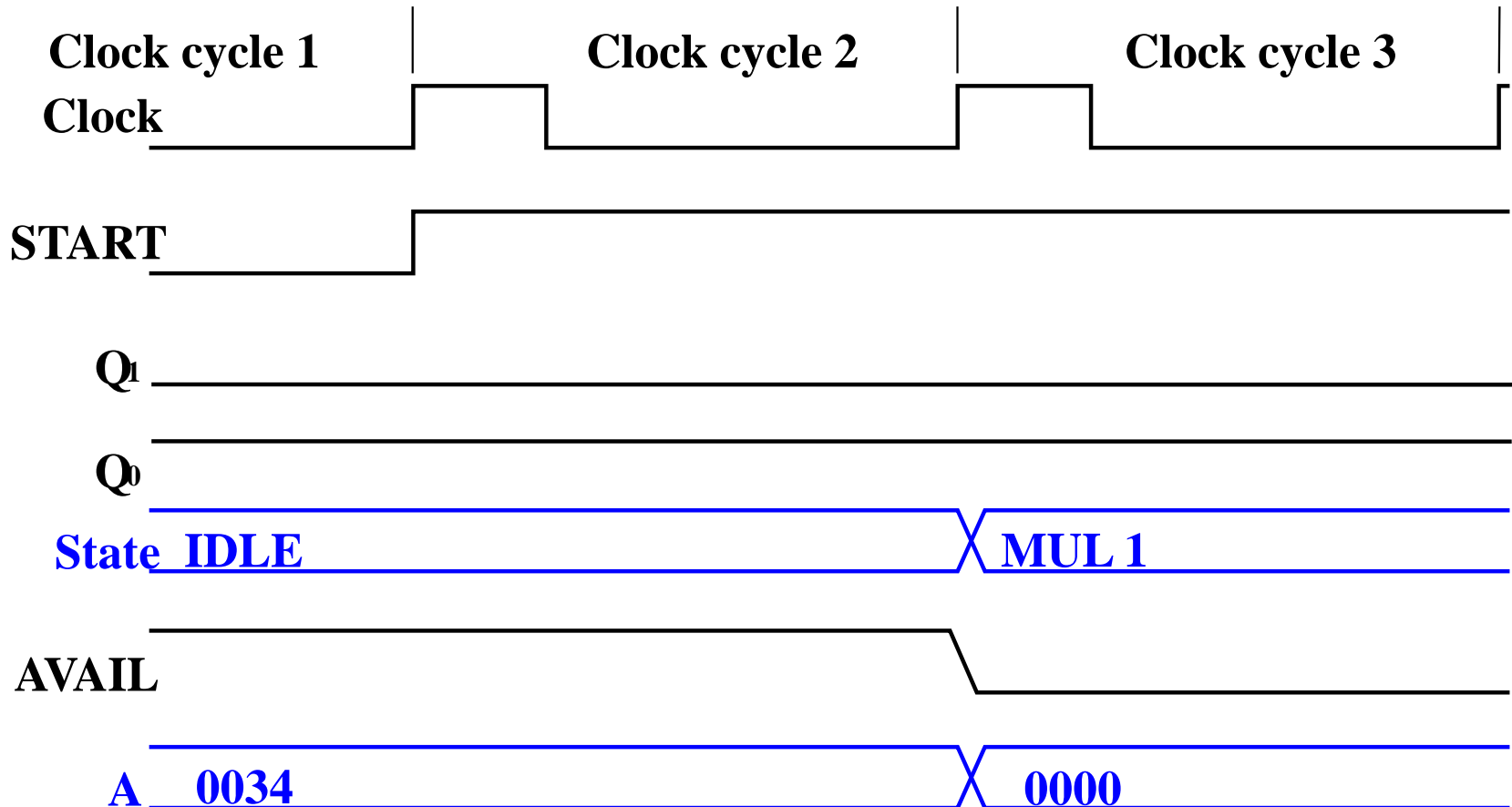- Outputs appear while in the state
- Register transfers occur at the clock while exiting the state - New value occur in the next state!



ASM : DP+CP Example

- Find the Data Path and ASM for the following problem: Addition of two numbers
 - We **first** need to load two registers (R1, R2) with some value.
 - We will **then** need to add the two Registers (R1, R2) and save the result in Register R3.
 - All these operations **should occur** if a “**start**” Signal is activated.


ASM : DP+CP Example

- Translation to Hardware:
 - We need to clear the registers first.
 - If the “**start**” signal is set to 0, I do nothing
 - Else If the “**start**” signal is set to 1, I will load R1, R2 with values
 - Next, enable R3 to be loaded (load-2) by the results of $R1+R2$


ASM : DP+CP Example

- Inputs/Outputs:
 - **start** is an input signal (Use a switch)
 - **clear** is an output signal generated and connected to R1, R2, R3
 - **load-1** is an output signal generated and connected to R1, R2
 - **load-2** is an output signal generated and connected to R3

Data Path

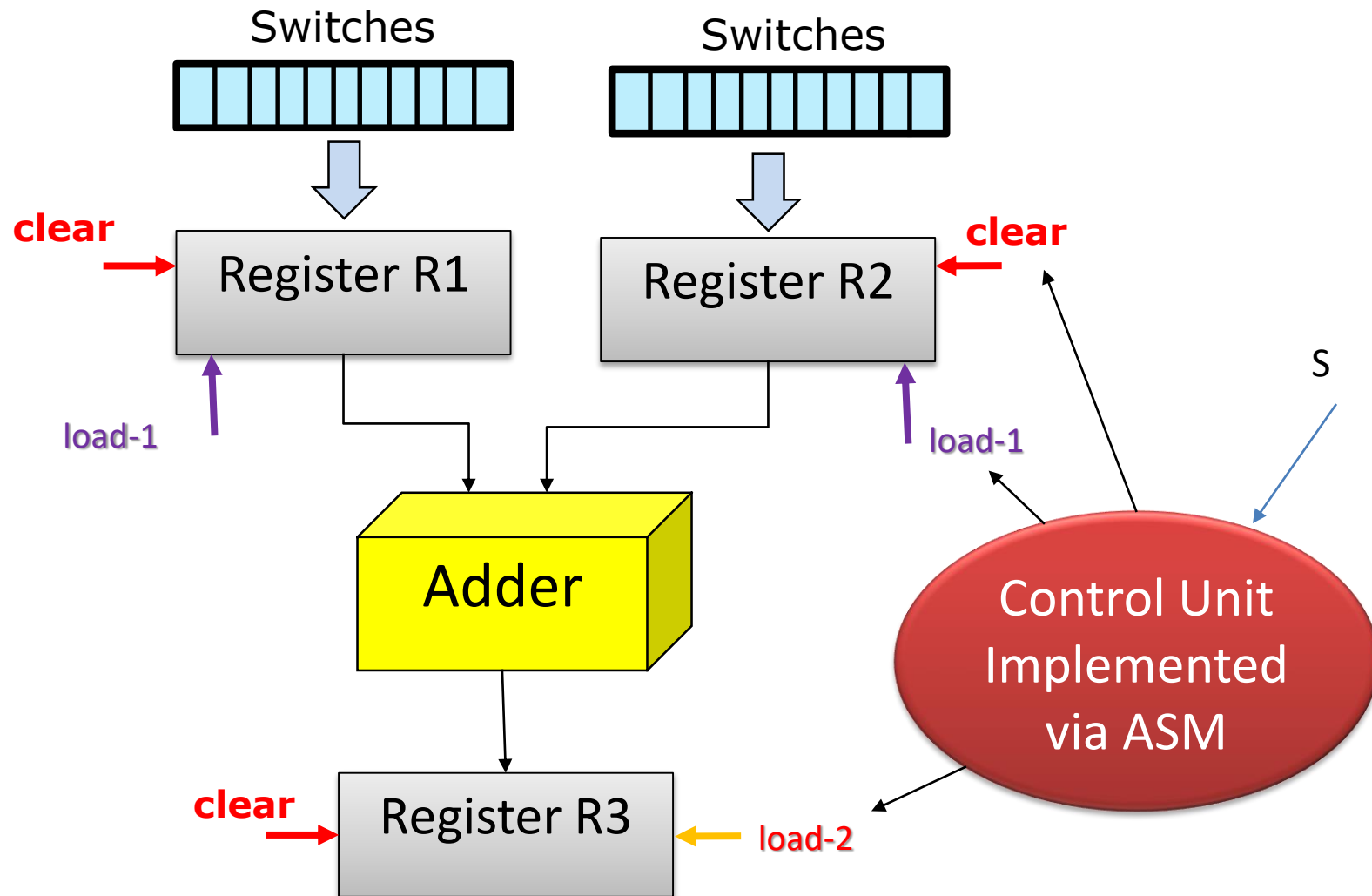

ASM : DP+CP Example

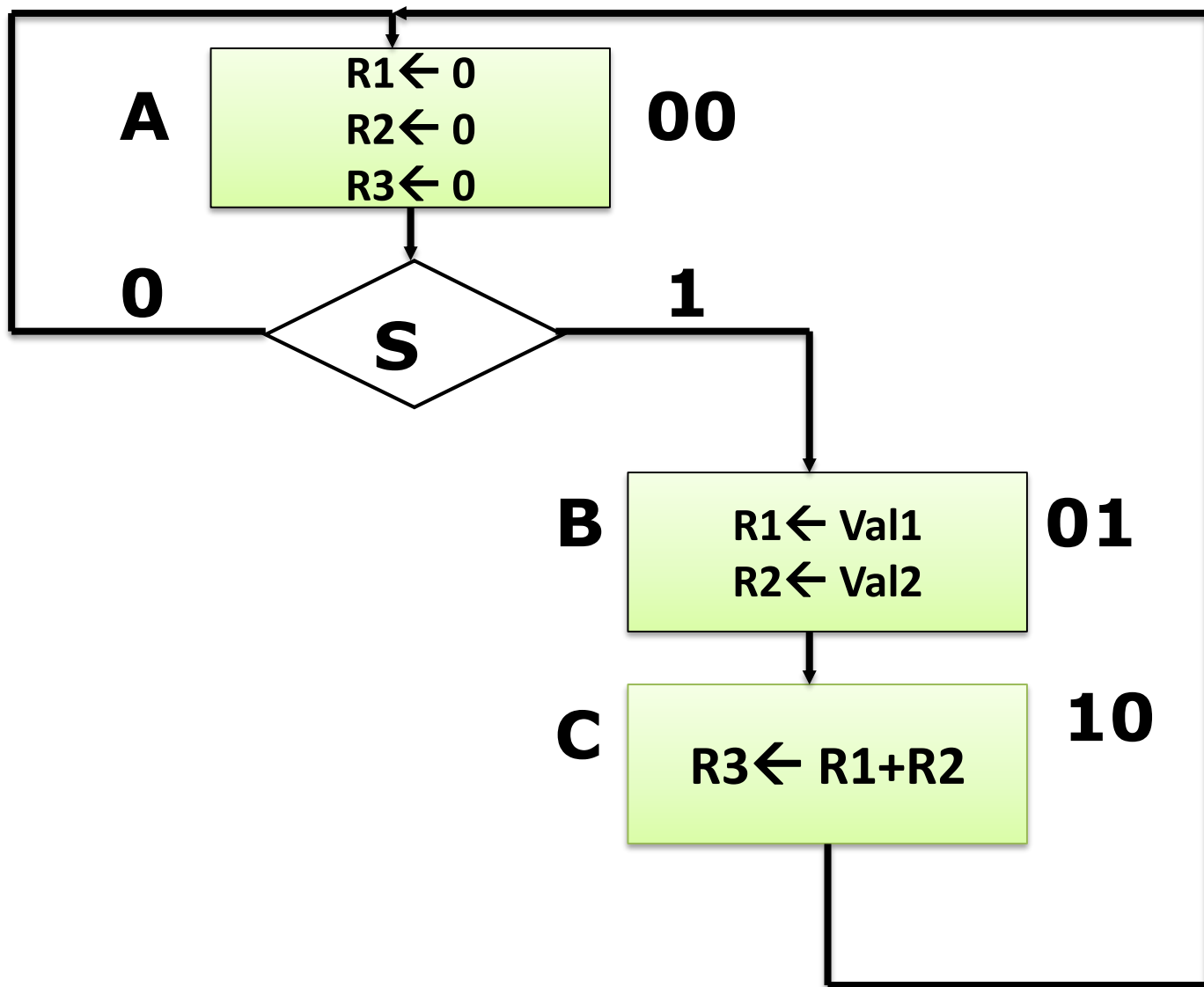

ASM : DP+CP Example Controller

PS		S	NS	
0	0	0	0	0
0	0	1	0	1
0	1	X	1	0
1	0	X	0	0
1	1	X	0	0


PS		CLR	L1	L2
0	0	1	0	0
0	1	0	1	0
1	0	0	0	1
1	1	X	X	X

ASM Charts: An Example


- A is a register;
- A_i stands for i^{th} bit of the A register.

$$A = A_3A_2A_1A_0$$

- E and F are single-bit flip-flops.

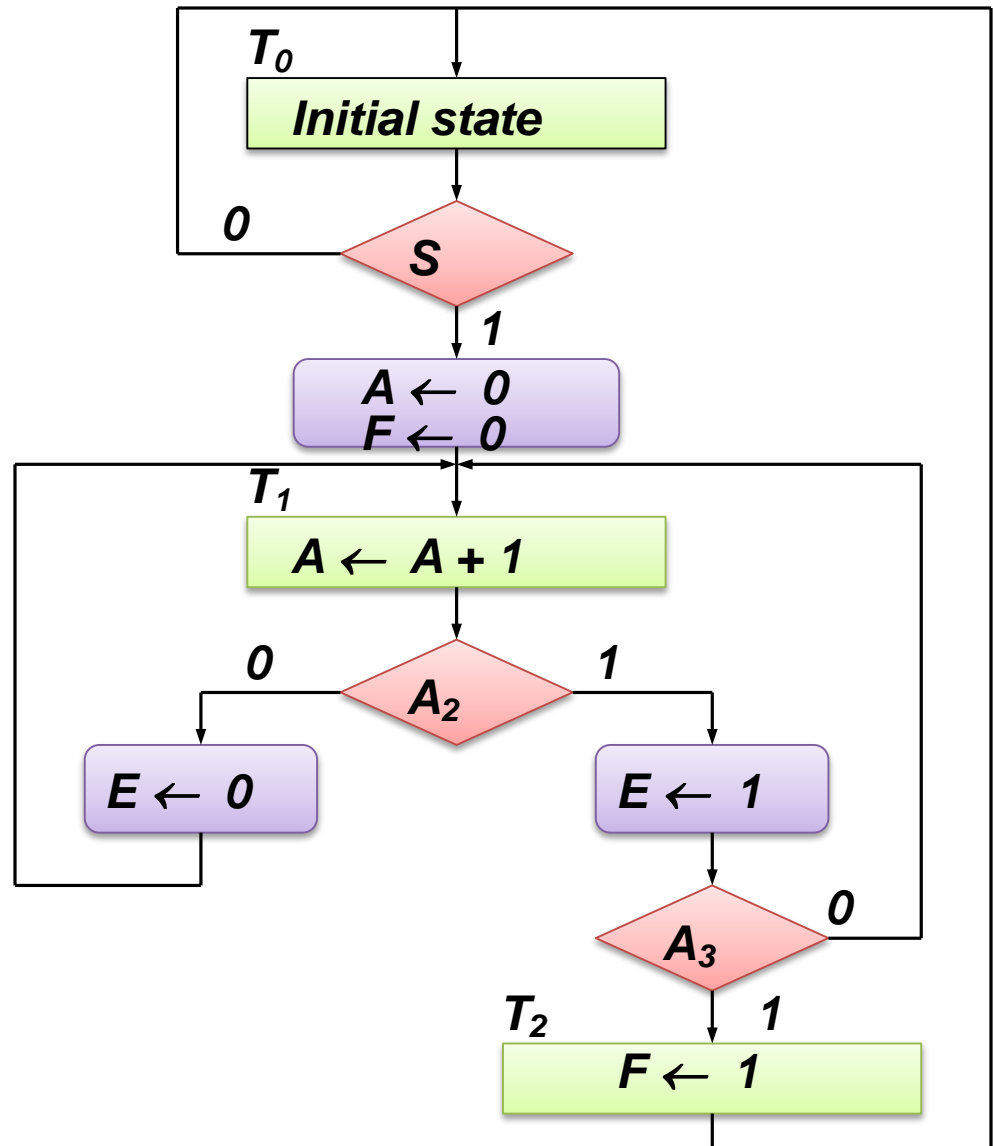

Timing in ASM Charts

 


Timing in ASM Charts

- Operations of ASM can be illustrated through a timing diagram.
- Two factors which must be considered are
 - Operations in an ASM block occur at the same time in ***one clock cycle***
 - Decision boxes are dependent on the status of the ***previous clock cycle*** (that is, they do not depend on operations of current block)

Timing in ASM Charts

CTR	E, F	Conditions	State
0000	1,0	$A_2=0, A_3=0$	T1
0001	0,0	--	--
0010	0,0	---	--
0011	0,0	---	--
0100	0,0	$A_2=1, A_3=0$	--
0101	1,0	--	--
0110	1,0	--	--
0111	1,0	--	--
1000	1,0	$A_2=0, A_3=1$	--
1001	0,0	--	--
1010	0,0	--	--
1011	0,0	--	--
1100	0,0	$A_2=1, A_3=1$	--
1101	1,0		T2
1101	1,1		T0

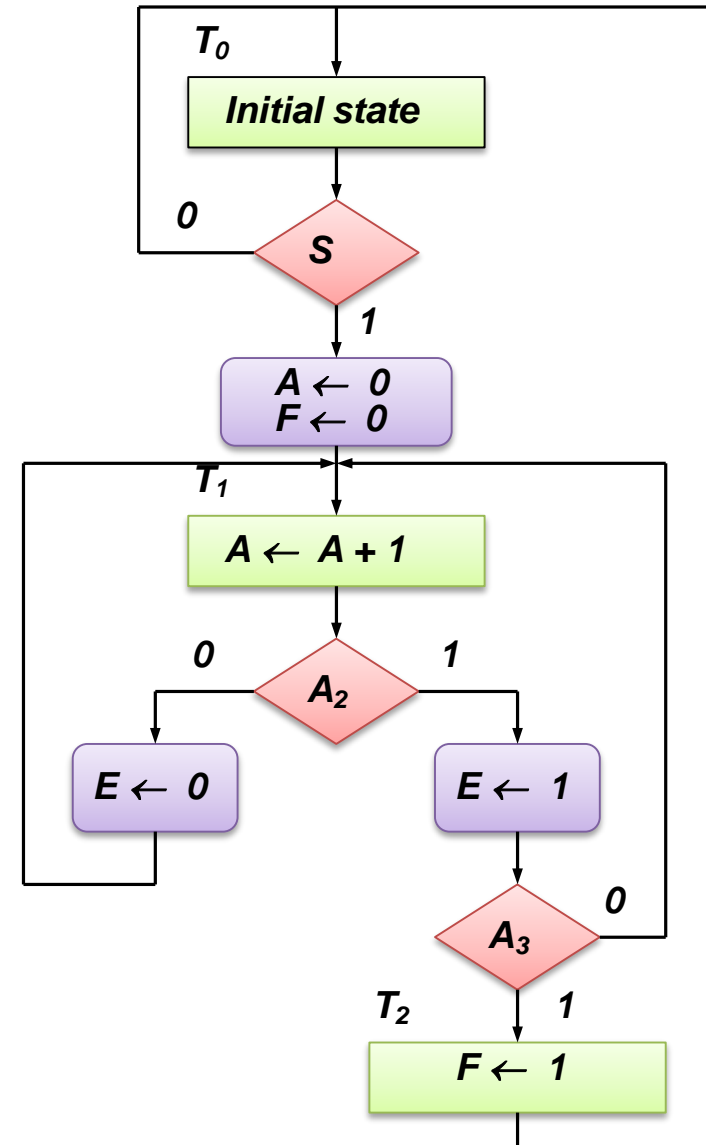


ASM Chart => Digital System

- ASM chart describes a digital system. From ASM chart, we may obtain:
 - Controller logic (via State Table/Diagram)
 - Architecture/Data Processor
- Design of controller is determined from the decision boxes and the required state transitions.
- Design requirements of data processor can be obtained from the operations specified with the state and conditional boxes.

ASM Chart => Controller

- Procedure:
 - Step 1: Identify all states and assign suitable codes.
 - Step 2: Formulate state table using
 - State** from state boxes
 - Inputs** from decision boxes
 - Outputs** from operations of state/conditional boxes.
 - Step 3: Obtain state/output equations and draw circuit.

ASM Chart => Controller

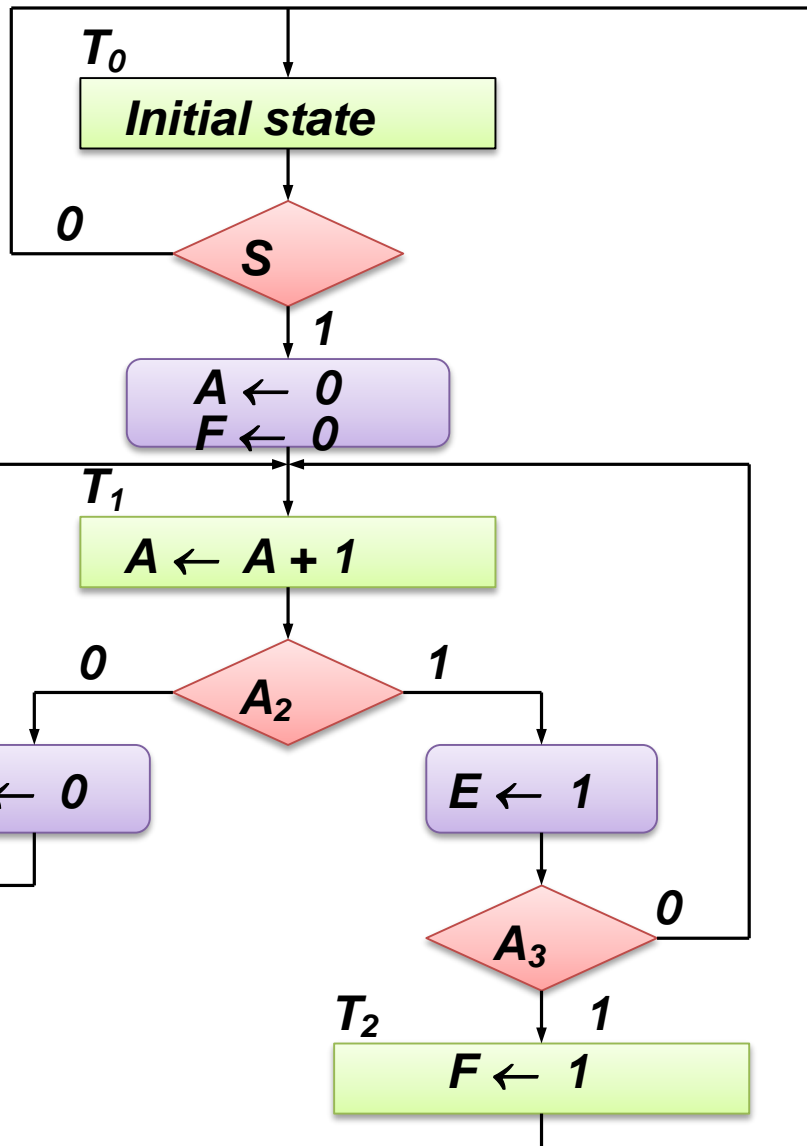

Assign codes to states:

$T_0 = 00$

$T_1 = 01$

$T_2 = 11$

Present state		inputs			Next state		outputs		
G_1	G_0	S	A_2	A_3	G_1^+	G_0^+	T_0	T_1	T_2
0	0	0	X	X	0	0	1	0	0
0	0	1	X	X	0	1	1	0	0
0	1	X	0	X	0	1	0	1	0
0	1	X	1	0	0	1	0	1	0
0	1	X	1	1	1	1	0	1	0
1	1	X	X	X	0	0	0	0	1

Inputs from conditions in decision boxes.

Outputs = present state of controller.

ASM Chart => Architecture/Data Processor


- Architecture is more difficult to design than controller.
- Nevertheless, it can be deduced from the ASM chart. In particular, the operations from the ASM chart determine:
 - What registers to use
 - How they can be connected
 - What operations to support
 - How these operations are activated.
- Guidelines:
 - always use high-level units
 - simplest architecture possible.

ASM Chart => Architecture/Data Processor



- Various operations are:
 - Counter incremented ($A \leftarrow A + 1$) when state = T_1 .
 - Counter cleared ($A \leftarrow 0$) when state = T_0 and $S = 1$.
 - E is set ($E \leftarrow 1$) when state = T_1 and $A_2 = 1$.
 - E is cleared ($E \leftarrow 0$) when state = T_1 and $A_2 = 0$.
 - F is set ($F \leftarrow 0$) when state = T_2 .
 - F is cleared ($F \leftarrow 0$) when state = T_0 and $S = 1$.
- Deduce:
 - One 4-bit register A (e.g.: 4-bit synchronous counter with clear/increment).
 - Two flip-flops needed for E and F (e.g.: JK/D flip-flops).

ASM Chart => Architecture/Data Processor

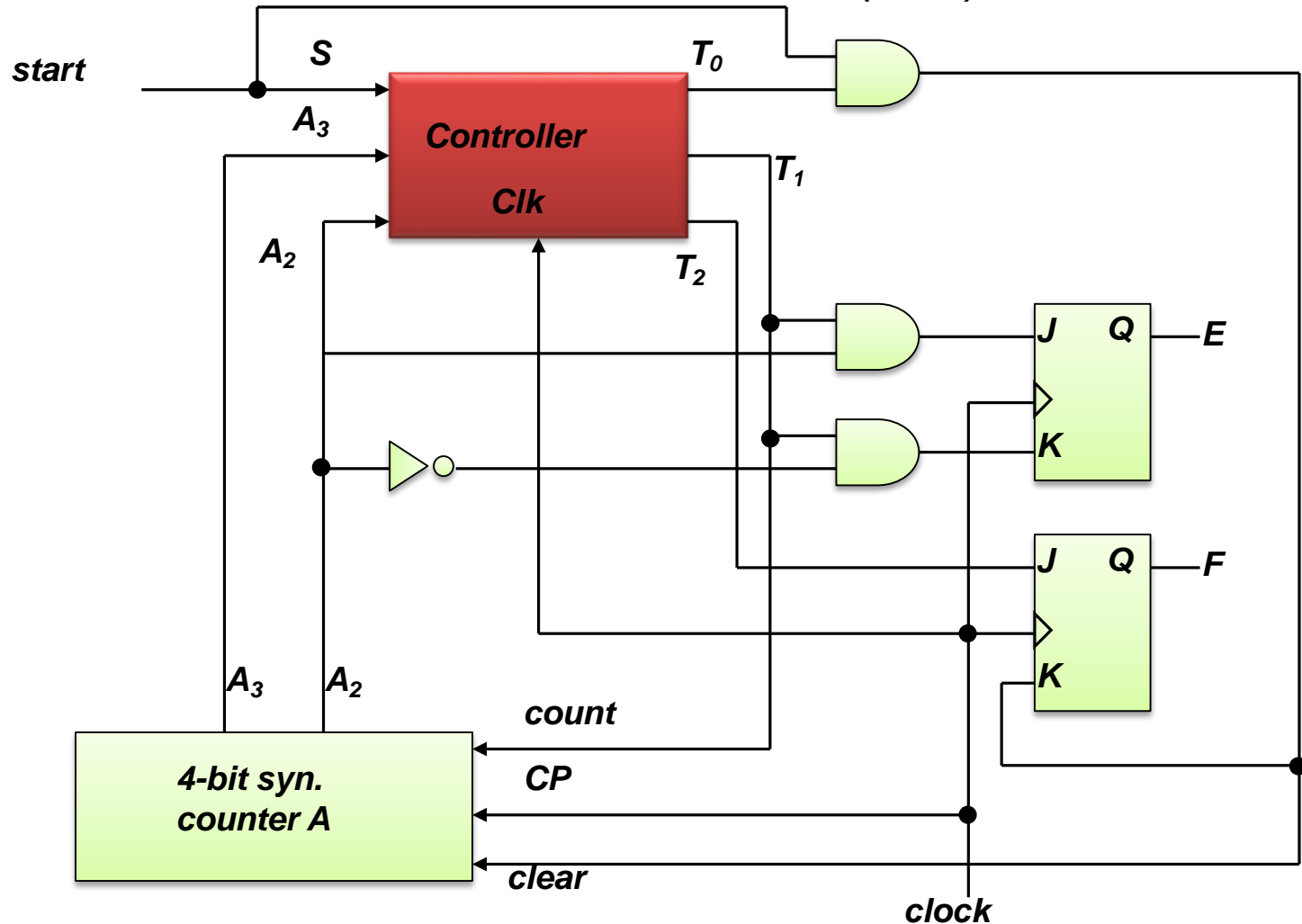$(A \leftarrow A + 1)$ when state = T_1 .
 $(A \leftarrow 0)$ when state = T_0 and $S = 1$.
 $(E \leftarrow 1)$ when state = T_1 and $A_2 = 1$.



ASM Chart => Controller

  

Assign codes to states:

$T_0 = 00$

$T_1 = 01$

$T_2 = 11$

Present state		inputs			Next state		outputs		
G_1	G_0	S	A_2	A_3	G_1^+	G_0^+	T_0	T_1	T_2
0	0	0	X	X	0	0	1	0	0
0	0	1	X	X	0	1	1	0	0
0	1	X	0	X	0	1	0	1	0
0	1	X	1	0	0	1	0	1	0
0	1	X	1	1	1	1	0	1	0
1	1	X	X	X	0	0	0	0	1

Inputs from conditions in decision boxes.

Outputs = present state of controller.

RTL: Multiplier Example

- Example: (101 x 011) Base 2
 - Note that the partial product summation for n digits, base 2 numbers requires adding up to n digits (with carries) in a column.
 - Note also $n \times m$ digit multiply generates up to an $m + n$ digit result (same as decimal).
- Partial products are:
101 x 0, 101 x 1, and 101 x 1

			1	0	1	
		x	0	1	1	
			<hr/>			
			1	0	1	
		1	0	1		
	0	0	0			
	<hr/>					
0	0	1	1	1	1	

Example (1 0 1) x (0 1 1) Again

- Reorganizing example to follow hardware algorithm:

		1	0	1				
	x	0	1	1				
→	0	0	0	0		Clear C A		
→	+	1	0	1		Multiplier0 = 1 => Add B		
→	0	1	0	1		Addition		
→	0	0	1	0	1	Shift Right (Zero-fill C)		
→	+	1	0	1		Multiplier1 = 1 => Add B		
→	0	1	1	1	1	Addition		
→	0	0	1	1	1	1	Shift Right	
→	0	0	0	1	1	1	1	Multiplier2 = 0 => No Add, Shift Right



Sequential Signed Multiplier

❖ ALU produces **32-bit** result + **Sign** bit


❖ **Sign** bit set as follows:

✧ **No overflow** → **Extend** sign-bit of result

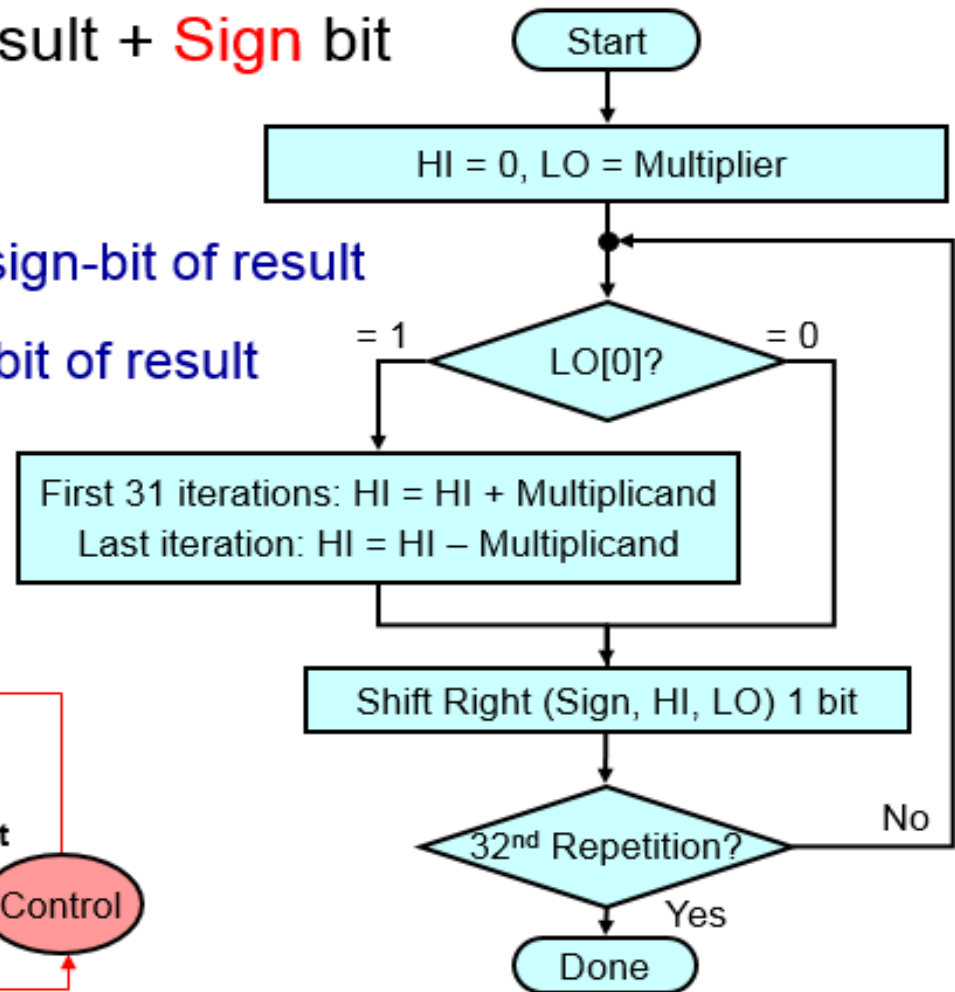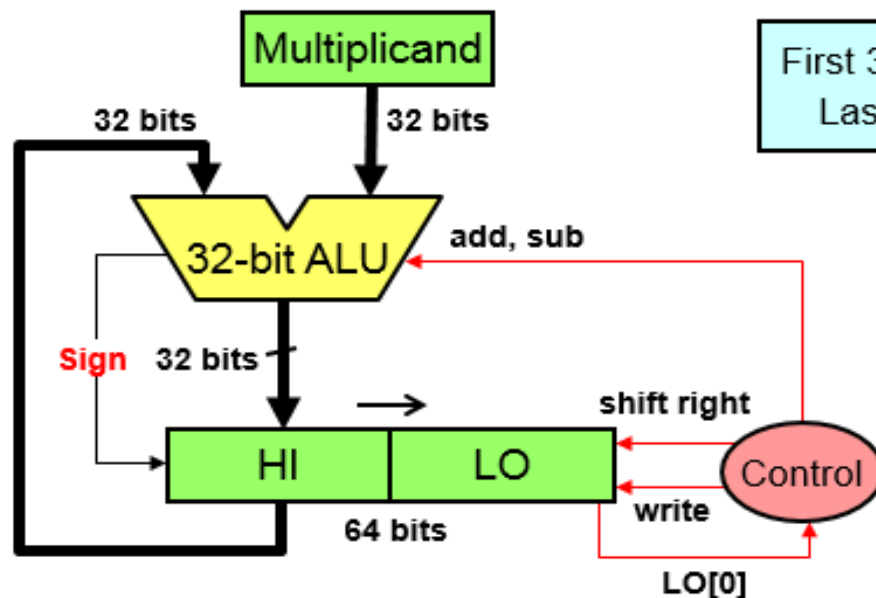✧ **Overflow** → **Invert** sign-bit of result



Multiplier Example: Block Diagram

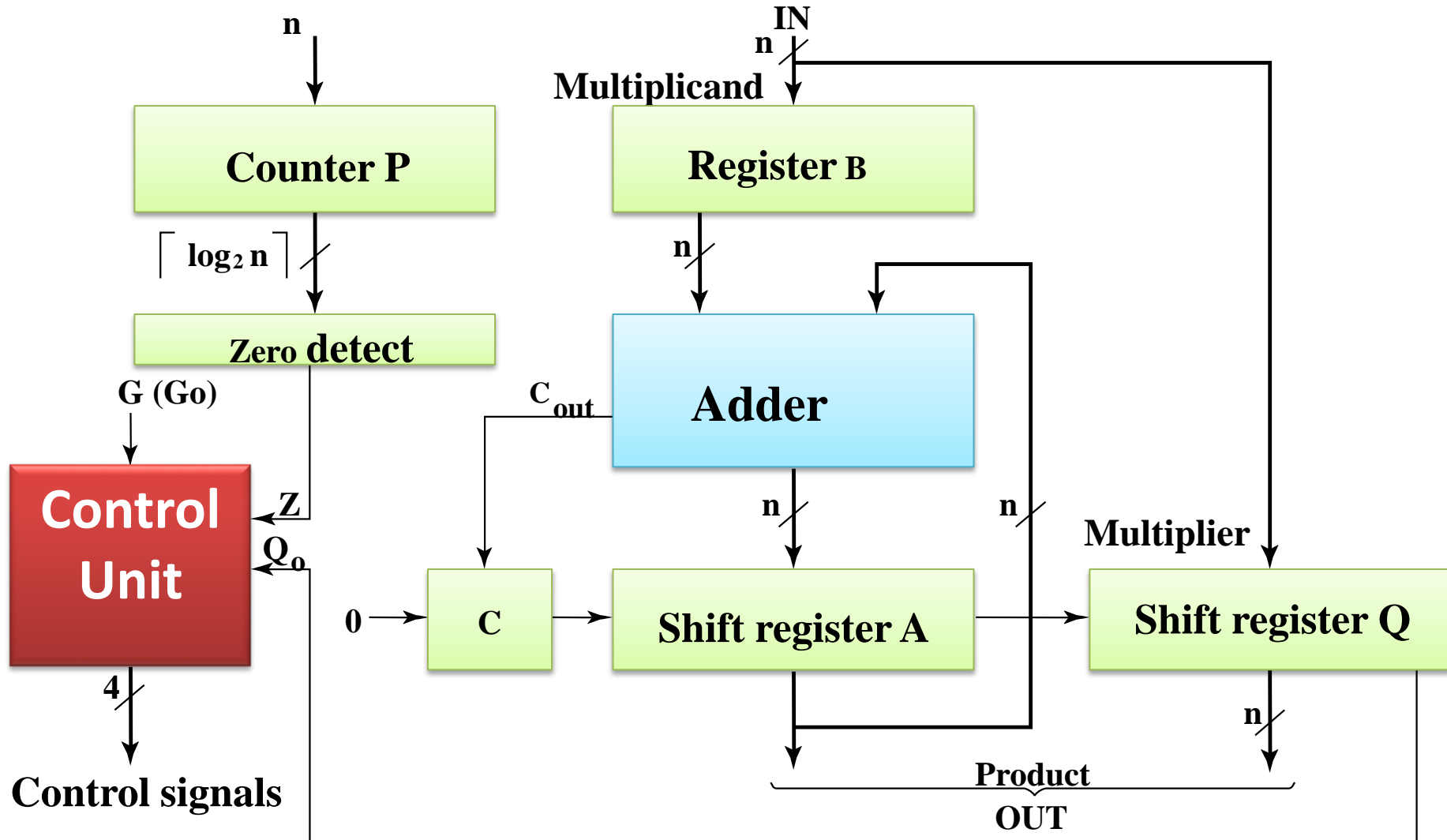


Multiplier Example: Operation

- Step1: The multiplicand (top operand) is loaded into register B.
- Step2: The multiplier (bottom operand) is loaded into register Q.
- Step3: Register C || A is initialized to 0 when G becomes 1.
- Step4: The partial products are summed iteratively in register C || A || Q.

Multiplier Example: Operation

- Step5: Each multiplier bit, beginning with the LSB, is processed (if bit is 1, use adder to add B to partial product; if bit is 0, do nothing)
- Step6: $C || A || Q$ is shifted right using the shift register
 - Partial product bits fill vacant locations in Q as multiplier is shifted out
 - If overflow during addition, the outgoing carry is recovered from C during the right shift
- Step 7: Steps 5 and 6 are repeated until Counter P = 0 as detected by Zero detect.
 - Counter P is initialized in step 4 to $n - 1$, n = number of bits in multiplier

Multiplier Example: ASM Chart

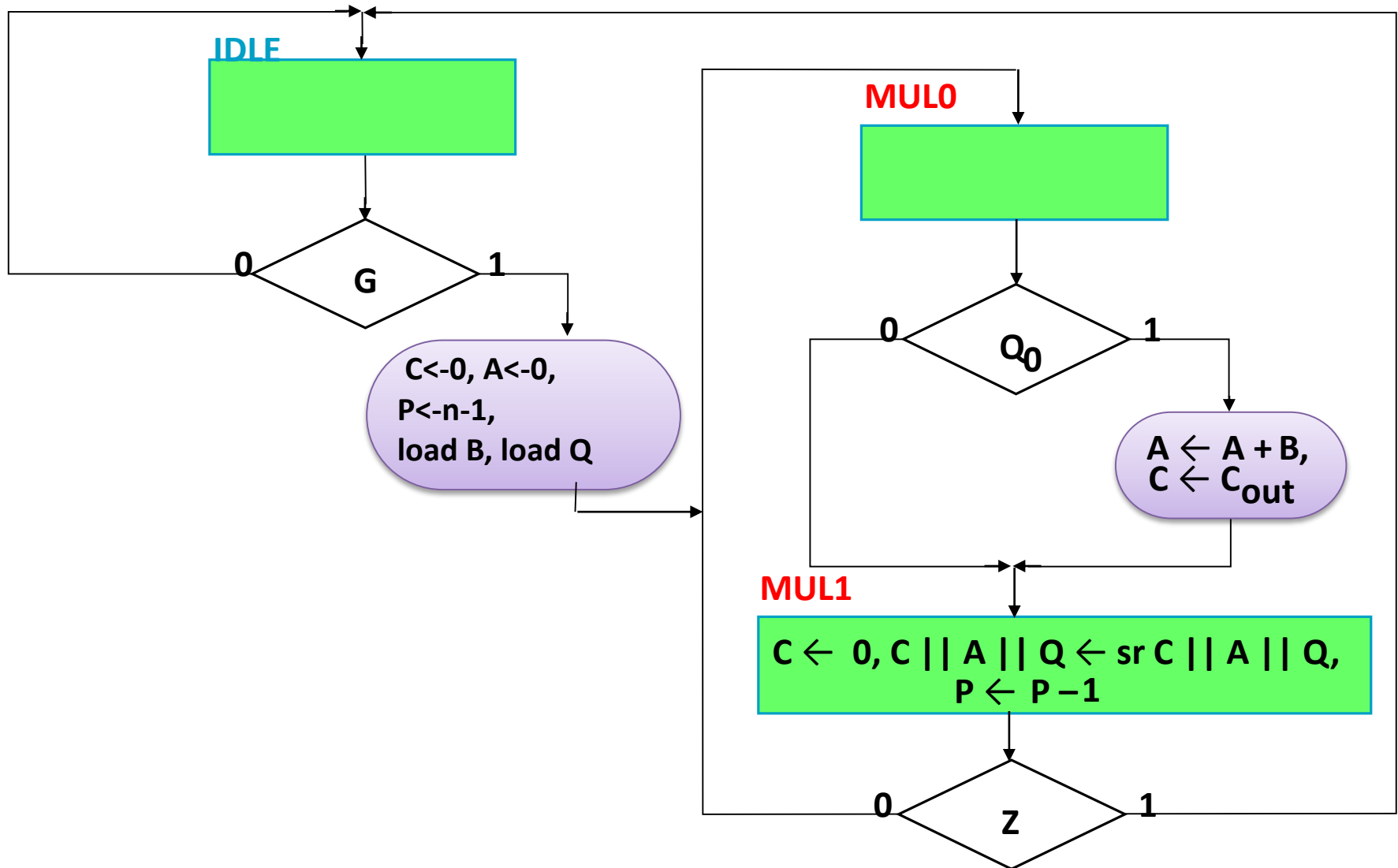

Multiplier Example: ASM Chart (continued)

- Combined Mealy - Moore output model
- **IDLE - state**
 - Input G is used as the condition for starting the multiplication, and
 - *C, A, and P are initialized and Load B, Load Q*
- **MUL0 - state**
 - Conditional addition is performed based on the value of Q_0 .
- **MUL1 - state**
 - Right shift is performed to capture the partial product and position the next bit of the multiplier in Q_0
 - the terminal count of 0 for down counter P is used to sense completion or continuation of the multiply.

Multiplier Example: Control Signal Table

Control Signals for Binary Multiplier

Block Diagram Module	Microoperation	Control Signal Name	Control Expression
Register A:	$A \leftarrow 0$ $A \leftarrow A + B$ $C \parallel A \parallel Q \leftarrow sr C \parallel A \parallel Q$	Initialize Load Shift_dec	$IDLE \cdot G$ $MUL0 \cdot Q$ $MUL1$
Register B:	$B \leftarrow IN$	Load_B	LO ADB
Flip-Flop C:	$C \leftarrow 0$ $C \leftarrow C_{out}$	Clear_C Load	$IDLE \cdot G + MUL1$ —
Register Q:	$Q \leftarrow IN$ $C \parallel A \parallel Q \leftarrow sr C \parallel A \parallel Q$	Load_Q Shift_dec	LO ADQ —
Counter P:	$P \leftarrow n - 1$ $P \leftarrow P - 1$	Initialize Shift_dec	— —